



Module 4 epc 1 - Operational amplifiers

Electronic principles and circuits (Visvesvaraya Technological University)



Scan to open on Studocu

Module - 4

Negative feedback


- stabilizes the voltage gain
- Increases input impedance.
- Decreases output " .

Four Types of Negative feedback

1. Voltage-controlled voltage source (VCVS)
2. Current- " " (ICVS)
3. Voltage- " " current source (VCIS)
4. Current- " " " (CICIS)

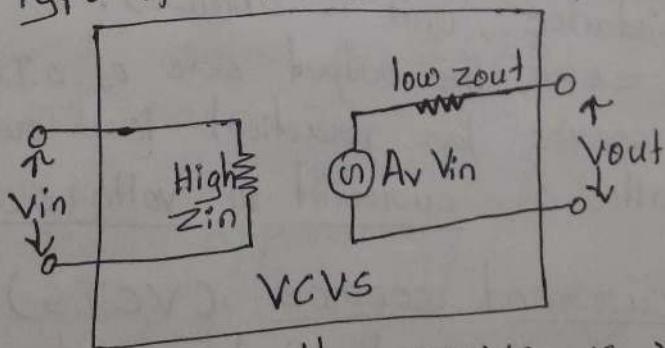1. Voltage controlled voltage source (VCVS)


- The circuit with negative feedback that accepts voltage input & produces voltage output , is called voltage of controlled voltage source .
- Type of voltage amplifier.



- Fig shows the VCVS, a voltage amplifier.
- It is an ideal voltage amplifier because it has ideal characteristic like stabilized voltage gain , infinite input impedance & zero output impedance.
- Practical circuit has high-Zin , low-Zout.
- Av is the voltage gain
- As Zout approaches zero , output side of a VCVS is a stiff voltage source to any practical load resistance.


RK

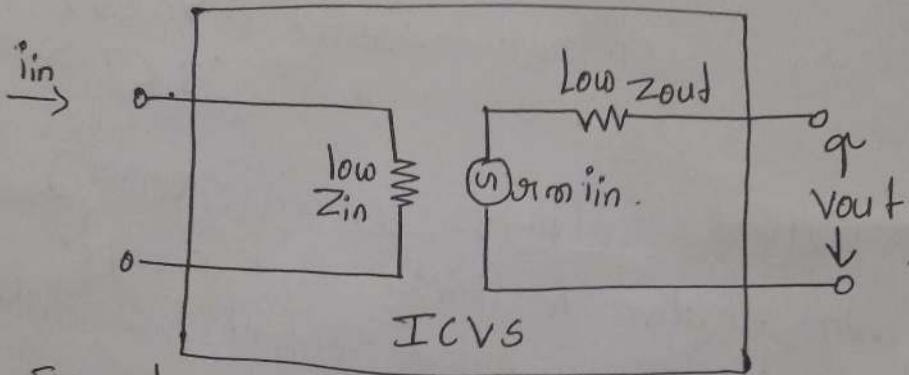2. Current controlled voltage source (ICVS)
- Type of the -ve feedback circuit that accepts current as an input & gives voltage as an output is called current controlled voltage source.
 - Input current controls an output voltage.
 - Also called as transresistance amplifier.
 - Because in $\frac{V_{out}}{I_{in}}$ has unit ohms. & trans means taking ratio of an output quantity to an input quantity.
 - Type of transresistance amplifier.



- Fig shows ICVS.
- It has $Z_{in} = \text{low}$ $Z_{out} = \text{low}$.
- gm is the transresistance, unit is ohm (Ω).
- As Z_{out} approaches zero, the output side of a ICVS is a stiff voltage source for practical load resistances.
- This circuit is also called as current to voltage converter.

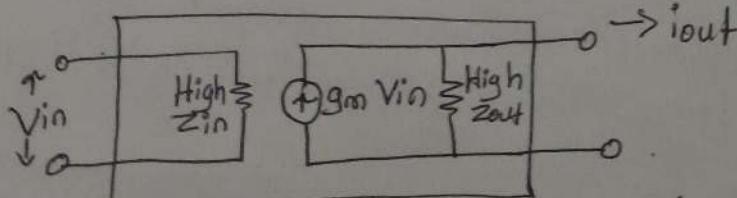3. Voltage controlled current source (VCVIS)
- Type of the -ve feedback circuit that accepts voltage as an input & gives current as an output is called voltage controlled current source.
 - It is also called as voltage to current converter.
 - " " " " " trans conductance amplifier.
 - Goi trans → ratio, conductance → (i_{out}/v_{in}) mhos or Siemens.




- Type of transconductance amplifier.

- Fig shows a VCI S.
 → It has $Z_{in} = \text{high}$, $Z_{out} = \text{high}$
 → g_m represents transconductance.
 → As Z_{out} approaches infinity, the output side of a VCI S is a stiff current source for load circuit.

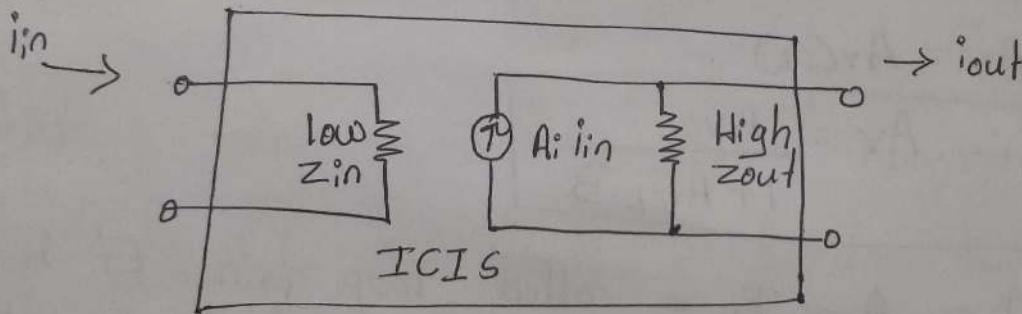4. Current-controlled current source (ICIS)

- The type of a negative feedback that accepts current as a input & gives current as a output is called current-controlled current source.
 → It is a type of current amplifier.
 → It is a ideal current amplifier with stabilized current gain, zero input impedance & infinite output impedance.



→ Fig shows an ICIS.


→ It has $Z_{in} = \text{low}$, $Z_{out} = \text{high}$.

→ A_i is the current gain.

→ Z_{out} approaches infinity, the output side of a VCVS is a stiff current source to any practical load resistance.

VCVS voltage gain

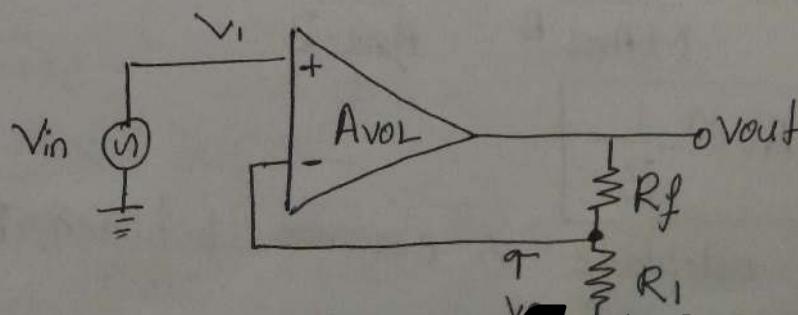→ non inverting amplifier circuit act as VCVS, therefore consider this to derive voltage gain.



RK

Exact closed loop voltage gain

- A_{VOL} is the open loop voltage gain of the amplifier.
- V_{out} is feed back to the non-inverting input using voltage divider network called feedback network. It has a feedback gain or feedback fraction B .
- $$\therefore B = \frac{V_{out}}{V_{input}} = \frac{V_2}{V_{out}}$$

Using I

- B is also called as feedback attenuation factor.
- Closed loop voltage gain is given by,

$$A_v(CCL) = \frac{A_{VOL}}{1 + A_{VOL}B}$$

$$A_v = A_v(CCL)$$

$$\boxed{\therefore A_v = \frac{A_{VOL}}{1 + A_{VOL} \cdot B}}$$

Loop gain - $A_{VOL} \cdot B$ is called loop gain. It is the voltage gain of the forward and feedback paths.

- Larger loop gain stabilizes the loop gain and produces enhanced (better) gain stability, distortion, offsets, input impedance & output impedance.

Ideal closed loop voltage gain

- For the better performance of the VCVS it is good to keep loop gain $\gg 1$ i.e $A_{VOL}B \gg 1$

$$\therefore A_v = \frac{A_{VOL}}{1 + A_{VOL} \cdot B} \cong \frac{A_{VOL}}{A_{VOL} \cdot B}$$

$$\boxed{A_v \cong \frac{1}{B}}$$

- Formula to calculate % error between ideal & exact voltage gain.

$$\% \text{ error} = \frac{100 \%}{1 + A_{\text{vol}} \cdot B}$$

Using Ideal Equation - we can derive B & Av in terms of resistance.

→ according to voltage divider rule.

$$V_2 = \frac{R_f}{R_f + R_1} \cdot V_{\text{out}}$$


$$\frac{V_2}{V_{\text{out}}} = B = \frac{R_f}{R_f + R_1}$$

$$A_v \stackrel{\text{defn}}{=} \frac{1}{B} \quad \therefore A_v = \frac{R_f + R_1}{R_1}$$

$$A_v = \frac{R_f}{R_1} + 1$$

which is same as voltage gain of non-inverting amplifier.

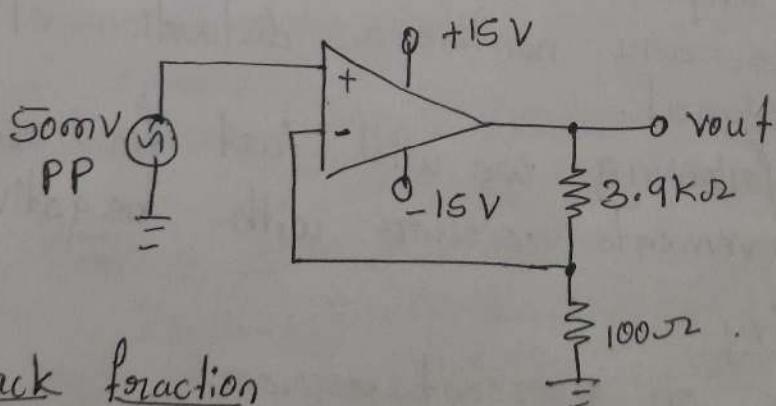Example - Calculate the feedback fraction, the ideal closed loop voltage gain, the percent error and the exact closed-loop voltage gain. Use a typical A_{vol} of 100,000 for the 741C.



Feedback fraction

$$B = \frac{R_f}{R_1 + R_f} = \frac{100\Omega}{100\Omega + 3.9k\Omega} = 0.025$$

Ideal closed loop gain

$$A_v = \frac{1}{B} = \frac{1}{0.025} = 40$$

The % error

$$\% \text{ error} = \frac{100\%}{1 + A_{\text{VOL}} B} = \frac{100\%}{1 + (100,000) (0.025)} = 0.0$$

exact closed loop gain (Av)

$$Av = Av - \frac{0.04\%}{(\% \text{ error})} \cdot Av$$

$$= 40 - (0.04\%) 40$$

$$Av = 39.984$$

OR

$$Av = \frac{A_{\text{VOL}}}{1 + A_{\text{VOL}} B} = \frac{100,000}{1 + (100,000) (0.025)} = 39.984$$

Practice - change the feedback resistor from $3.9k\Omega$ to $4.9k\Omega$. calculate the feedback fraction, the ideal-closed loop voltage gain, the % error & the exact closed loop gain.

Other VCVS Equations

→ Negative feedback in a VCVS amplifier increases the input impedance, decreases the output impedance and reduce any nonlinear distortion of the amplified signal.

→ We will just find out how much improvements occurs with negative feedback.

Gain stability

→ It depends on percent error

→ The smaller the percent error, the better the stability.

→ The worst case error of closed loop voltage gain occurs when the open-loop voltage gain is minimum.

RK


$$\% \text{ Maximum error} = \frac{100 \%}{1 + A_{VOL(\min)} B}$$

According to data sheet of 741 IC
 $A_{VOL(\min)} = 20,000$

$$\therefore \% \text{ maximum error} = \frac{100 \%}{500} = 0.2 \%$$

→ In mass production the closed-loop voltage gain of any VCVS amplifier is ~~is~~ within 0.2% of ideal value.

Closed-Loop input impedance

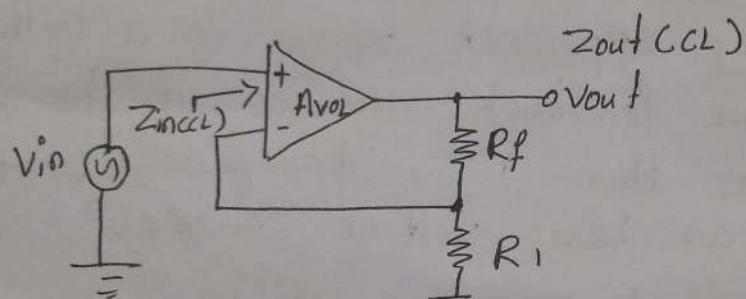

→ Exact equation for the closed-loop input impedance of the VCVS amplifier.

$$Z_{in(CL)} = (1 + A_{VOL} B) R_{in} \| R_{cm}$$

R_{in} = the open loop input resistance of the op-amp.

R_{cm} = the common-mode input resistance of the op-amp.

From the data sheet $R_{in} = 2 M\Omega$

" " " " " $R_{cm} = R_E = 100 M\Omega$

→ often R_{cm} is ignored because it is large

$$\therefore Z_{in(CL)} \approx (1 + A_{VOL} B) R_{in}$$

→ In practical VCVS amplifier $(1 + A_{VOL} B) \gg 1$.
 $Z_{in(CL)}$ will be extremely high.

→ ultimate limit on $Z_{in(CL)}$ is

RK $Z_{in(CL)} = R_{cm}$

→ $Z_{in(CL)}$ is larger than R_{in} but less than ultimate limit on R_{cm} .

Closed-loop output impedance

→ Overall output impedance looking back into the VCVS amplifier is called closed loop output impedance. ($Z_{out(CL)}$)

$$\rightarrow \text{Equation for } Z_{out(CL)} = \frac{R_{out}}{1 + A_{VOL} B}$$


→ $R_{out} \rightarrow$ Open-loop output resistance of the opamp (as per data sheet of 741C $R_{out} = 75\Omega$)

→ $A_s (1 + A_{VOL} \cdot B) \gg 1$ in practical VCVS amplifiers $Z_{out(CL)}$ is less than 1Ω .


→ $Z_{out(CL)}$ may approach zero in a voltage follower.

→ VCVS negative feedback reduces it to values much smaller than 1Ω . Therefore $Z_{out(CL)}$ approaches an ideal voltage source.

Non linear Distortion

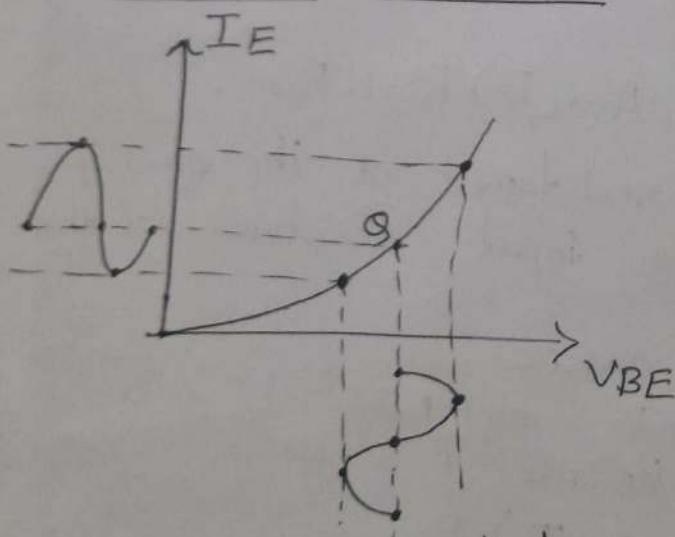

non-linear distortion

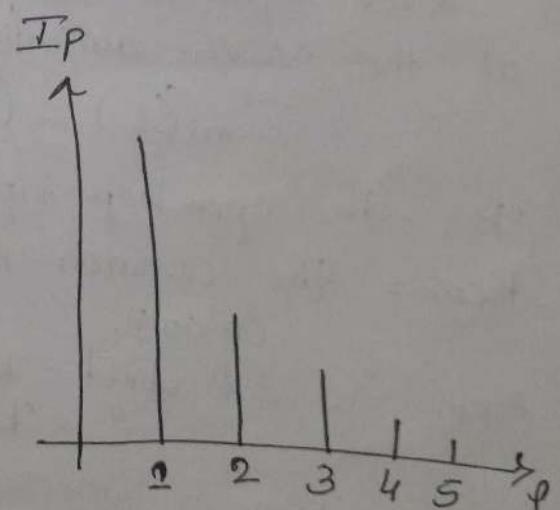

Fundamental & harmonics

→ In fig non linear graph of the base-emitter diode distorts a large signal by elongating the positive half cycle & compressing the -ve half cycle.

→ If 1kHz is the fundamental frequency rest 2, 3, 4, 5 kHz are the harmonics.

K → RMS values of all the harmonics measured together gives the distortion.

the $\rightarrow \therefore$ Nonlinear distortion is called as harmonic distortion.

\rightarrow Harmonic distortion can be measured by the instrument called a distortion analyzer.

\rightarrow Total Harmonic Distortion (THD) is given by the formula $THD = \frac{\text{Total harmonic voltage}}{\text{Fundamental voltage}} \times 100\%$.

Ex - If $THV = 0.1 \text{ V rms}$ & $FV = 1 \text{ V}$ then $THD = 10\%$

\rightarrow Negative feedback reduces harmonic distortion equation for closed loop harmonic distortion is

$$THD_{CL} = \frac{THD_{OL}}{1 + A_{VOL} B}$$

where $THD_{OL} \rightarrow$ open loop harmonic distortion

$THD_{CL} \rightarrow$ closed loop "


\rightarrow As $1 + A_{VOL} B \gg 1$, so it reduces the harmonic distortion to negligible level.

\rightarrow In stereo amplifiers, we hear high-fidelity (HF) music instead of distorted sounds.

Discrete Negative feedback amplifier.

RK

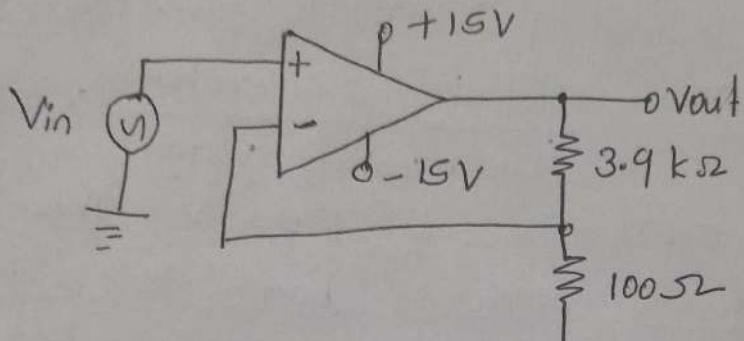Example - In fig the 741C has an R_{in} of $2M\Omega$ & R_{cm} of $200M\Omega$. What is the closed-loop input impedance? Use $A_{VOL} = 1,00,000$ for 741C.



$$B = \frac{R_f}{R_1 + R_f} = \frac{100}{100 + 3.9k} = 0.025$$

$$\therefore 1 + A_{VOL} B = 1 + 1,00,000 \times 0.025 = 2500$$

$$Z_{in(CL)} \approx (1 + A_{VOL} B) \cdot R_{in} = 2500 \times 2 \times 10^6$$

$$Z_{in(CL)} \approx 5000 M\Omega$$

When $Z_{in(CL)} \gg 100 M\Omega$, use the formula

$$Z_{in(CL)} = (1 + A_{VOL} B) \parallel R_{cm}$$

$$= 5000 \parallel 11 \text{ } 200 M\Omega$$

$$Z_{in(CL)} = 192 M\Omega$$

high $Z_{in(CL)}$ represents that VCVS approaches an ideal voltage amplifier.

* In fig change the $3.9 k\Omega$ resistor to $4.9 k\Omega$ & solve for $Z_{in(CL)}$

Example - with values $A_{VOL} = 1,00,000$, $R_f = 3.9 k\Omega$, $R_1 = 100 \Omega$, $R_{out} = 75 \Omega$ calculate the closed loop output impedance

$$B = \frac{R_f}{R_1 + R_f} = \frac{100}{100 + 3.9k} = 2500 \cdot 0.025$$

$$1 + A_{VOL} \cdot B = 1 + 1,00,000 \cdot 0.025 \approx 2500$$

$$Z_{out(CL)} = \frac{R_{out}}{(1 + A_{VOL} \cdot B)} = \frac{75}{2500} = 0.03 \Omega$$

Low output impedance means that a VCVS approaches an ideal voltage amplifier.

(11)

Example - Suppose the amplifier has an open-loop total harmonic distortion of 7.5 percent. What is the closed loop total harmonic distortion?

$$THD_{CL} = \frac{THD_{OL}}{1 + A_{VOL} B} = \frac{7.5\%}{2500} = 0.003\%$$


* Repeat the same problem with $3.9k\Omega$ resistor changed to $4.9k\Omega$.

* The IC vs amplifier

→ It is an almost perfect current-to-voltage converter because it has zero input impedance & zero output impedance.

Output voltage

→ Consider an IC vs amplifier.

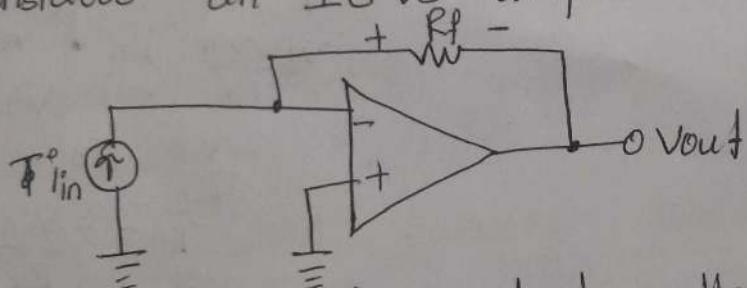

→ exact equation for output voltage is

$$V_{out} = -\left(I_{in} R_f \cdot \frac{A_{VOL}}{1 + A_{VOL}}\right)$$

as $A_{VOL} \gg 1$

$$V_{out} = -I_{in} R_f \frac{A_{VOL}}{A_{VOL}}$$

$$\boxed{V_{out} = -I_{in} R_f}$$

Non-inverting Input & Output Impedances

→ The exact equations for closed-loop input & output impedances are


$$\boxed{Z_{in(CL)} = \frac{R_f}{1 + A_{VOL}}}$$

$$\boxed{Z_{out(CL)} = \frac{R_f}{1 + A_{VOL}}}$$

RK

→ Large denominator will reduce the impedance to a very low value.

The inverting amplifier

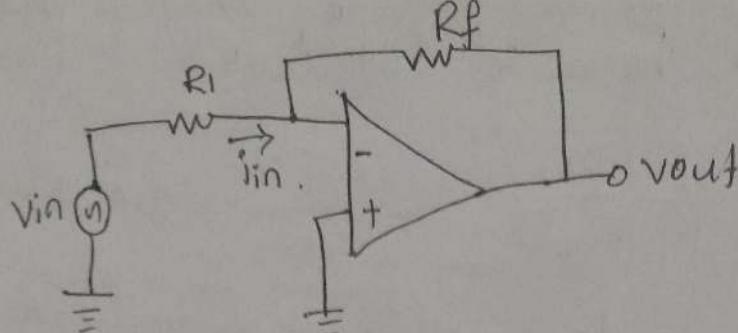


mple
c/

→ inverting amplifier has closed loop voltage gain

$$A_v = -\frac{R_f}{R_1}$$

→ It uses ICVS negative feedback. Because of the virtual ground on the inverting input, the input current equals

$$i_{in} = \frac{V_{in}}{R_1}$$

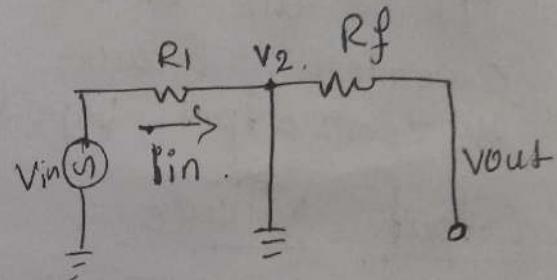


$$\frac{V_2 - V_{in}}{R_1} = i_{in} \Rightarrow V_2 = 0.$$

$$\frac{-V_{in}}{R_1} = i_{in}$$

$$i_{in} = -\frac{V_{in}}{R_1}$$

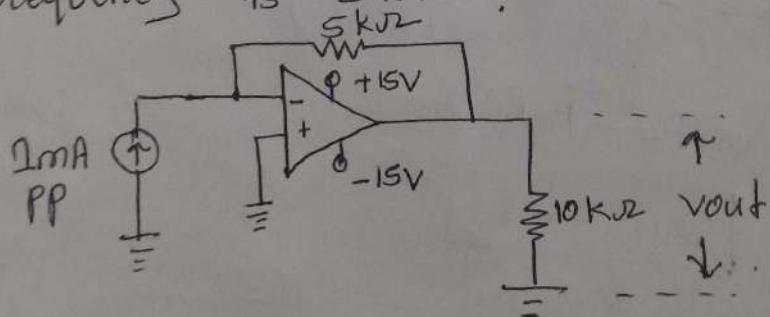Example - What is the output voltage if the input frequency is 9 kHz?



$$\begin{aligned} V_{out} &= -i_{in} R_f \\ &= -1\text{mA} (5\text{k}\Omega) \\ &= -5\text{V}_{pp}. \end{aligned}$$

RK

* Practice the same with $R_f = 2\text{k}\Omega$.

(13)

Example - For the above circuit what are the closed-loop input and output impedance? Use 741C parameters.

$$Z_{in(CCL)} = \frac{R_f}{1 + A_{VOL}} = \frac{5k\Omega}{1 + 100,000} \underset{\text{A}_{VOL} = 1,00,000}{=} \frac{5k\Omega}{1,00,000} = 0.05\Omega$$


$$Z_{out(CCL)} = \frac{R_{out}}{1 + A_{VOL}} = \frac{75}{1 + 1,00,000} \underset{\text{A}_{VOL} = 1,00,000}{=} \frac{75}{1,00,000} = 0.00075\Omega$$

* Repeat the example with $A_{VOL} = 200,000$.

The VCIS amplifier

- It converts an input voltage to a precise value of output current.
- Fig shows VCIS amplifier. It is same as VCVS except R_L & feedback resistor R_1 .
- Output is the current through R_L .
- Output current is stabilized, exact equation for i_{out} is
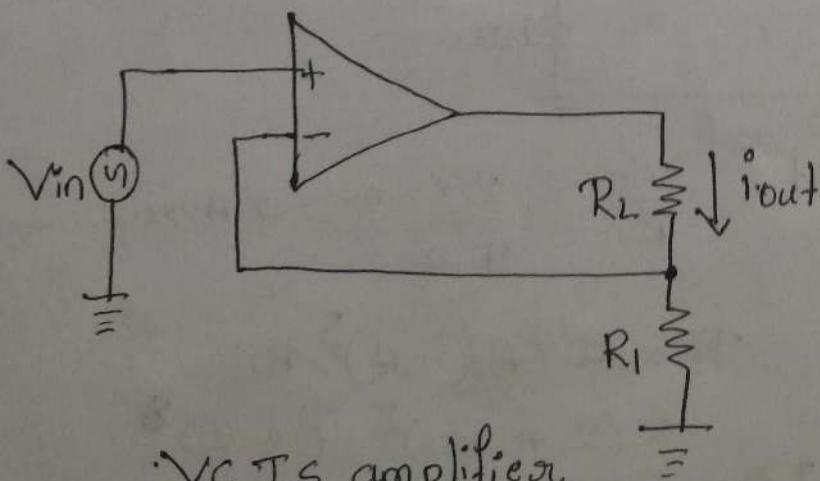
$$i_{out} = \frac{V_{in}}{R_1 + (R_1 + R_L)/A_{VOL}}$$



RK

VCIS amplifier.

→ In a practical circuit, $(R_1 + R_2) / A_{VOL} \ll R_1$

$$\therefore I_{out} = \frac{V_{in}}{R_1}$$

also written as $I_{out} = g_m V_{in}$ where $g_m = \frac{1}{R_1}$

→ As the output side of a VCTIS is same as input side of VCVS amplifier the closed loop input impedance is given by

$$Z_{in(CCL)} = (1 + A_{VOL} B) R_{in}$$


→ Output impedance is given by

$$Z_{out(CCL)} = (1 + A_{VOL}) R_1$$

→ The circuit is an almost perfect voltage to current converter because it has very high $Z_{in(CCL)}$ & $Z_{out(CCL)}$.

Example - What is the load current in fig? The load power? What happens if the load resistance changes to 4Ω ?

Load

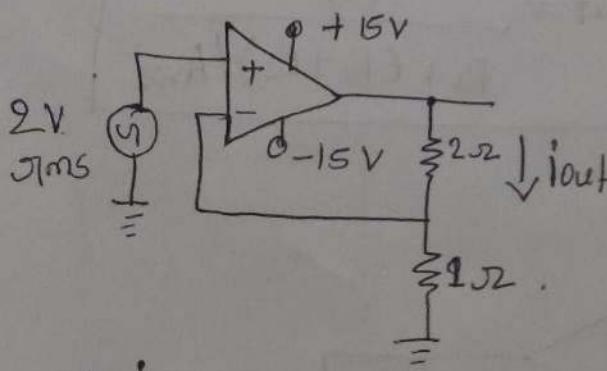

$$\text{Load Current } I_{out} = \frac{V_{in}}{R_1} = \frac{2V_{rms}}{1\Omega} = 2A_{rms}$$

RK

$$\begin{aligned} \text{Load Power } P_L &= I^2 R (I_{out})^2 R_L \\ &= (2 A_{rms})^2 (2\Omega) \end{aligned}$$

→ If load resistances changes to $4\ \Omega$


$$P_L = (i_{out})^2 R_L \\ = (2)^2 4.$$

$$P_L = 16\text{W}$$

* Practice the problem by changing the input voltage to 3V_{rms} & solve for i_{out} & P_L .

The ICIS amplifier

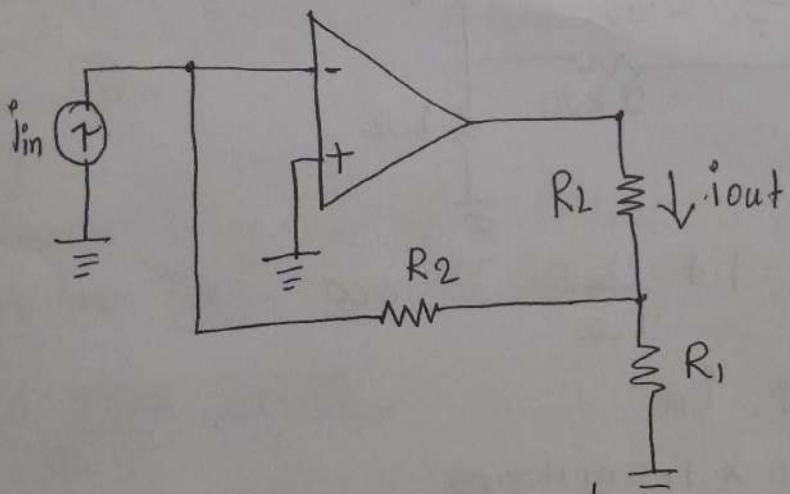- It act as a perfect current amplifier.
- It has heavy negative feedback.
- It has low input impedance ($Z_{in(\text{CL})}$) & a very high output impedance $Z_{out(\text{CL})}$.
- Fig shows ICIS amplifier.



→ The closed-loop current gain is stabilized & given by

$$A_i = \frac{A_{VOL} (R_1 + R_2)}{R_L + A_{VOL} R_1}$$

→ usually $A_{VOL} R_1 \gg R_L$

$$\therefore A_i = \frac{A_{VOL} (R_1 + R_2)}{A_{VOL} R_1} = \frac{R_1}{R_1} + \frac{R_2}{R_1}$$

$$A_i = 1 + \frac{R_2}{R_1}$$


$$Z_{in(CCL)} = \frac{R_2}{1 + A_{VOL} B}$$

feedback fraction $B = \frac{R_1}{R_1 + R_2}$

$$Z_{out(CCL)} = (1 + A_{VOL}) R_1$$

→ Large A_{VOL} produces small Z_{in} & large Z_{out} so it acts as a perfect current amplifier.

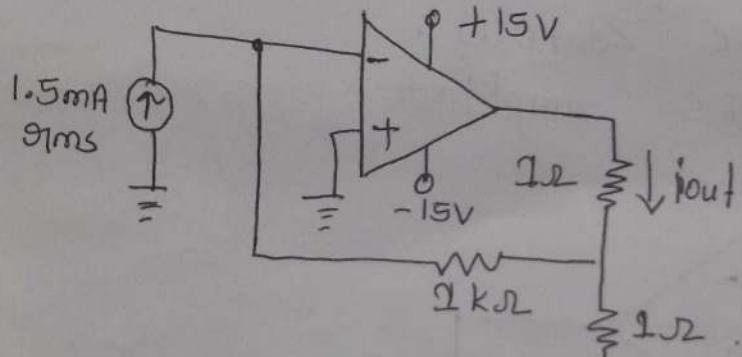Example - What is the load current in fig? the load power? If the load resistance is changed to $2\text{ }\Omega$. what are the load current & power?



$$A_i = 1 + \frac{R_2}{R_1} = 1 + \frac{1\text{ k}\Omega}{2\text{ }\Omega} \approx 1000$$

$$\begin{aligned} i_{out} &= A_i \cdot i_{in} \\ &= 1000 \times 1.5 \text{ mA rms} \\ i_{out} &= 1.5 \text{ A rms} \end{aligned}$$

$$\begin{aligned} \text{Load Power } P_L &= \frac{i_{out}^2 R_L}{(2\text{ }\Omega)} \\ P_L &= 2.25 \text{ W} \end{aligned}$$

For $R_L = 2\text{ }\Omega$.

$$i_{out} = 1.5 \text{ A}$$

$$\begin{aligned} P_L &= (i_{out})^2 R_L \\ &= (1.5 \text{ mA})^2 2\text{ }\Omega \\ P_L &= 4.5 \text{ mW} \end{aligned}$$

Practice - Using above fig
change i_{in} to 200A
calculate i_{out} & P_L .

Active Filters

- A filter is an electronic circuit that passes one band of frequencies while rejecting other.
- 2 types - Active filter, Passive filter.
- Passive filter.
- Built with $R, L \& C$
- Used above 1 MHz
- Do not have power gain.
- Difficult to tune
- Built with R, C & op-amp.
- Useful below 1 MHz
- Have power gain.
- Easy to tune.

Active filters


Ideal Responses

There are five types of filters.

1. Low-pass filter
2. High-pass "
3. Band- "
4. Bandstop "
5. All pass "

Note - Frequency response of a filter is the graph of its voltage gain versus frequency.

1. Low Pass Filter.

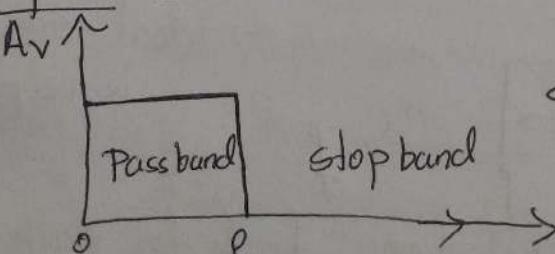

↳ ideal lowpass filter.

- the filter that passes lower frequencies & stops higher frequency is called low pass filter.
- It passes all the frequencies from zero to the cut off frequency 'fc' called pass band.
- Blocks all frequencies above f_c called stop band.


RK

→ An ideal low-pass filter has zero attenuation (signal loss) in pass band. Infinite attenuation in the stopband & vertical attenuation.

2. High-pass filter

→ A filter that passes the frequency above f_1 and stops the signal frequency below f_1 is called high-pass filter.

Av ↑

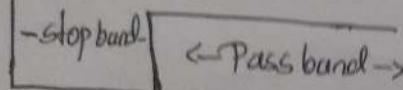

ideal high-pass response

→ blocks all frequencies from zero to f_c


→ Passes " from zero to f_c called stop band

→ ideal HPF has infinite attenuation in stop band & zero attenuation in pass band

3. Band pass Filter

A filter that passes all the frequencies between the lower & upper cutoff frequencies is called Band pass filter.

Av ↑

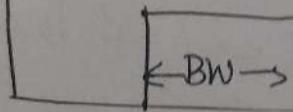

ideal response of bandpass

→ Passes frequencies between f_1 & f_2 called pass band.

→ Blocks frequencies below f_1 (lower cut off) & above f_2 (higher cut off) are called stop band.

$$\text{Band width} = f_2 - f_1$$

→ An ideal band pass filter has zero attenuation in pass band, infinite attenuation in the stopband & two vertical transition.

$$|P_L| = 4.5W$$

→ Center frequency $f_0 = \sqrt{f_1 f_2}$

$$\Omega = \frac{f_0}{BW}$$


$$\text{If } Q > 10 \quad f_0 \approx \frac{f_1 + f_2}{2}$$

→ If $Q < 1$, band pass filter is called wide band filter

→ If $Q > 1$, " " " " " Narrow "

Band stop filter

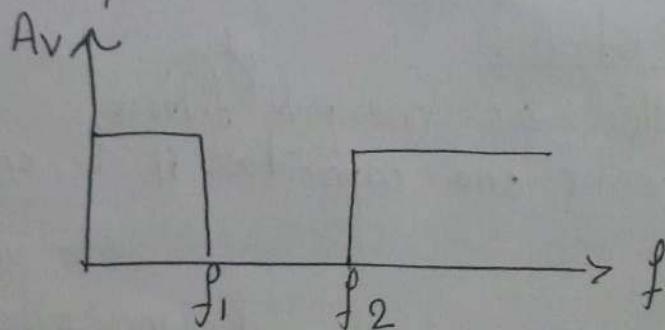→ A filter that passes all frequencies from zero up to lower cutoff frequency & above upper cutoff frequency is called band stop filter.



Ideal response of BSF

- 0 to f_1 & above f_2 is the pass band
- f_1 to f_2 is the stop band
- Ideal band stop filter has infinite attenuation in the stop band, no attenuation in the pass band by two, vertical transition.

$$BW = f_2 - f_1$$

$$f_0 = \sqrt{f_1 f_2}$$

RK

$$Q = \frac{f_0}{BW}$$

→ It is sometimes called as notch filter because it notches out (removes) all frequencies in the stopband.


All-Pass Filter

→ A filter that passes all the frequency is called All pass filter.

→ It has passband and no stopband.

→ It passes all frequencies between zero & infinity.

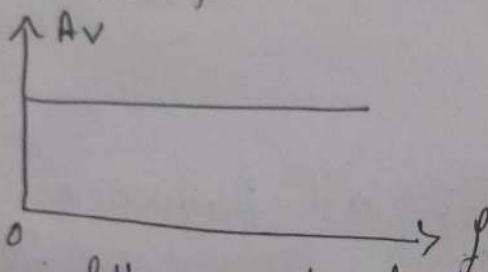→ Since it has zero attenuation for all frequencies it is called as filter.



→ In all pass filter, each frequency can be shifted by a certain amount as it passes through the filter.

First Order Stages

→ It is also called as one-pole ^{active} filter.

→ Stages have only one capacitor if it is called as 1st order.

Low-pass stages

→ Below are 3 ways to implement low pass stages.

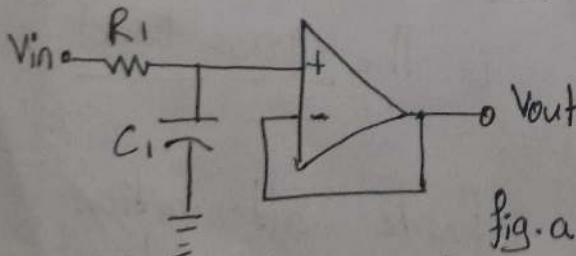


fig.a

$$Av = 1$$

$$f_c = \frac{1}{2\pi R_1 C_1} \quad (3\text{-dB cutoff frequency})$$

Non inverting unity gain 1st order low pass filter


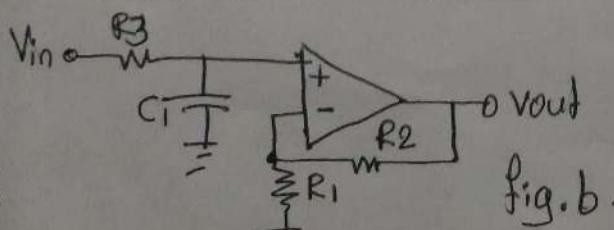


fig.b

$$Av = \frac{R_2}{R_1} + 1$$

$$f_c = \frac{1}{2\pi R_1 C_1}$$

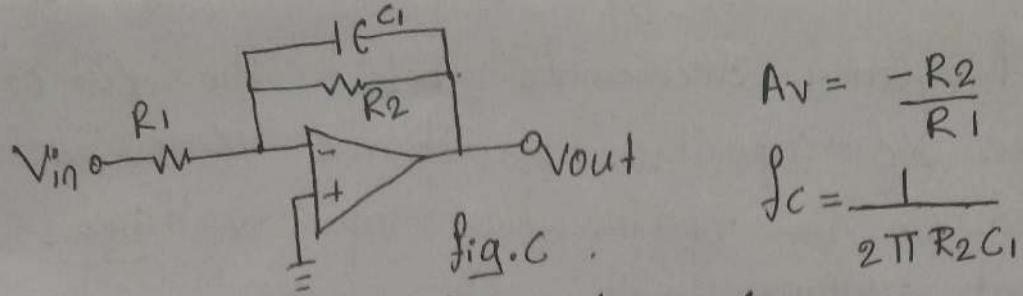Non-inverting with voltage gain 1st order LPF



$$A_v = -\frac{R_2}{R_1}$$


$$f_c = \frac{1}{2\pi R_2 C_1}$$

~~Non Inverting with voltage gain~~
1st order LPF.

→ In fig.a as the frequency increases above cut off frequency f_c , $X_C \downarrow$ decreases & reduces the non inverting input voltage.

→ So output is roll off after f_c .

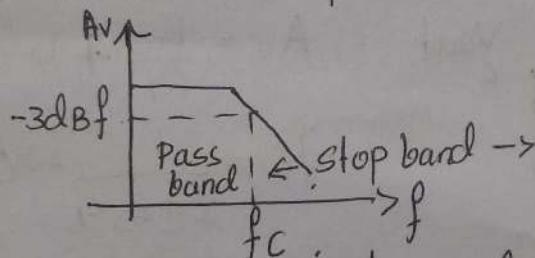
→ As frequency reaches ' ∞ ' capacitor becomes short & there is zero input voltage & zero output voltage.




→ Fig.b shows non inverting first order low pass filter.
→ It produces an voltage gain

$$A_v = \frac{R_2}{R_1} + 1$$

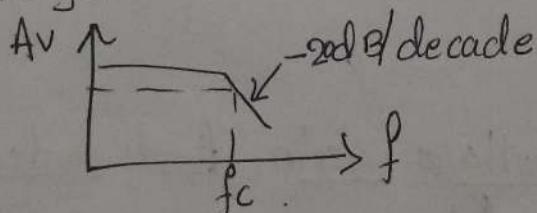→ $R_3 C_1$ lag circuit is outside the feedback loop, the output voltage rolls off at a rate of 20 dB per decade



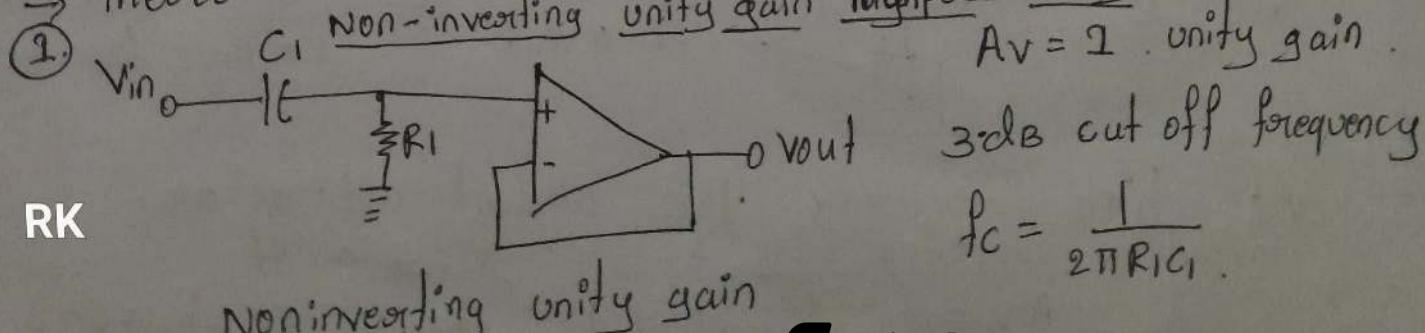High pass stage
Theore are 3 ways to implement high pass stages




$$A_v = 1 \text{ unity gain}$$

3-dB cut off frequency

$$f_c = \frac{1}{2\pi R_1 C_1}$$


RK

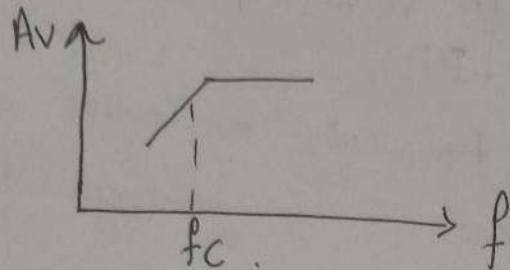→ when frequency decreases below the cut off frequency. $X_C \rightarrow$ capacitive reactance increases and reduces the non inverting input voltage. So output voltage rolls off.



→ As the frequency approaches zero, capacitor becomes open & there is zero input voltage.

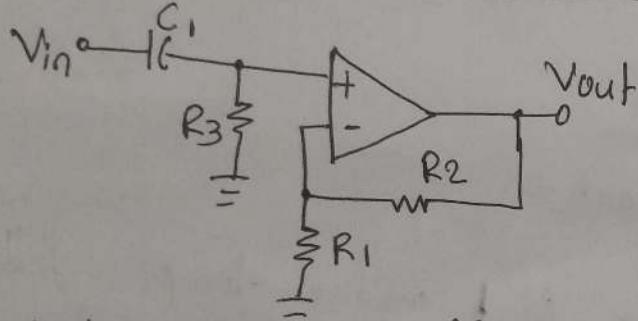
② Non-inverting with voltage gain - high-pass stage.




$$A_v = \frac{R_2}{R_1} + 1 \text{ Gain}$$

$$f_c = \frac{1}{2\pi R_3 C_1} \text{ 3dB cut off frequency.}$$

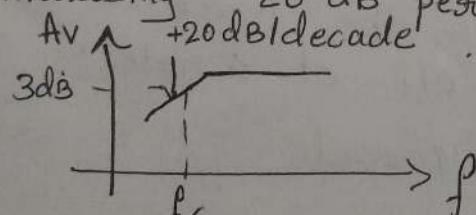→ below the cut off frequency f_c , circuit reduces the non inverting input voltage. So output voltage starts increasing 20 dB per decade.



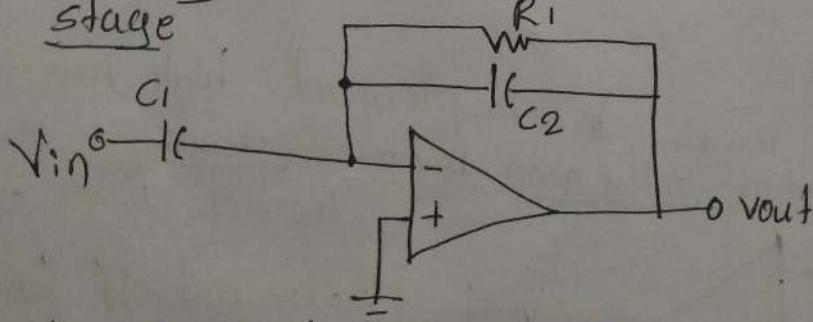③ Inverting stage with voltage gain first order high pass



$$A_v = -\frac{C_1}{C_2} \text{ gain}$$

$$f_c = \frac{1}{2\pi R_1 C_2} \text{ 3dB cut off frequency.}$$

→ At high frequency the circuit acts as an inverting amplifier with a voltage gain of

RK

$$A_v = -\frac{X_C 2}{X_C 1} = -\frac{C_1}{C_2}$$


$$\cancel{X_C 1} = \frac{1}{X_C 1} = C_1 \quad \frac{1}{X_C 2} = C_2$$

- As the frequency decreases, X_C & ω reduces the input signal & the feed back.
- Voltage gain also reduces.
- As the frequency approaches zero, the capacitor becomes open and there is no input signal.

VCVS Unity-Gain Second-Order Low-Pass Filters (LPF)

- It is a second order or 2-pole filter.
- called as Sallen-Key LPF (named after inventors).
- called as VCVS filters because the op-amp is used as a voltage controlled voltage source.
- VCVS LPF circuit can implement 3 basic approximation: Butterworth, Chebyshev, and Bessel.

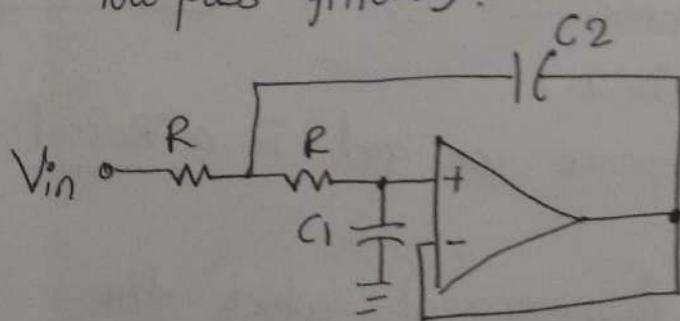Second-order VCVS stage for Butterworth and Bessel (Sallen-Key Second-order low pass filter).



$$\text{unity gain} \rightarrow A_V = 1$$

$$Q\text{-factor} \rightarrow Q = 0.5 \sqrt{\frac{C_2}{C_1}}$$

$$\text{Butterworth} \quad f_p = \frac{1}{2\pi R \sqrt{C_1 C_2}}$$

Butterworth

$$Q = 0.707$$

$$K_C = 2$$

Bessel

$$Q = 0.577$$

$$K_C = 0.786$$

- In the circuit two resistors have same value. But the two capacitors have different value.
- Lag circuit is connected to non-inverting terminal (output) is connected through capacitor C_2 .

- When frequency is low both capacitors appear as open circuit.
- Circuit is connected as a voltage follower $\therefore A_{VZ}$
- As when frequency increases, impedance of C_1 decreases & the noninverting input voltage decreases.
- As C_2 is connected in the feedback provides the signal to the noninverting input which is inphase. So feedback signal adds the source signal, feedback is positive.
- $C_2 > C_1$ to get positive feedback. It increases ' Q '.

Pole frequency - A special frequency used in the design of active filters is called Pole frequency (f_p)

Pole frequency is given by $f_p = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}}$

as $R_1 = R_2 = R$.

$$f_p = \frac{1}{2\pi R\sqrt{C_1 C_2}}$$

If $Q = 0.707$, the response we get is a butterworth response and k_c value is 1.

If $Q = 0.577$, the response we get is a Bessel response & $k_c = 0.786$.


→ cut off frequency - A frequency at which the attenuation is 3dB is given by

$$f_c = k_c f_p$$

Second order VCVS stage for $Q > 0.707$.
(Peaked response).

→ Fig analyze the circuit when $Q > 0.707$.

RK

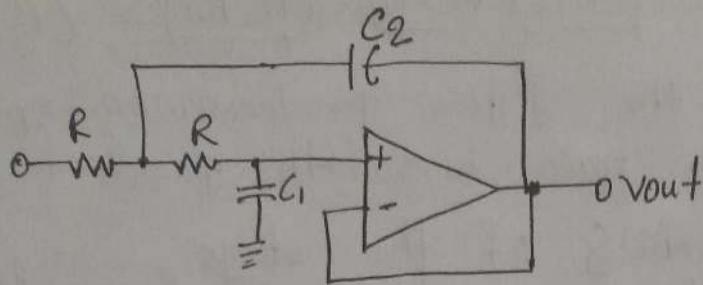

→ Resonant frequency where
Peaking appears

$$f_0 = k_0 f_p$$

→ Edge frequency

$$f_c = k_c f_p$$

→ 3dB frequency

$$f_{3dB} = k_3 f_p$$

$$A_v = 1$$

$$Q = 0.5 \sqrt{\frac{C_2}{C_1}}$$

$$f_p = \frac{1}{2\pi R \sqrt{C_1 C_2}}$$

$$Q > 0.707$$

$$f_0 = k_0 f_p$$

$$f_c = k_c f_p$$

$$f_{3dB} = k_3 f_p$$

$$\rightarrow \text{For } Q > 10$$

$$k_0 = 1$$

$$k_c = 1.414$$


$$k_3 = 1.55$$

$$A_p = 20 \log Q$$

RK

- \Rightarrow Gain-Bandwidth Product of op Amps (G_{BW})
- Not to affect the filter performance op-amps must have enough gain-bandwidth product (G_{BW}).
 - Limited G_{BW} (inherent) of the stage
 - " " change performance of a filter.
 - Using Padé approximation method limited G_{BW} can be corrected.

V_C vs Equal-Component Low-pass Filters

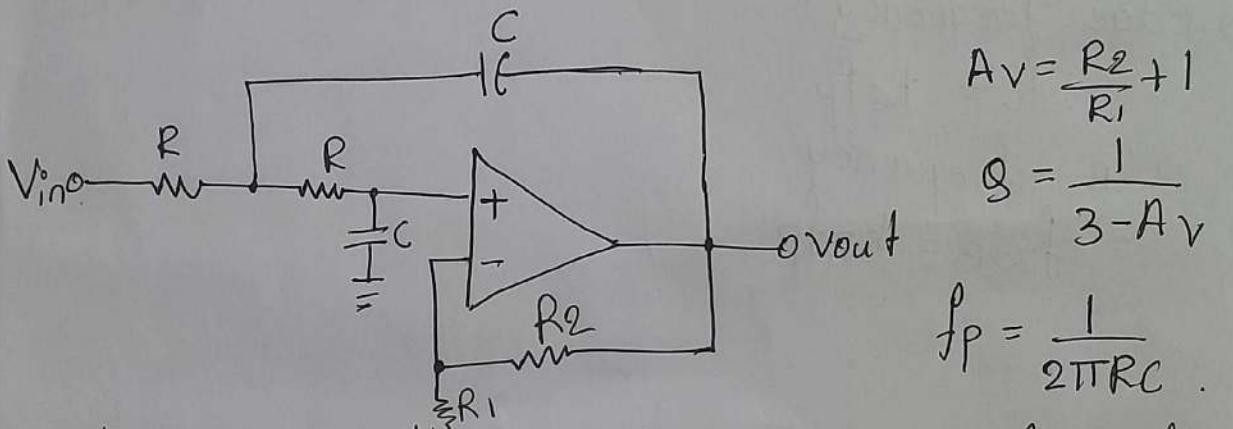

$$A_v = \frac{R_2}{R_1} + 1$$

$$Q = \frac{1}{3 - A_v}$$


$$f_p = \frac{1}{2\pi R C}$$

- It is another Sallen-Key second order low-pass filter.
- It uses same values of 'R' & same values of 'C'.
- This is why the circuit called a Sallen-Key equal component filter.
- Voltage gain of the circuit is $A_v = \frac{R_2}{R_1} + 1$.
- Q of the circuit is $Q = \frac{1}{3 - A_v}$.
- Condition is A_v can be no smaller than unity (1 to 3) & minimum Q is 0.5 V.
- When $A_v > 3$, positive feedback becomes too large and it breaks in to oscillation. When A_v approaches 3 component tolerance & drift causes A_v to exceed 3.

VCVS High-Pass filters

There are two configuration.

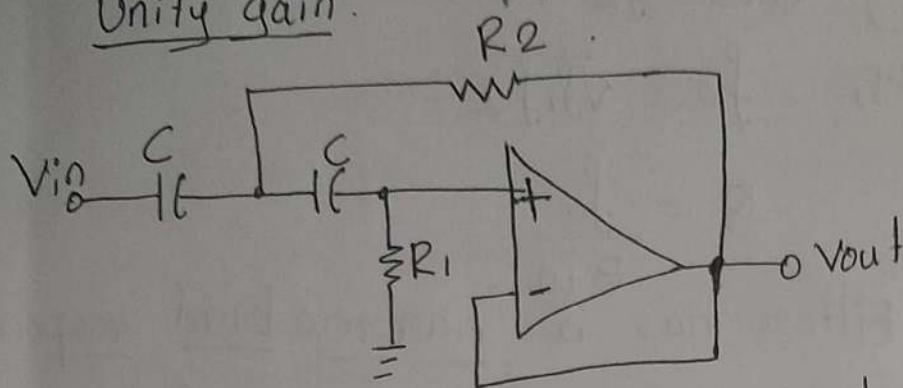- ① Second order VCVS high-pass filter stages - Unity gain.



$$A_V = 1$$

$$Q = 0.5 \sqrt{\frac{R_1}{R_2}}$$

$$f_p = \frac{1}{2\pi C \sqrt{R_1 R_2}}$$

→ Fig shows the sallen-key unity gain high pass filter and its equation.


→ Here position of R & C are reversed.

→ Q depends on value of R .

→ cut off frequency of a high pass filter

$$f_c = \frac{f_p}{K_c}$$

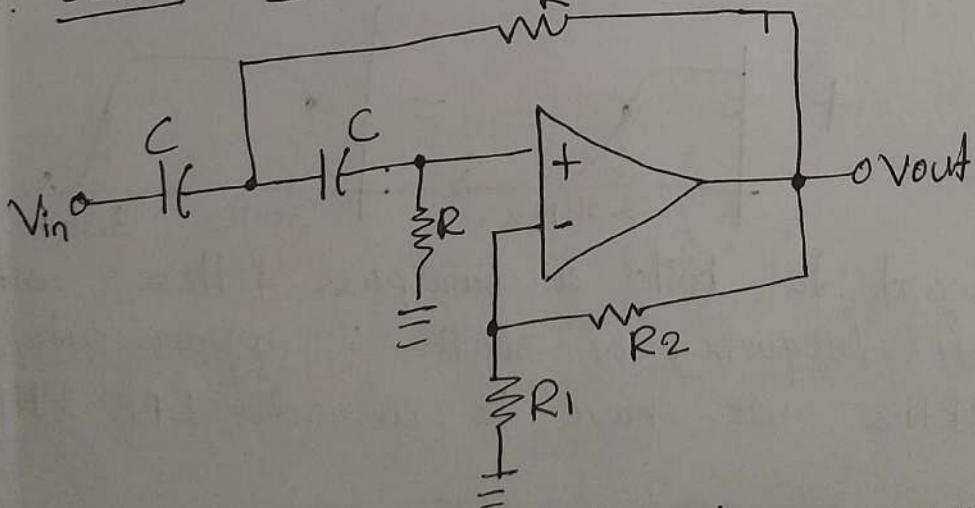- ② Second order VCVS high-pass stages - voltage gain



$$A_V = \frac{R_2}{R_1} + 1$$

$$Q = \frac{1}{3 - A_V}$$

$$f_p = \frac{1}{2\pi R C}$$

→ Fig shows the sallen-key equal component high pass filter and its equation.

RK

BFB Bandpass Filters

→ A bandpass filter has a center frequency & a bandwidth.

$$\text{Band width, } BW = f_2 - f_1$$

$$\text{center frequency, } f_0 = \sqrt{f_1 f_2}$$


$$Q = \frac{f_0}{BW}$$

When $Q > 1$ Filter has a narrow band response
 " $Q < 1$ " " Wide band response

Wide Band Filters

→ When $Q < 1$ Filter has a wide band response

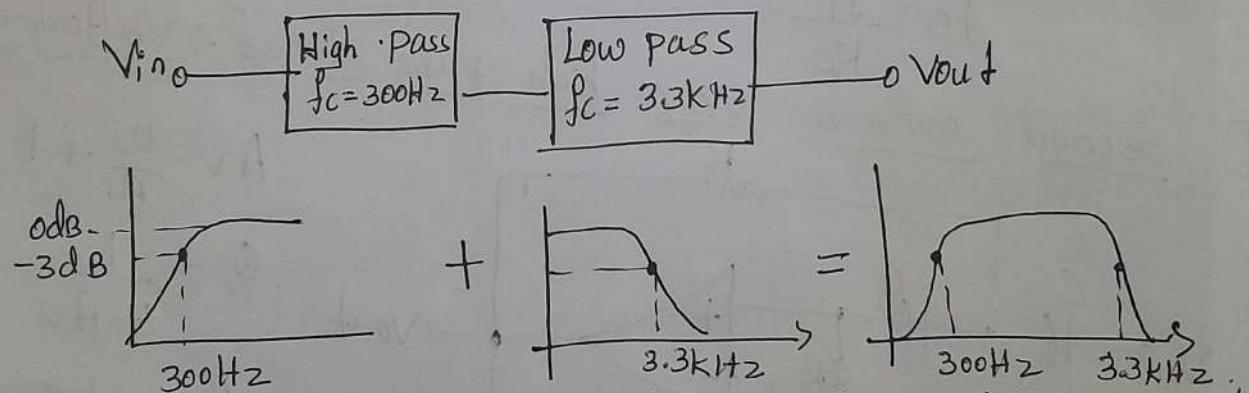→ we can construct wide band filter by cascading low-pass & high pass stages.



→ suppose we want to build a bandpass filter with a lower cutoff frequency of 300Hz & upper cutoff frequency 3.3kHz. we have to cascade LPF & HPF as above.

$$f_0 = \sqrt{f_1 f_2} = \sqrt{300\text{Hz} \cdot 3.3\text{kHz}} = 995\text{Hz}$$

$$BW = f_2 - f_1 = 3.3\text{kHz} - 300\text{Hz} = 3\text{kHz}$$

$$Q = \frac{f_0}{BW} = \frac{995}{3\text{kHz}} = 0.332$$


RK

Q is less than 1.

→ HPF has a cut $f_c = 300\text{Hz}$.
 → LPF " " $f_c = 3.3\text{kHz}$.

→ When we add the responses we get bandpass filter with cutoff frequencies of 300Hz & 3.3kHz .

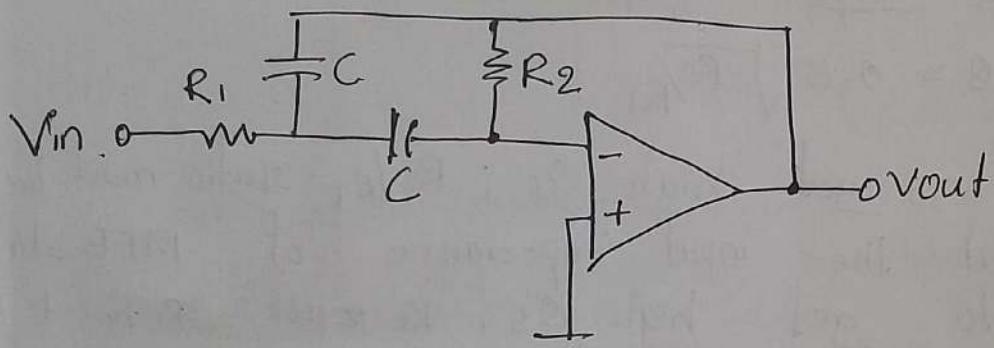Narrow band Filters [Multiple feedback (MFB)].
 → When $Q > 1$, multiple - feedback filter is used.



$$A_v = \frac{-R_2}{2R_1}$$

$$Q = 0.5 \sqrt{\frac{R_2}{R_1}}$$

$$f_0 = \frac{1}{2\pi C \sqrt{R_1 R_2}}$$

- V_{in} is given to the inverting terminal.
- Circuit has two feedback path one through 'C' & another through ' R_2 '
- At lower frequencies (when f is low) capacitor act as open switch. Therefore input signal cannot reach the opamp and the output is zero.
- At high frequency (when f is high) capacitor act as a closed switch. so voltage gain is zero as capacitor has zero impedance.
- Between extremes low and high frequency, there is a band of frequencies where the circuit acts like an inverting amplifier. voltage gain at the center frequency is given by $A_v = \frac{-R_2}{2R_1}$.

Q of the circuit is given by

$$Q = 0.5 \sqrt{\frac{R_2}{R_1}}$$

$$\Omega = 0.707 \star \sqrt{-A_v}$$

If $A_v = -100$.

$$Q = 0.707 \sqrt{100} = 7.07.$$

→ Greater the voltage gain higher the Q.


$$f_0 = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$
 Since $C_1 = C_2$.

$$f_0 = \frac{1}{2\pi C \sqrt{R_1 R_2}}$$


Increasing the input Impedance

We have $Q = 0.5 \sqrt{R_2/R_1}$

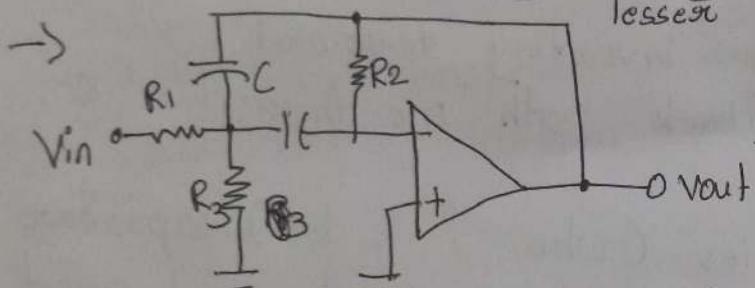→ $Q \propto R_2/R_1$, To get high Qs; R_2/R_1 ratio must be kept high. But the input impedance of MFB stage is too low to get high Qs. $R_2 = 100k\Omega$, R_1 has to be lesser than $1k\Omega$



Increasing input impedance of MFB stage

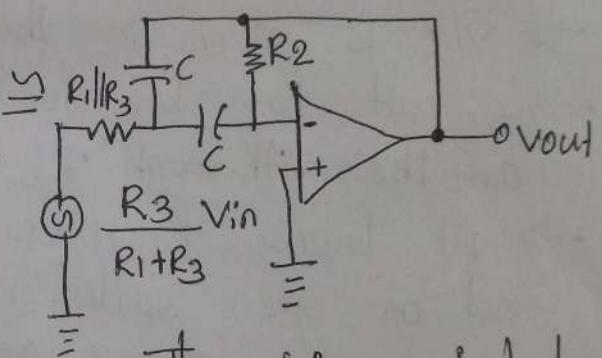

Thevenin's equivalent circuit

→ Fig shows an MFB bandpass filter that increases the input impedance. Extra resistor R_3 is used to divide the voltage.

Voltage gain $A_v = -\frac{R_2}{2R_1}$

Q factor


$$Q = 0.5 \sqrt{\frac{R_2}{R_1 || R_3}}$$

$$f_0 = \frac{1}{2\pi C \sqrt{(R_1 || R_3) R_2}}$$

RK

Tunable center Frequency with constant Bandwidth

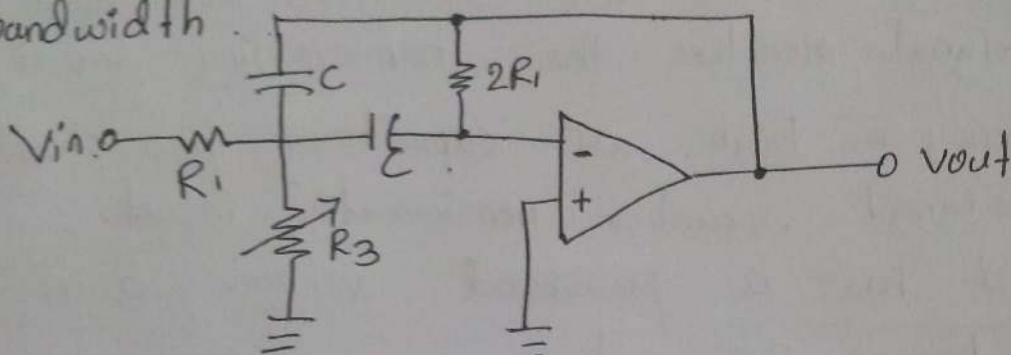→ Fig shows the modified circuit that has $A_v = 1$ & it has a variable center frequency and constant bandwidth.



→ In the above circuit, $R_2 = 2R_1$ & R_3 is variable. The circuit has following equations.

$$A_v = -1$$

$$Q = 0.707 \sqrt{\frac{R_1 + R_3}{R_3}}$$

$$f_0 = \frac{1}{2\pi C \sqrt{2R_1 (R_1 + R_3)}}$$


f_0 depends on R_3
 R_3 changes center frequency
 f_0 changes.

Since $BW = \frac{f_0}{Q}$

$$BW = \frac{1}{2\pi R_1 C} \quad BW \text{ does not depend on } R_3$$

∴ even though R_3 changes BW remains constant.

Bandstop filters : R/2

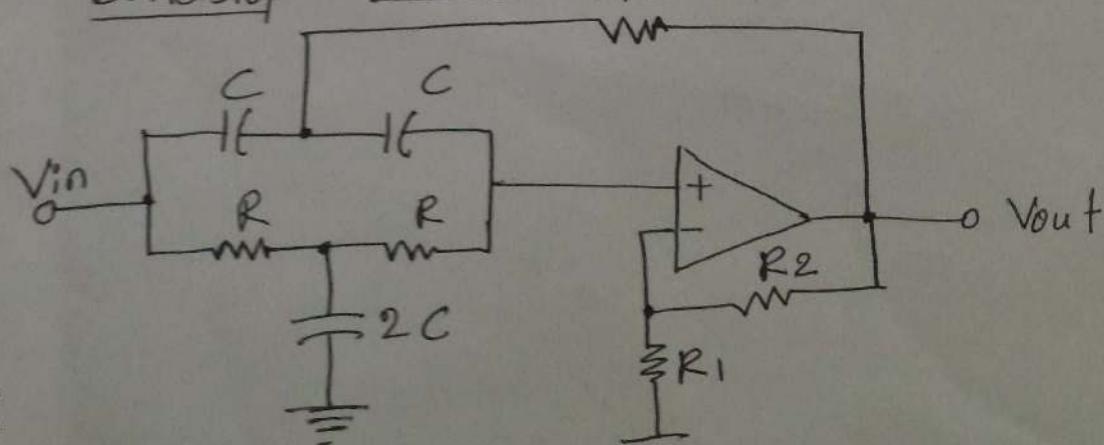

Sallen - key second - order notch filter

→ Fig shows a Sallen-Key second order notch filter & its equations.

→ Bandstop filter block only a single frequency (notch filter)

→ When frequency is low all capacitors are open, all input signal reaches the non inverting input.

→ When frequency is high, all capacitors are shorted, all input signal reaches non inverting input.

→ The circuit has a passband voltage gain

$$Av = \frac{R_2}{R_1} + 1$$

→ Center frequency (f_0) is between extreme low & high frequency.

$$f_0 = \frac{1}{2\pi RC}$$

→ At f_0 feedback signal returns with the correct amplitude and phase to attenuate the signal on the non-inverting input.

→ The Q of the circuit

$$Q = \frac{0.5}{2 - Av}$$

→ $Av < 2$ to avoid oscillations. & Q must be less than 10

First Order Stages


33

Example 19-1


What is the voltage gain in Fig. 19-23a? What is the cutoff frequency? What is the frequency response?

Figure 19-23 Example.


(1)

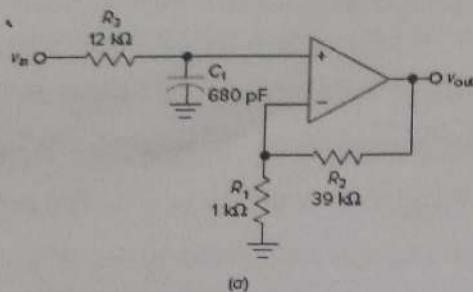


(a)

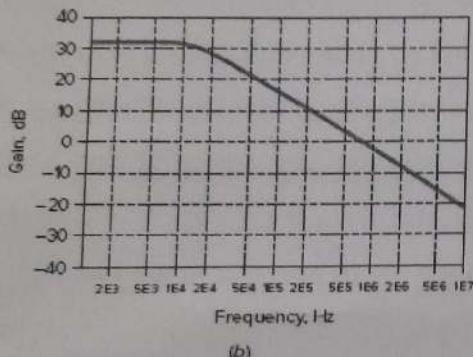

(b)

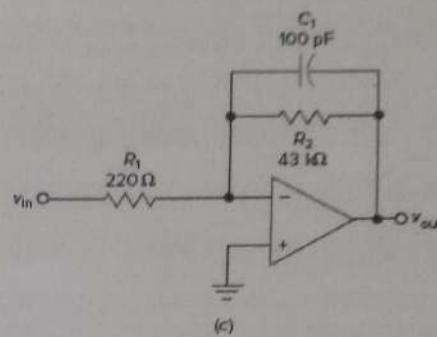

(c)

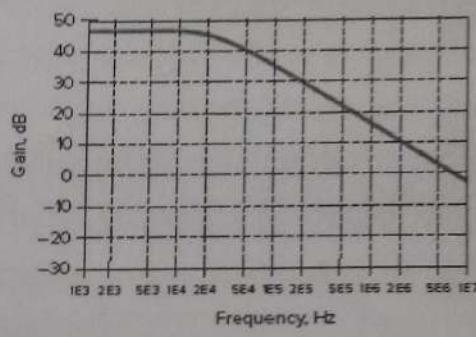

(d)

SOLUTION This is a noninverting first-order low-pass filter. With Eqs. (19-10) and (19-11), the voltage gain and cutoff frequencies are:

$$Av = \frac{39 \text{ k}\Omega}{1 \text{ k}\Omega} + 1 = 40$$

$$\left[1 + R_f/R_1\right]$$

$$f_c = \frac{1}{2\pi(12 \text{ k}\Omega)(680 \text{ pF})} = 19.5 \text{ kHz}$$

$$\frac{1}{2\pi R_2 C_1}$$

Figure 19-23b shows the frequency response. The voltage gain is 32 dB in the passband. The response breaks at 19.5 kHz and then rolls off at a rate of 20 dB per decade.

PRACTICE PROBLEM 19-1 Using Fig. 19-23a, change the 12-kΩ resistor to 6.8 kΩ. Find the new cutoff frequency.

(2)

Example 19-2

What is the voltage gain in Fig. 19-23c? What is the cutoff frequency? What is the frequency response?

SOLUTION This is an inverting first-order low-pass filter. With Eqs. (19-12) and (19-13), the voltage gain and cutoff frequencies are:

$$Av = \frac{-43 \text{ k}\Omega}{220 \Omega} = -195$$

$$-\frac{R_f}{R_1}$$

$$f_c = \frac{1}{2\pi(43 \text{ k}\Omega)(100 \text{ pF})} = 37 \text{ kHz}$$

$$\frac{1}{2\pi R_2 C_1}$$

Figure 19-23d shows the frequency response. The voltage gain is 45.8 dB in the passband. The response breaks at 37 kHz and then rolls off at a rate of 20 dB per decade.

RK PRACTICE PROBLEM 19-2 In Fig. 19-23c, change the 100-pF capacitor to 220 pF. What is the new cutoff frequency?


Second order stages

Application Example 19-3


III Multisim

What are the pole frequency and Q of the filter shown in Fig. 19-27? What is the cutoff frequency? Show the frequency response using a Multisim Bode plotter.

Figure 19-27 (a) Butterworth unity-gain example; (b) Multisim frequency response.

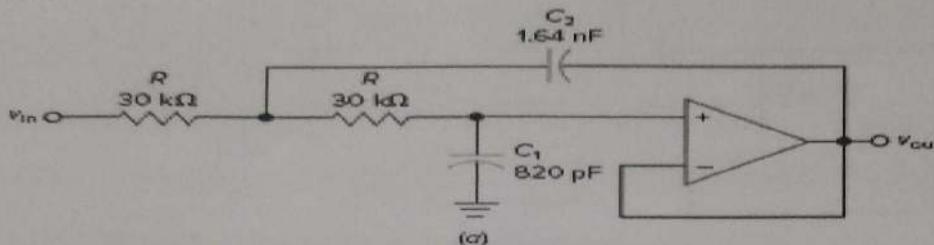

(a)

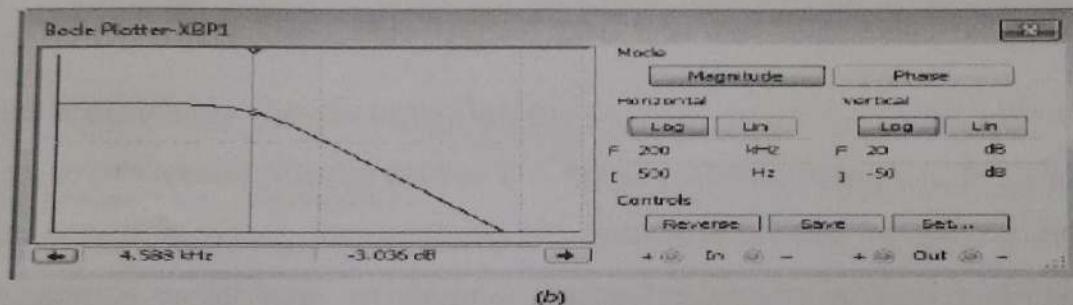

(b)

Courtesy of National Instruments.

SOLUTION The Q and pole frequency are:

$$Q = 0.5\sqrt{\frac{C_2}{C_1}} = 0.5\sqrt{\frac{1.64 \text{ nF}}{820 \text{ pF}}} = 0.707$$

$$f_p = \frac{1}{2\pi R \sqrt{C_1 C_2}} = \frac{1}{2\pi(30 \text{ k}\Omega)\sqrt{(820 \text{ pF})(1.64 \text{ nF})}} = 4.58 \text{ kHz}$$

The Q value of 0.707 tells us that this is a Butterworth response, so the cutoff frequency is the same as the pole frequency:

$$f_c = f_p = 4.58 \text{ kHz} \quad f_c = k_C f_p$$

The response of the filter breaks at 4.58 kHz and rolls off at a rate of 40 dB per decade because $n = 2$. Figure 19-27b shows the Multisim frequency response plot.

PRACTICE PROBLEM 19-3 Repeat Application Example 19-3 with the resistor values changed to 10 kΩ.


RK

Second order LPF .

Example 19-4

In Fig. 19-28, what are the pole frequency and Q ? What is the cutoff frequency?

Figure 19-28 Bessel unity-gain example.

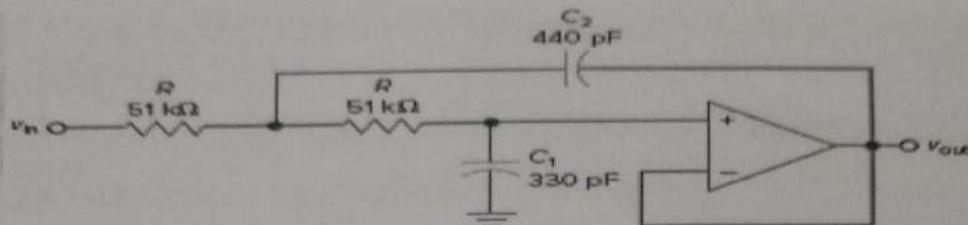

SOLUTION The Q and pole frequency are:

$$Q = 0.5\sqrt{\frac{C_2}{C_1}} = 0.5\sqrt{\frac{440 \text{ pF}}{330 \text{ pF}}} = 0.577$$

$$f_p = \frac{1}{2\pi R\sqrt{C_1 C_2}} = \frac{1}{2\pi(51 \text{ k}\Omega)\sqrt{(330 \text{ pF})(440 \text{ pF})}} = 8.19 \text{ kHz}$$

The Q value of 0.577 tells us that this is a Bessel response. With Eq. (19-21), the cutoff frequency is given by:


$$f_c = K_c f_p = 0.786(8.19 \text{ kHz}) = 6.44 \text{ kHz}$$

PRACTICE PROBLEM 19-4 In Example 19-4, if the value of C_1 changed to 680 pF, what value should C_2 be to maintain a Q of 0.577?

Example 19-5

What are the pole frequency and Q in Fig. 19-29? What are the cutoff and 3-dB frequencies?

Figure 19-29 Unity-gain example with $Q > 0.707$.

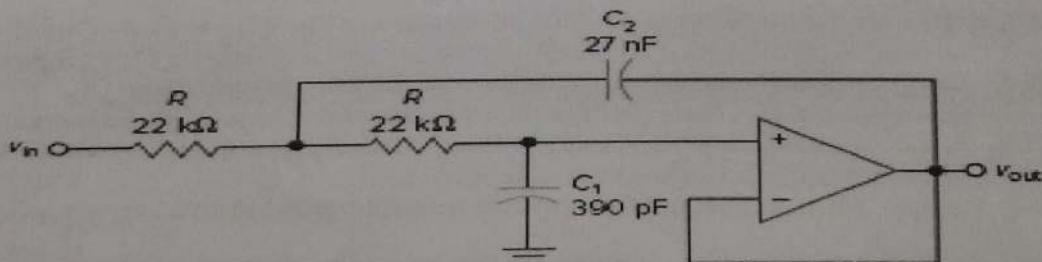

SOLUTION The Q and pole frequency are:

$$Q = 0.5\sqrt{\frac{C_2}{C_1}} = 0.5\sqrt{\frac{27 \text{ nF}}{390 \text{ pF}}} = 4.16$$

$$f_p = \frac{1}{2\pi R\sqrt{C_1 C_2}} = \frac{1}{2\pi(22 \text{ k}\Omega)\sqrt{(390 \text{ pF})(27 \text{ nF})}} = 2.23 \text{ kHz}$$

Referring to Fig. 19-26, we can read the following approximate K and A_p values:

$$K_0 = 0.99 //$$

$$K_c = 1.38 //$$

$$K_3 = 1.54 //$$

$$A_p = 12.5 \text{ dB}$$

The cutoff or edge frequency is:

$$f_c = K_c f_p = 1.38(2.23 \text{ kHz}) = 3.08 \text{ kHz}$$

and the 3-dB frequency is:

$$f_{3\text{dB}} = K_3 f_p = 1.54(2.23 \text{ kHz}) = 3.43 \text{ kHz}$$


RK

PRACTICE PROBLEM 19-5 In Fig. 19-29, change the 27-nF capacitor to 14 nF and repeat Example 19-5.


Application Example 19-6

What are the pole frequency and Q of the filter shown in Fig. 19-32? What is the cutoff frequency? Show the frequency response using a Multisim Bode plotter.

Figure 19-32 (a) Butterworth equal-component example. (b) Multisim pole frequency.

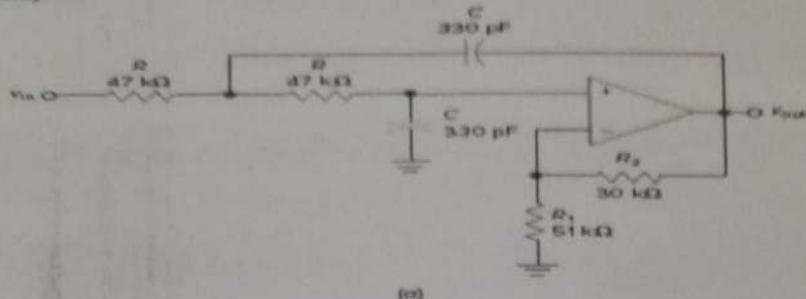

(a)

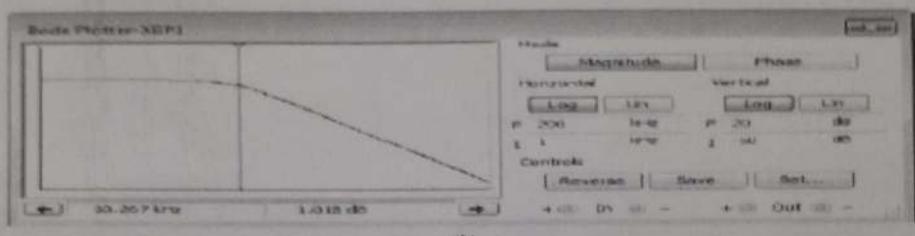

(b)

Courtesy of National Instruments.

SOLUTION The A_V , Q , and f_p are:

$$A_V = \frac{30 \text{ k}\Omega}{51 \text{ k}\Omega} + 1 = 1.59$$

$$Q = \frac{1}{3 - A_V} = \frac{1}{3 - 1.59} = 0.709$$

$$f_p = \frac{1}{2\pi RC} = \frac{1}{2\pi(47 \text{ k}\Omega)(330 \text{ pF})} = 10.3 \text{ kHz}$$

It takes a Q of 0.77 to produce a ripple of 0.1 dB. Therefore, a Q of 0.709 produces a ripple of less than 0.003 dB. For all practical purposes, the calculated Q of 0.709 means that we have a Butterworth response to a very close approximation.

The cutoff frequency of a Butterworth filter is equal to the pole frequency of 10.3 kHz. Notice in Fig. 19-32b that the pole frequency is at approximately 1 dB. This value is 3 dB down from the passband gain of 4 dB.

PRACTICE PROBLEM 19-6 In Application Example 19-6, change the 47-kΩ resistors to 22 kΩ and solve for A_V , Q , and f_p .

Example 19-7

In Fig. 19-33, what are the pole frequency and Q ? What is the cutoff frequency?


SOLUTION The A_V , Q , and f_p are:

$$A_V = \frac{15 \text{ k}\Omega}{56 \text{ k}\Omega} + 1 = 1.27$$

$$Q = \frac{1}{3 - A_V} = \frac{1}{3 - 1.27} = 0.578$$

$$f_p = \frac{1}{2\pi RC} = \frac{1}{2\pi(82 \text{ k}\Omega)(100 \text{ pF})} = 19.4 \text{ kHz}$$

Figure 19-33 Bessel equal-component example.

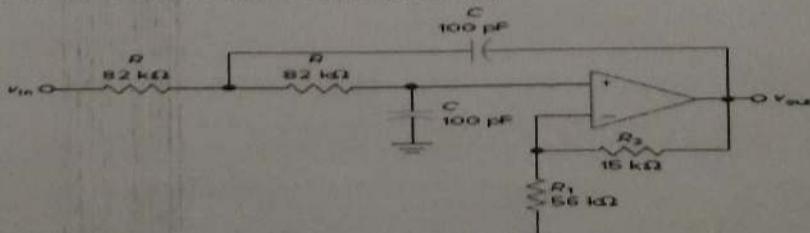

RK

This is the Q of a Bessel second-order response. Therefore, $K_c = 0.786$ and the cutoff frequency is:

$$f_c = 0.786 f_p = 0.786(19.4 \text{ kHz}) = 15.2 \text{ kHz}$$

PRACTICE PROBLEM 19-7 Repeat Example 19-7 with the capacitors equal to 330 pF and the R value set to 100 k Ω .

Example 19-8

What are the pole frequency and Q in Fig. 19-34? What are the resonant, cutoff, and 3-dB frequencies? What is the ripple depth in decibels?

SOLUTION The A_V , Q , and f_p are:

$$A_V = \frac{39 \text{ k}\Omega}{20 \text{ k}\Omega} + 1 = 2.95$$

$$Q = \frac{1}{3 - A_V} = \frac{1}{3 - 2.95} = 20$$

$$f_p = \frac{1}{2\pi RC} = \frac{1}{2\pi(56 \text{ k}\Omega)(220 \text{ pF})} = 12.9 \text{ kHz}$$

Figure 19-26 has Q s only between 1 and 10. In this case, we need to use Eqs. (19-25) through (19-28) to get the K and Q values:


$$K_0 = 1$$

$$K_c = 1.414$$

$$K_3 = 1.55$$

$$A_p = 20 \log Q = 20 \log 20 = 26 \text{ dB}$$

Figure 19-34 Equal-component example with $Q > 0.707$.

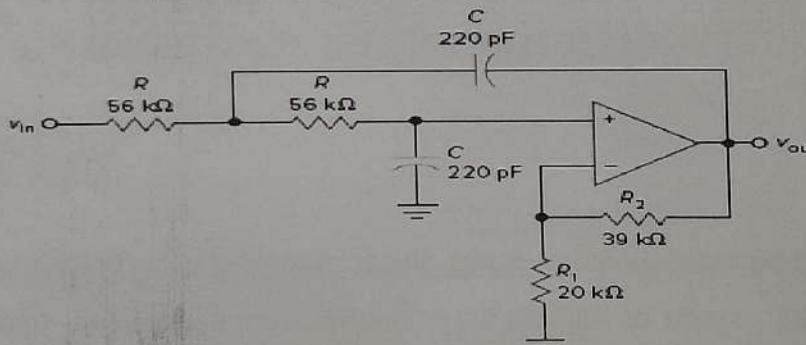

The resonant frequency is:

$$f_0 = K_0 f_p = 12.9 \text{ kHz}$$

The cutoff or edge frequency is:

$$f_c = K_c f_p = 1.414 (12.9 \text{ kHz}) = 18.2 \text{ kHz}$$

and the 3-dB frequency is:

$$f_{3\text{dB}} = K_3 f_p = 1.55 (12.9 \text{ kHz}) = 20 \text{ kHz}$$

The circuit produces a 26-dB peak in the response at 12.9 kHz, rolls off to 0 dB at the cutoff frequency, and is down 3 dB at 20 kHz.

A Sallen-Key circuit like this is impractical because the Q is too high. Since the voltage gain is 2.95, any error in the values of R_1 and R_2 can cause large increases in Q . For instance, if the tolerance of the resistors is ± 1 percent, the voltage gain can be as high as:

$$A_V = \frac{1.01(39 \text{ k}\Omega)}{0.99(20 \text{ k}\Omega)} + 1 = 2.989$$

This voltage gain produces a Q of:

$$Q = \frac{1}{3 - A_V} = \frac{1}{3 - 2.989} = 90.9$$

The Q has changed from a design value of 20 to an approximate value of 90.9, which means that the frequency response is radically different from the intended response.

Even though the Sallen-Key equal-component filter is simple compared to other filters, it has the disadvantage of component sensitivity when high Q s are used. This is why more complicated circuits are typically used for high- Q stages. The added complexity reduces the component sensitivity.

RK

Application Example 19-9

|||| Multisim

What are the pole frequency and Q of the filter shown in Fig. 19-36(a)? What is the cutoff frequency? Show the frequency response using a Multisim Bode plotter.

SOLUTION The Q and pole frequency are:

$$Q = 0.5\sqrt{\frac{R_1}{R_2}} = 0.5\sqrt{\frac{24 \text{ k}\Omega}{12 \text{ k}\Omega}} = 0.707$$


$$f_p = \frac{1}{2\pi C\sqrt{R_1 R_2}} = \frac{1}{2\pi(4.7 \text{ nF})\sqrt{(24 \text{ k}\Omega)(12 \text{ k}\Omega)}} = 2 \text{ kHz}$$

Since $Q = 0.707$, the filter has a Butterworth second-order response and:

$$f_c = f_p = 2 \text{ kHz}$$

The filter has a high-pass response with a break at 2 kHz, and it rolls off at 40 dB per decade below 2 kHz. Figure 19-36(b) shows the Multisim frequency response plot.

Figure 19-36 (a) High-pass Butterworth example; (b) Multisim cutoff frequency.

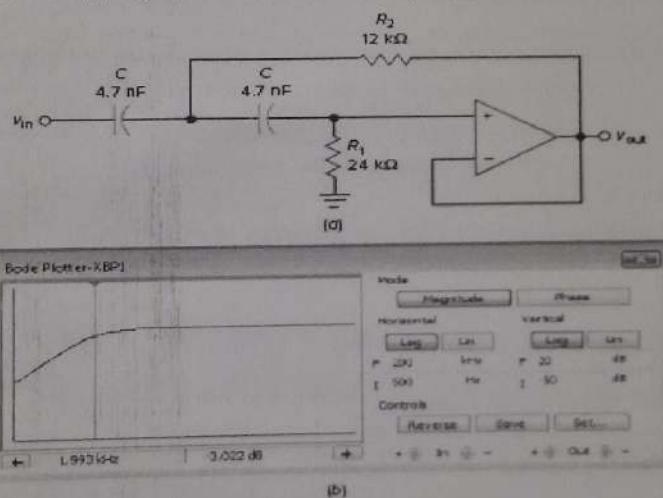


Courtesy of National Instruments.

PRACTICE PROBLEM 19-9 In Fig. 19-36, double the two resistor values. Find the circuit's Q , f_p , and f_c values.

Example 19-10

What are the pole frequency and Q in Fig. 19-37? What are the resonant, cutoff, and 3-dB frequencies? What is the ripple depth or peaking in decibels?

Figure 19-37 High-pass example with $Q > 1$.

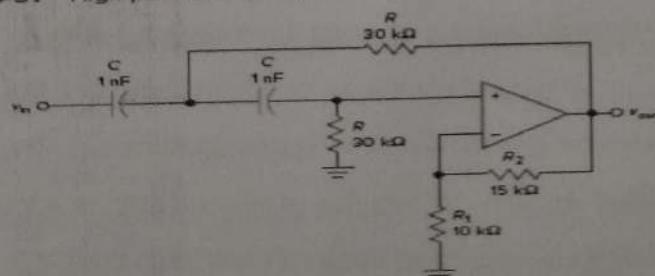

SOLUTION The A_V , Q , and f_p are:

$$A_V = \frac{15 \text{ k}\Omega}{10 \text{ k}\Omega} + 1 = 2.5$$

$$Q = \frac{1}{3 - A_V} = \frac{1}{3 - 2.5} = 2$$

$$f_p = \frac{1}{2\pi R C} = \frac{1}{2\pi(30 \text{ k}\Omega)(1 \text{ nF})} = 5.31 \text{ kHz}$$

RK

In Fig. 19-26, a Q of 2 gives the following approximate values:

$$K_0 = 0.94$$

$$K_c = 1.32$$

$$K_3 = 1.48$$

$$A_p = 20 \log Q = 20 \log 2 = 6.3 \text{ dB}$$

The resonant frequency is:

$$f_0 = \frac{f_p}{K_0} = \frac{5.31 \text{ kHz}}{0.94} = 5.65 \text{ kHz}$$

The cutoff frequency is:

$$f_c = \frac{f_p}{K_c} = \frac{5.31 \text{ kHz}}{1.32} = 4.02 \text{ kHz}$$

The 3-dB frequency is:

$$f_{3\text{dB}} = \frac{f_p}{K_3} = \frac{5.31 \text{ kHz}}{1.48} = 3.59 \text{ kHz}$$

The circuit produces a 6.3-dB peak in the response at 5.65 kHz, rolls off to 0 dB at the cutoff frequency of 4.02 kHz, and is down 3 dB at 3.59 kHz.

PRACTICE PROBLEM 19-10 Repeat Example 19-10 with the 15-k Ω resistor changed to 17.5 k Ω .

Example 19-11

The gate voltage of Fig. 19-42 can vary the JFET resistance from 15 to 80 Ω . What is the bandwidth? What are the minimum and maximum center frequencies?

SOLUTION Equation (19-42) gives the bandwidth:

$$\text{BW} = \frac{1}{2\pi R_1 C} = \frac{1}{2\pi(18 \text{ k}\Omega)(8.2 \text{ nF})} = 1.08 \text{ kHz}$$


With Eq. (19-41), the minimum center frequency is:

$$\begin{aligned} f_0 &= \frac{1}{2\pi C \sqrt{2R_1(R_1 \parallel R_3)}} \\ &= \frac{1}{2\pi(8.2 \text{ nF}) \sqrt{2(18 \text{ k}\Omega)(18 \text{ k}\Omega \parallel 80 \Omega)}} \\ &= 11.4 \text{ kHz} \end{aligned}$$

The maximum frequency is:

$$f_0 = \frac{1}{2\pi(8.2 \text{ nF}) \sqrt{2(18 \text{ k}\Omega)(18 \text{ k}\Omega \parallel 15 \Omega)}} = 26.4 \text{ kHz}$$

Figure 19-42 Tuning an MFB filter with a voltage-controlled resistance.

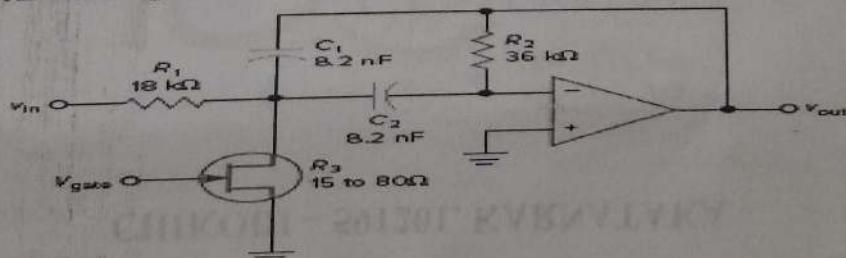

PRACTICE PROBLEM 19-11 Using Fig. 19-42, change R_1 to 10 k Ω , change R_2 to 20 k Ω , and repeat Example 19-11.

Example 19-12

What are the voltage gain, center frequency, and Q for the bandstop filter shown in Fig. 19-43 if $R = 22 \text{ k}\Omega$, $C = 120 \text{ nF}$, $R_1 = 13 \text{ k}\Omega$, and $R_2 = 10 \text{ k}\Omega$?

SOLUTION With Eqs. (19-43) through (19-45):

$$A_V = \frac{10 \text{ k}\Omega}{13 \text{ k}\Omega} + 1 = 1.77$$

$$f_0 = \frac{1}{2\pi(22 \text{ k}\Omega)(120 \text{ nF})} = 60.3 \text{ Hz}$$

$$Q = \frac{0.5}{2 - A_V} = \frac{0.5}{2 - 1.77} = 2.17$$

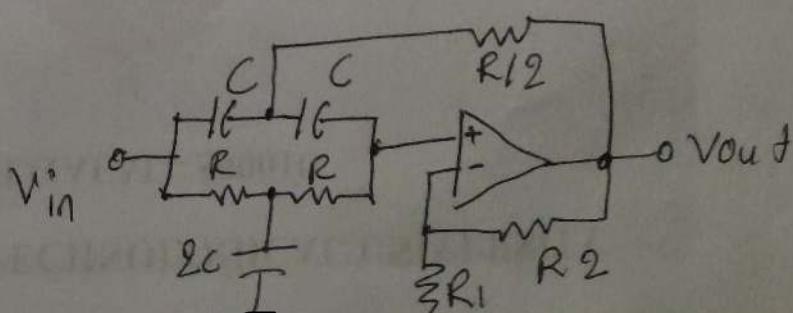


Figure 19-44 (a) Second-order notch filter at 60 Hz; (b) notch filter with $n = 20$.

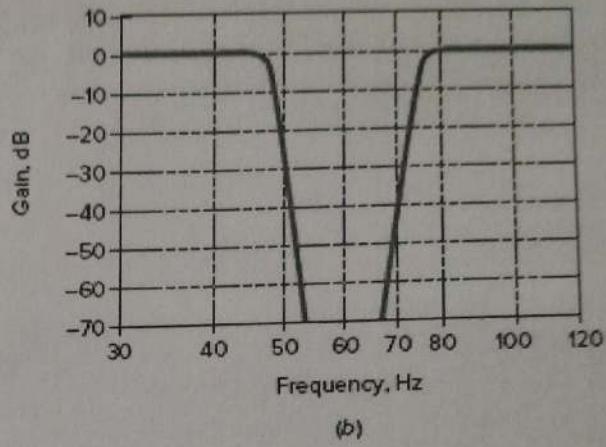
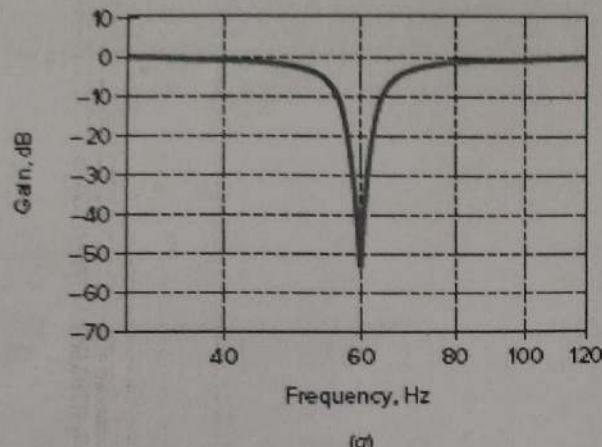


Figure 19-44a shows the response. Notice how sharp the notch is for a second-order filter.

By increasing the order of the filter, we can broaden the notch. For instance, Fig. 19-44b shows the frequency response for a notch filter with $n = 20$. The broader notch reduces component sensitivity and guarantees that the 60-Hz hum will be heavily attenuated.

PRACTICE PROBLEM 19-12 In Fig. 19-43, change R_2 to obtain a Q value of 3. Also, change the C value for a center frequency of 120 Hz.

RK