



## Electronic principles and circuits Module 1 notes

Electronic principles and circuits (Visvesvaraya Technological University)



Scan to open on Studocu

Linear op-amp circuits or

[No Hage amplifiers,  
Current sources & active filters]

### Summing Amplifier

The main function of summing amplifier is to amplify the sum of two input signals.

→ Whenever we need to combine two or more analog signals into single output, the summing amplifier is used.

→ Let consider that when circuit is having two input signals, then gain of each input is given by the ratio of feedback resistance to the appropriate input resistance.

$$A_{CL1} = \frac{R_F}{R_1} \quad \text{&} \quad A_{CL2} = \frac{R_F}{R_2}$$

The summing circuit combines all the amplified input signals into a single output signal.

$$\therefore V_{out} = A_{CL1}V_1 + A_{CL2}V_2$$

### Subtractor

The circuit that subtract two input voltages to produce an output voltage equal to the difference of  $V_1$  &  $V_2$ .

$$V_{out} = V_1 - V_2$$

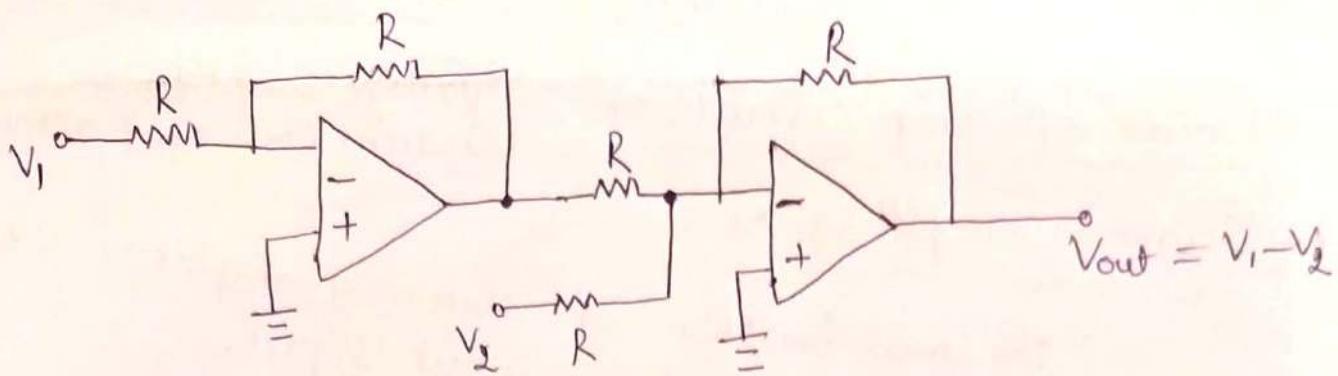


Fig. Substracter.

- In the above ckt input  $V_1$  drives an inverter with a voltage gain of unity, hence op of first stage is  $-V_1$ . This voltage is one of the inputs to the second-stage summing circuit.
- The other inp is  $V_2$ . Since the gain of each channel is unity, the output voltage is

$$\boxed{V_0 = V_1 - V_2}$$

Summing on both Inputs

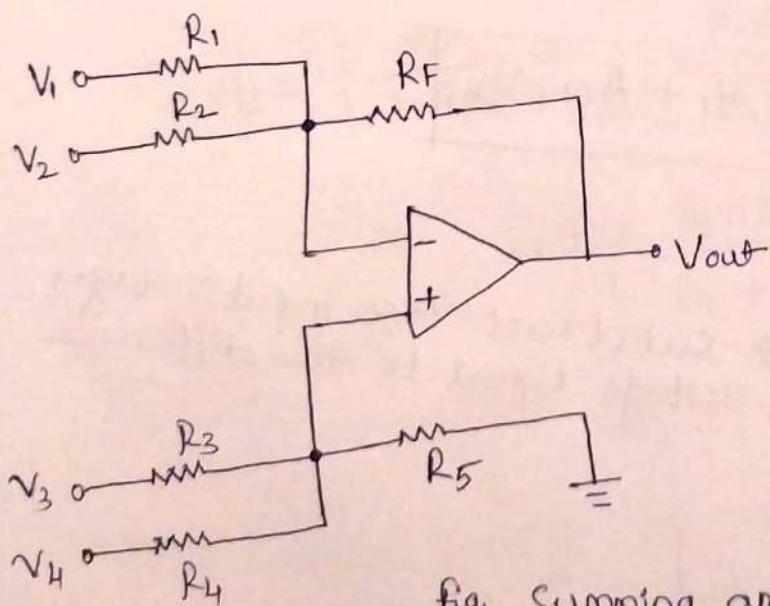


fig. Summing amplifier using both sides of op-amps.

Let consider a summing ckt that consist of two input terminal i.e. Inverting and noninverting input terminals.

- The inverting side of amplifier has two input channels & the non inverting side has two input channels.
- The gain of each inverting channel is the ratio of feedback resistor R<sub>F</sub> to input channel resistance R<sub>1</sub> or R<sub>2</sub>

$$\therefore A_1 = \frac{-AF}{R_1}$$

$$\text{&} A_2 = -\frac{RF}{R_2}$$

Now the gain of each non inverting channel is

$$A_3 = \left[ \frac{RF}{R_1 \parallel R_2} + 1 \right] \left[ \frac{R_4 \parallel R_5}{(R_3 + R_4 \parallel R_5) \parallel R_5} \right]$$

$$A_3 = \left[ \frac{RF}{R_1 \parallel R_2} + 1 \right] \left[ \frac{R_4 \parallel R_5}{R_3 + R_4 \parallel R_5} \right]$$


$$A_4 = \left( \frac{RF}{R_1 \parallel R_2} + 1 \right) \left( \frac{R_3 \parallel R_5}{R_4 + R_3 \parallel R_5} \right)$$

$$\left. \begin{aligned} & \frac{RF}{R_1 \parallel R_2} + 1 \\ & \text{By using Voltage divider} \\ & \Rightarrow \frac{R_4 \parallel R_5}{R_3 + R_4 \parallel R_5} \\ & \Rightarrow \frac{R_3 \parallel R_5}{R_4 + R_3 \parallel R_5} \end{aligned} \right\}$$

The output voltage of ckt is given by.

$$V_{out} = A_1 V_1 + A_2 V_2 + A_3 V_3 + A_4 V_4$$

## The averager

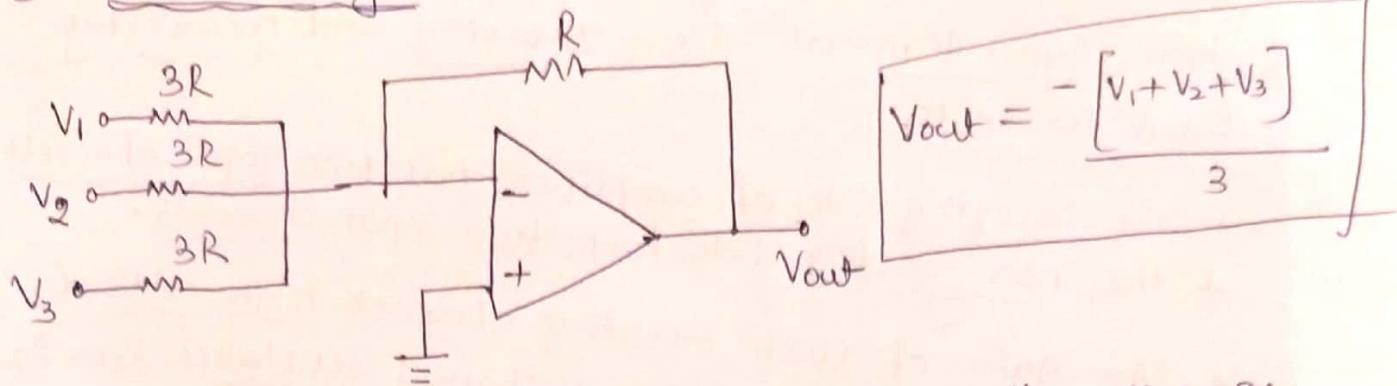

$$V_{out} = -\frac{[V_1 + V_2 + V_3]}{3}$$

"The circuit whose output equals to the average of input voltages.


Each channel has a voltage gain of

$$Av = \frac{R}{3R} = \frac{1}{3}$$

→ when all the amplified outputs are added, we can get average of all IP voltages.

→ Any number of inputs can be used, as long as each channel input resistance is changed to  $nR$ , where  $n$  is number of channels

## D/A Converter

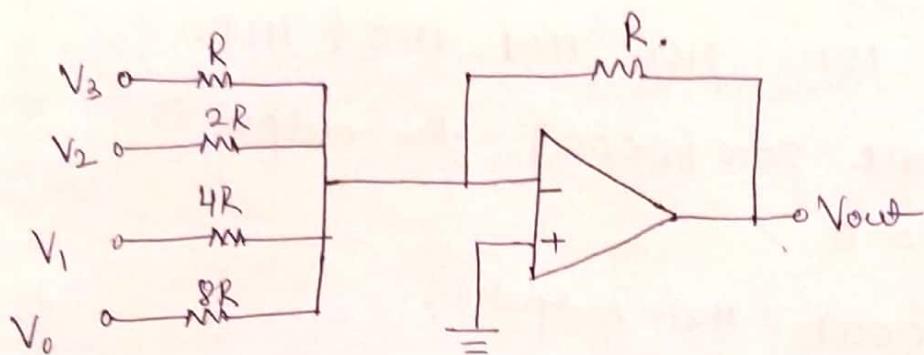

$$A = -\frac{R_f}{R} = -\frac{R}{R} = -1$$

$$A = -\frac{R}{2R} = -0.5$$

$$A = -\frac{R}{4R} = -0.25$$

$$A = -\frac{R}{8R} = -0.125$$

Fig. D/A converter changes digital I/P to analog Voltage.

→ D/A converter is a weighted summing circuit that produces an output equal to the weighted sum of inputs.

→ The weight is same as that of gain of channel.

→ In the above fig the channel gains are

$$A_3 = -1$$

$$A_2 = -0.5$$

$$A_1 = -0.25$$

$$A_0 = -0.125$$

→ In the above fig it is having digital inputs i.e. 1 or 0. & it is having 4 inputs hence it consist of 16 possible input combinations of  $V_3 V_2 V_1 V_0$ .

The digital inputs are  $V_3, V_2, V_1, V_0 \Rightarrow$   
0000, 0001, 0010, 0011, 0100, 0101, 0110, 0111,  
1000, 1001, 1010, 1011, 1100, 1101, 1110 & 1111.

when all inputs are zero [0000], the output is

$$V_{out} = 0$$

when  $V_3, V_2, V_1, V_0 = 0001$ , then output is

$$V_{out} = -[0.125] = -0.125$$

when  $V_3, V_2, V_1, V_0 = 0010$  then output is

$$V_{out} = -[0.25] = -0.25$$

when all i/p are 1' i.e. 1111 then o/p is maximum

$$\therefore V_{out} = -[1 + 0.5 + 0.25 + 0.125]$$

$$\boxed{V_{out} = -1.875}$$


$$\boxed{\therefore V_{out} = -[V_3 + 0.5V_2 + 0.25V_1 + 0.125V_0]}.$$

→ A 4 i/p D/A converter has 16 possible outputs.

→ A 8 i/p " " 256 "

→ A 16 i/p " " 65,536 "

 Problem 8r

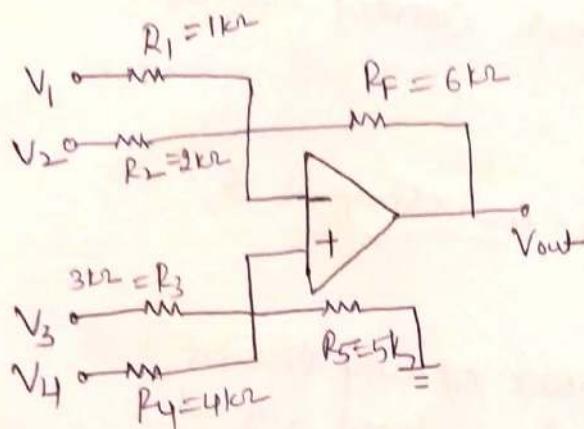

for the circuit shown below  
what is the voltage gain of  
each channel.

$$\text{SOLN} : - A_1 = - \frac{R_F}{R_1}$$

$$A_1 = - \frac{6\text{k}\Omega}{1\text{k}\Omega} = -6$$

$$A_2 = - \frac{R_F}{R_2} = - \frac{6\text{k}\Omega}{2\text{k}\Omega} = -3$$

$$A_3 = \left[ \frac{R_F}{R_1 \parallel R_2} + 1 \right] \left[ \frac{R_4 \parallel R_5}{R_3 + R_4 \parallel R_5} \right]$$

$$= \left[ \frac{6\text{k}\Omega}{1\text{k}\Omega \parallel 2\text{k}\Omega} + 1 \right] \left[ \frac{4\text{k}\Omega \parallel 5\text{k}\Omega}{3\text{k}\Omega + 4\text{k}\Omega \parallel 5\text{k}\Omega} \right]$$

$$A_3 = 4.26$$

$$A_4 = \left[ \frac{R_F}{R_1 \parallel R_2} + 1 \right] \left[ \frac{R_3 \parallel R_5}{R_4 + R_3 \parallel R_5} \right]$$

$$= \left[ \frac{6\text{k}\Omega}{1\text{k}\Omega \parallel 2\text{k}\Omega} + 1 \right] \left[ \frac{3\text{k}\Omega \parallel 5\text{k}\Omega}{4\text{k}\Omega + 3\text{k}\Omega \parallel 5\text{k}\Omega} \right]$$

$$A_4 = 3.19$$

## ④ Non linear op-amp circuits

Linear  $\Rightarrow$  Voltage amplifiers, Current sources, and active filters.

Non linear  $\Rightarrow$  Comparator, waveshapers, & active diode circuits.

The output of a nonlinear op-amp circuit usually has a different shape from input signal because the op-amp saturates during part of input signal or cycle.

## ④ Comparator with zero Reference

$\Rightarrow$  Comparators are the circuit which is used to compare one voltage with another voltage.

Comparators are similar to an op-amp because it has two input voltages [NI & INV] and one o/p voltage i.e. either low or High. [0 or 1].



④ Basic Idea


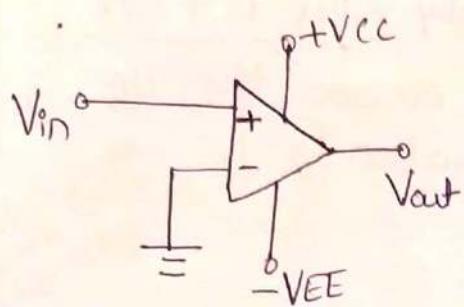


Fig ④ comparator

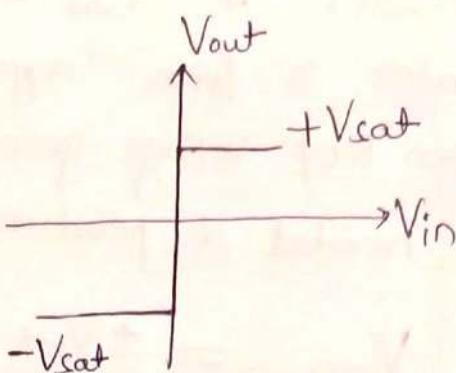

⑤ I/O Response.

→ When we are connecting op-amp without feedback resistor then circuit results in comparator.

Due to high open-loop voltage gain, a positive input voltage produces a positive saturation, & negative input voltage produces negative saturation.

→ The above circuit is also called as zero-crossing-detector because the output voltage ideally switches from low to high or vice versa whenever input voltage crosses zero.

Fig ⑥ The input-output response of a zero crossing detector is shown in fig.

⇒ The minimum input voltage that produces a saturation is

$$\boxed{V_{in(min)} = \frac{\pm V_{sat}}{A_{OL}}}$$

where,

$A_{OL} \rightarrow$  open loop gain.

Let consider if  $V_{sat} = 14V$ , then o/p swing of Comparator is from approximately  $-14V$  to  $+14V$ .

If open loop voltage gain is 1,00,000 the i/p voltage needed to produce saturation is

$$V_{in(min)} = \frac{\pm V_{sat}}{AOL}$$
$$= \frac{\pm 14V}{100\ 000}$$

$$\boxed{V_{in(min)} = \pm 0.014mV}$$

→ From above value we can say that when i/p voltage more positive than  $+0.014mV$  drives the comparator into positive saturation. & when  $-0.014mV$  drives into negative saturation.

#### ④ Lissajous pattern

It appears on an oscilloscope when harmonically related signals are applied to the horizontal & vertical inputs.

## ④ Inverting Comparator

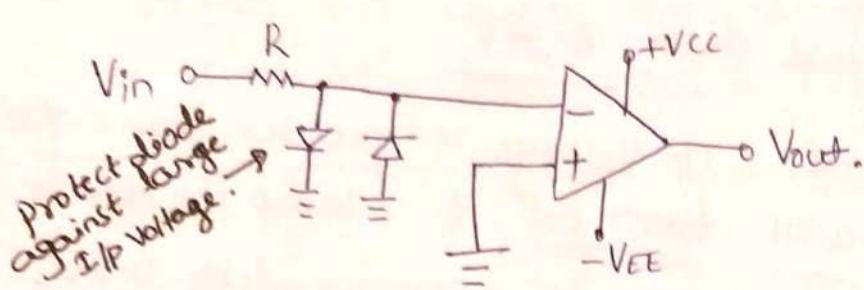


Fig. @ Inverting comparator with Clamping diode.

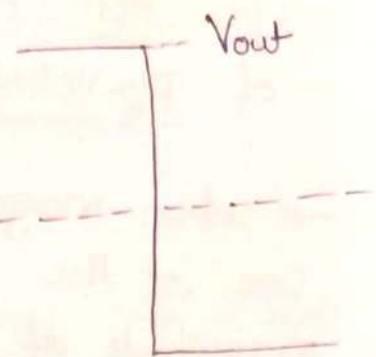


Fig. ⑥ Input/Output.

→ Inverting comparator is a ckt in which we are applying input to INV terminal of comparator & NI terminal is connected to ground.

→ As we are applying <sup>+ve Voltage</sup> I/p to INV terminal hence it produces a maximum negative output.

& -ve i/p Voltage produces a maximum +ve output.

### Diode Clamps

→ In the above ckt we are using diode clamps, the main function of diode clamp is to protect the comparator against excessively large input Voltage.

→ Ex: IC LF311 is an IC comparator it is having maximum I/p rating of  $\pm 15V$ , If I/p Voltage exceeds  $\pm 15V$ , LF311 will be destroyed.

→ Some comparators are having rating of  $\pm 5V$ ,  $\pm 30V$ ,

→ The diodes are not having any effect on operation of circuit as long as the magnitude of I<sub>p</sub> Voltage is less than 0.7V



→ When magnitude of I<sub>p</sub> Voltage is greater than 0.7V one of the diode will turn ON & clamp the ~~theode~~ magnitude of INV I<sub>p</sub> Voltage to approximately 0.7V.

④ Converting sine wave to square wave or

Threshold point / Ref. point / Trip point ⇒ It is an input voltage that causes the output voltage to switch states from low to high & High to low.

→ Zero crossing detector has two output states, any periodic I<sub>p</sub> signal that crosses zero threshold will produce a rectangular O<sub>p</sub> waveform.

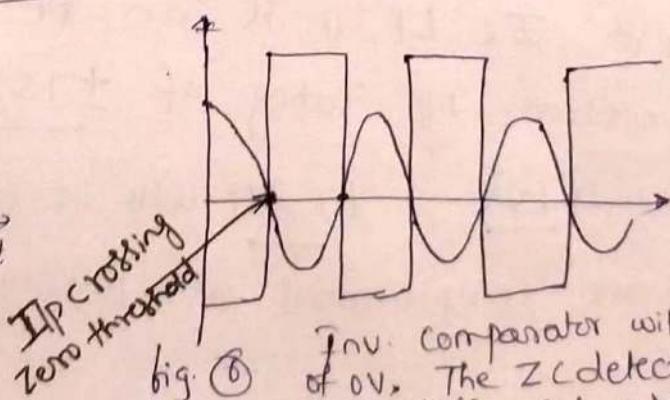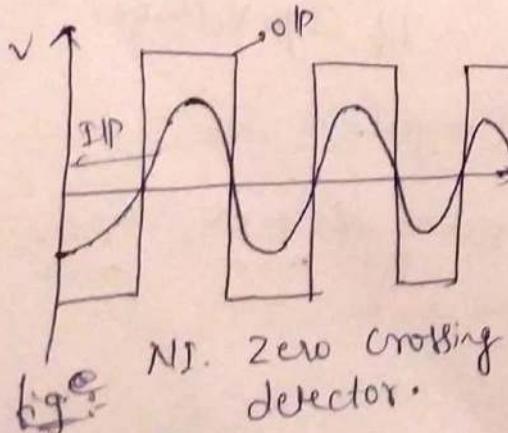
Ex If a sine wave is a I<sub>p</sub> to NJ comparator with a threshold of 0V, the O<sub>p</sub> will be square wave. From below fig we can say that the O<sub>p</sub> of zero crossing detector switches states each time the input voltage crosses the zero threshold.



Inv. comparator with threshold of 0V. The ZC detector the O<sub>p</sub> sq. wave is 180° out of phase with I<sub>p</sub> sine wave.
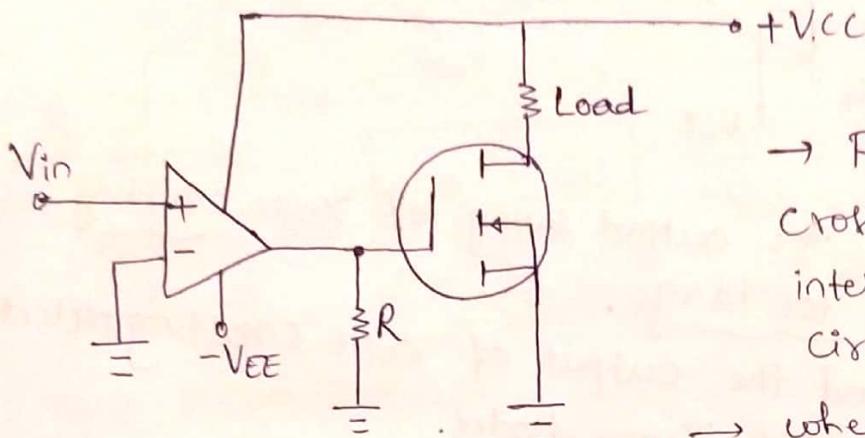
## ★ Interfacing Analog & Digital Circuits

⇒ Comparators usually interface at their o/p with digital ckt such as CMOS, EMOS & TTL.



→ Fig. shows how a zero crossing detector can interface with an EMOS circuit.

→ when I<sub>IP</sub> voltage greater than zero, the o/p of comparator is high. This turns on the power FET & produces a large load current.


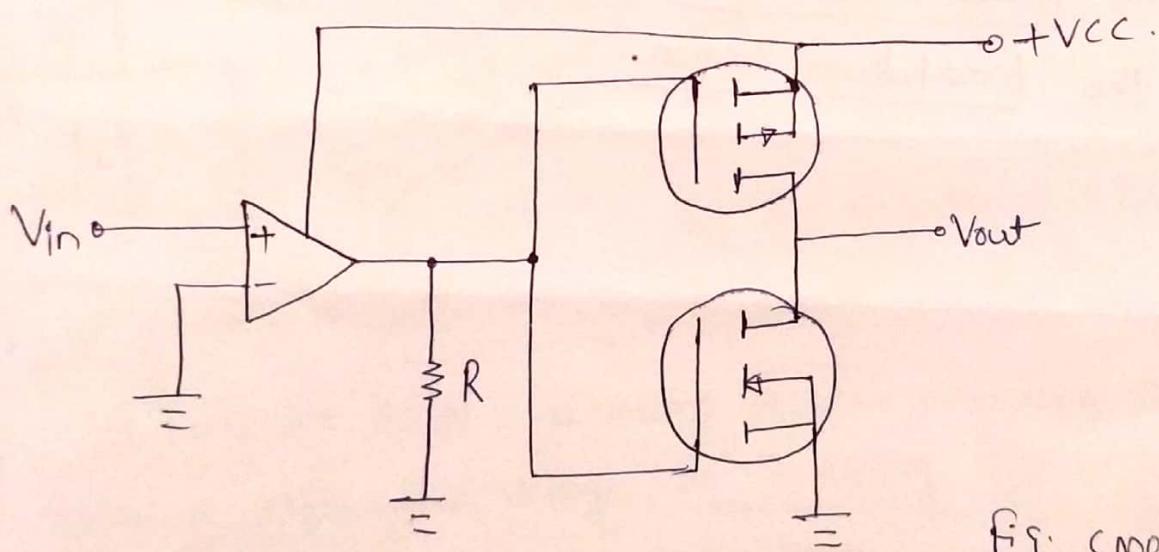


fig. CMOS

→ Above fig. shows Zero crossing detector interfacing with a CMOS inverter. A comparator I<sub>IP</sub> greater than zero produces a high I<sub>IP</sub> to CMOS inverter.

## Bounded output or

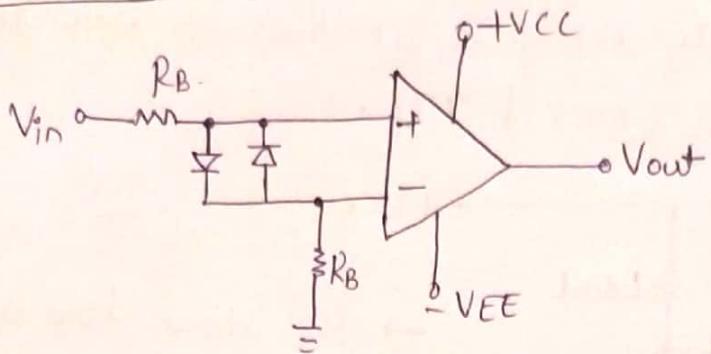

→ In some cases the output swing of zero crossing detector may be too large.

we can bound the output of zero crossing detector by using back to back Zener diodes.

→ In the above fig the INV comparator has bounded output because one of the diode will be conducting in the forward direction & other will be operating in the breakdown region.

## Comparators with Nonzero References


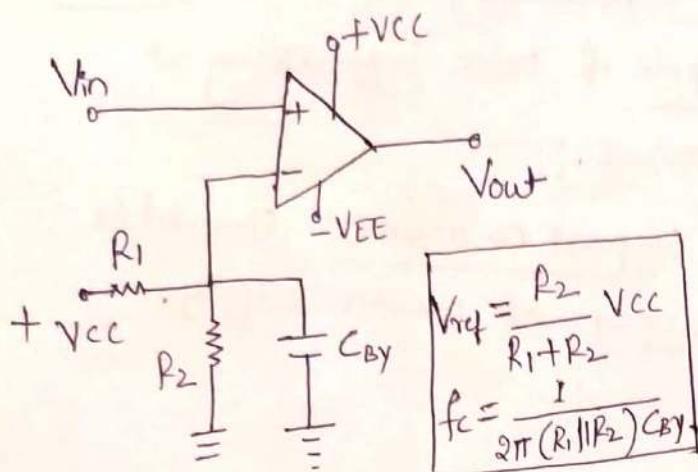


Fig. ④ positive threshold.

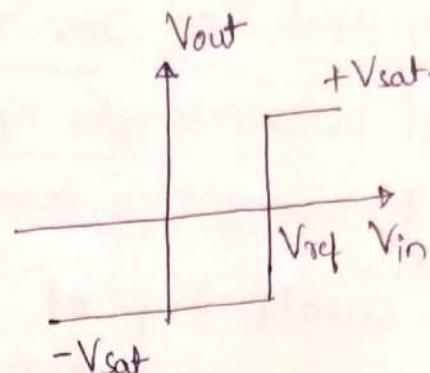

- Key points
- Ref voltage at Inv  
 $V_{ref} = \frac{R_2}{R_1 + R_2} V_{CC}$ .
- When  $V_{in} > V_{ref} \Rightarrow$  Diff I/P is +ve & Vo = high
- When  $V_{in} < V_{ref} \Rightarrow$  Diff I/P is -ve & Vo = low

Fig. ⑤ positive I/O response.

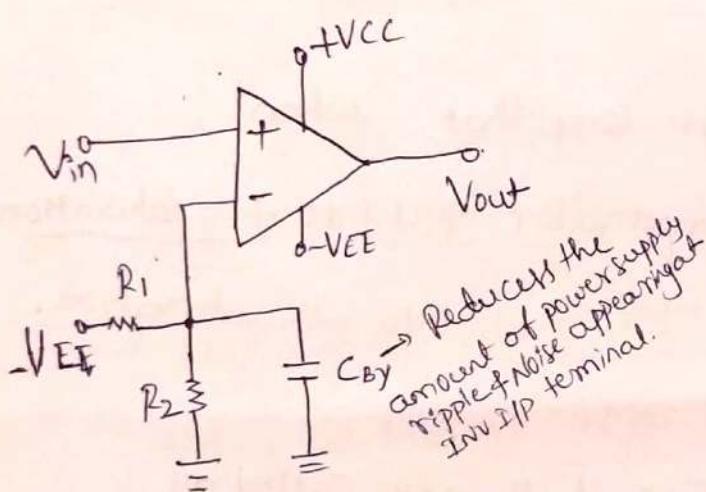


Fig. ⑥ Negative threshold.

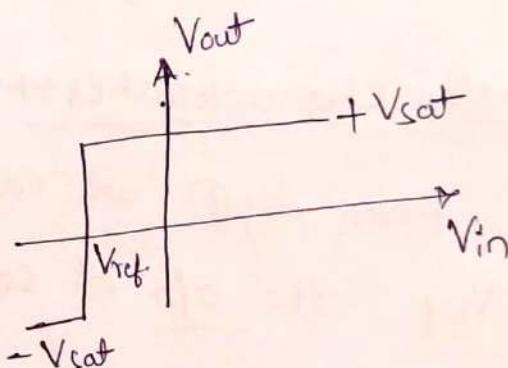


Fig. ⑦ Negative I/O Response.

Let consider fig. ⑦, a voltage divider produces the following reference voltage for inverting I/P.

$$V_{ref} = \frac{R_2}{R_1 + R_2} V_{CC}$$

Note:- ① When  $V_{in} > V_{ref}$ , The differential I/P voltage is +ve & the o/p is high.

② When  $V_{in} < V_{ref}$ , The diff I/P voltage is -ve & o/p is low.

→ In the above circuit diagram a bypass capacitor is typically used on Inv I/P terminal, it will reduce amount of power supply ripple & noise appearing at Inverting I/p terminal.

→ The cutoff freq. of bypass capacitor should be lower than the ripple frequency of power supply.

$$\therefore f_c = \frac{1}{2\pi(R_1||R_2)C_{By}}$$

### Transfer characteristics

from fig.① we can say that, when  $V_{in} > V_{ref}$ , the o/p of comparator goes into +ve saturation.  
 $V_{in} < V_{ref}$ , the " " " into -ve saturation.

→ The above comparator circuit is also called as limit detector because +ve o/p indicates that the input voltage exceeds a specific limit with different values of  $R_1$  &  $R_2$ , we can set the limit anywhere between 0 &  $V_{CC}$ .

→ when a -ve reference voltage is applied to the INV. I/P when  $V_{in}$  is more positive than  $V_{ref}$ , the differential I/P voltage is +ve & o/p is high.  
→ when  $V_{in}$  is more -ve than  $V_{ref}$ , o/p is low.

## ④ Single supply comparator

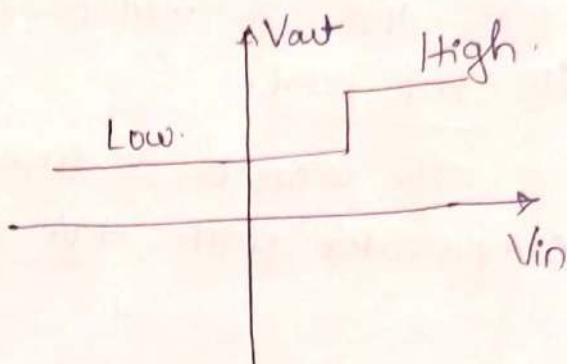
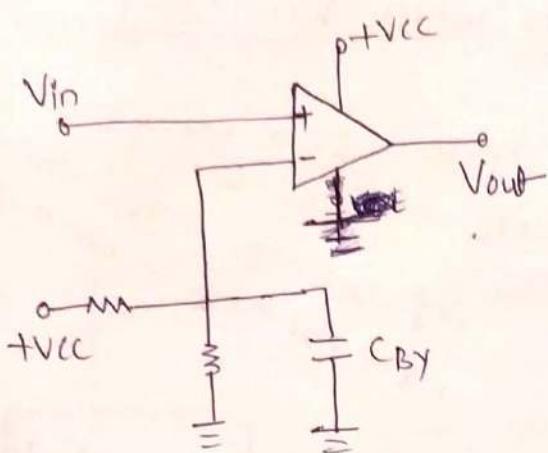


fig. ④ Single supply comparator

fig. I/O Response.

- A single supply comparator is a circuit in which -VEE pin is directly connected to ground.
- Here the O/P Voltage has only the polarity either a low or high positive voltage.
- Let consider when  $V_{CC} = 15V$  then O/P swing is from approximately  $+1.5V$  to  $+13.5V$ .  
 $(\text{low state})$        $(\text{high state})$ .

when  $V_{in} > V_{ref} \Rightarrow V_o = \text{high}$  —

$V_{in} < V_{ref} \Rightarrow V_o = \text{low.}$  —

## # Comparator with Hysteresis

→ when  $V_{op}$  to comparator contains large amount of noise, the  $V_{op}$  will be erratic when  $V_{in}$  is near the trip point.

The way to reduce the noise is by using a comparator with +Ve feedback.

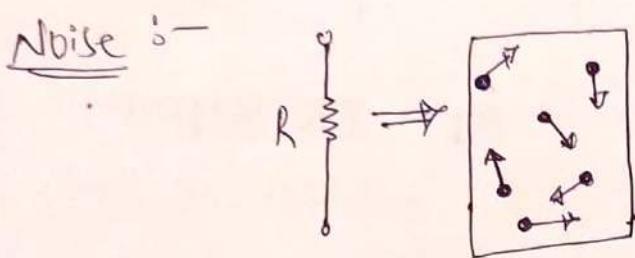


fig. ② Random Electron motion in resistor

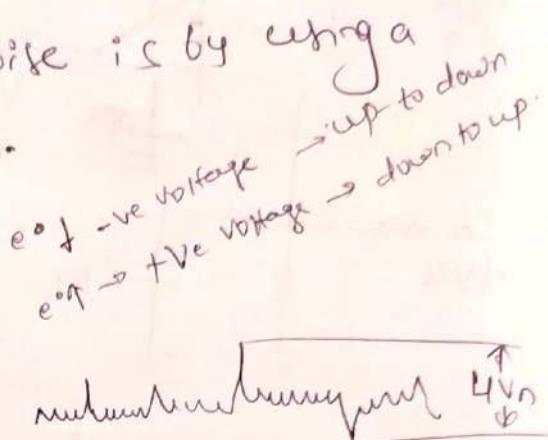


fig. ③ Noise on oscilloscope.

- Noise is any kind of unwanted signal:  
The electric motors, neon signs, power lines, car ignitions, lightning, etc. produces an electromagnetic field that can induce a noise voltages into electronics.  
→ Power supply ripple is also classified as noise.  
By using regulated power supplies we can reduce the ripple & induced noise to an acceptable level.

Thermal noise → The noise generated due to random motion of free electrons inside resistor.  
The energy for this electron motion comes from the thermal energy of surrounding air.

→ when electrons move up than down, producing a small negative voltage across resistor. when electrons move down than up producing a +ve voltage.

The randomness of electrons motion inside resistor produces distribution of noise at virtually all frequencies.

### ④ Schmitt Trigger ↗


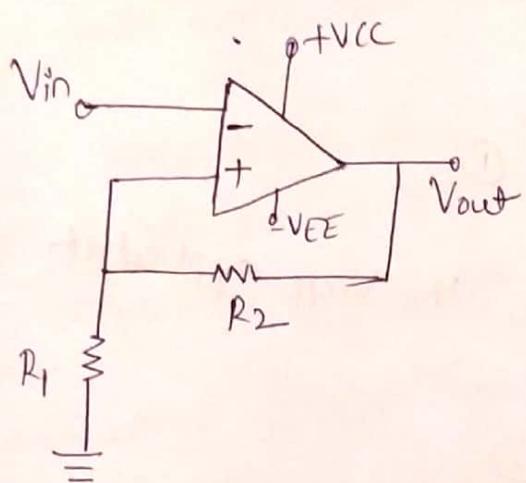


fig. INV Schmitt trigger

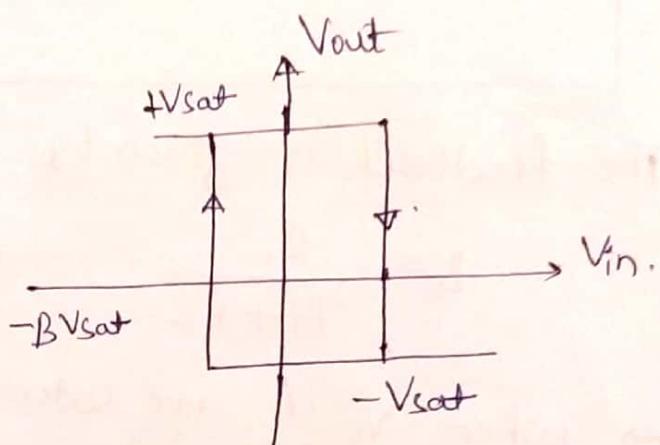

⑥ I/O response has Hysteresis.

→ Let consider above comparator circuit, in which we are applying i/p voltage to inverting input. Because the feedback voltage is aiding the i/p voltage, the feedback is +ve.

∴ Schmitt trigger ↗ A comparator using +ve feedback is called as Schmitt trigger.

Working → When comparator is +vely saturated, a positive voltage is fed back to NI i/p terminal. The +ve feedback holds o/p to high state.

→ when comparator is -vely saturated, a -ve voltage is fed back to NI terminal, holding  $V_o = \text{low}$ .

Comparator:-

+ve saturation  $\Rightarrow$  +ve feedback to NI  $\Rightarrow V_o = +\text{Ve}$

-ve "  $\Rightarrow$  -ve " "  $\Rightarrow V_o = -\text{Ve}$

The feedback is given by

$$B = \frac{R_1}{R_1 + R_2} \quad \text{--- } ①$$

$\Rightarrow$  when  $V_o$  is +ve saturated, the  $V_{ref}$  applied at NI input terminal is

$$V_{ref} = +B V_{sat} \quad \text{--- } ②$$

$\Rightarrow$  when IIP is -veley saturated

$$V_{ref} = -B V_{sat} \quad \text{--- } ③$$

Hysteresis  $\Rightarrow$  The unusual response of Schmitt trigger is called as hysteresis.

Let consider fig ⑥. let consider the point  $+V_{sat} = V_0$

now move slightly towards right side along horizontal line

then  $V_{in}$  is changing but  $V_0 = +V_{sat}$ .

→ when reached at corner of horizontal line. then  
 $V_{in} = +BV_{sat}$ , then  $V_0$  goes into transition region  
b/w high & low states.

→ Now move finger down along vertical line, when  
it reaches to lower horizontal line o/p voltage is  
negatively saturated & equal to  $-V_{sat}$ .

→ when finger reaches to lower left corner  
i.e.  $V_{in} = -BV_{sat}$ , then o/p voltage goes into  
transition from low to high.

Here we are using two trip points.

$$UTP = BV_{sat} -$$

$$\& LTP = -BV_{sat}.$$

The difference b/w UTP & LTP is called as  
Hysteresis.

$$\boxed{H = UTP - LTP.}$$

$$H = BV_{sat} - [-BV_{sat}]$$

$$\boxed{H = 2BV_{sat}}$$

## Non inverting schmitt trigger:-

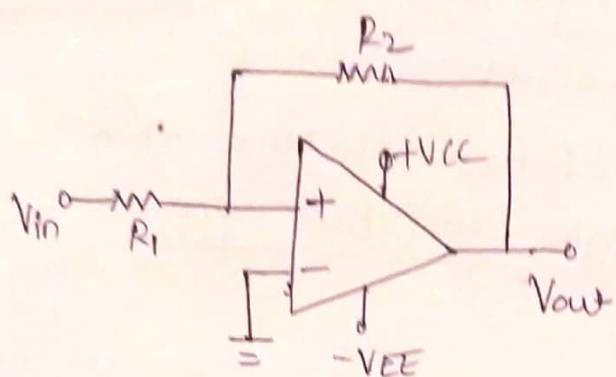


Fig. NI Schmitt trigger

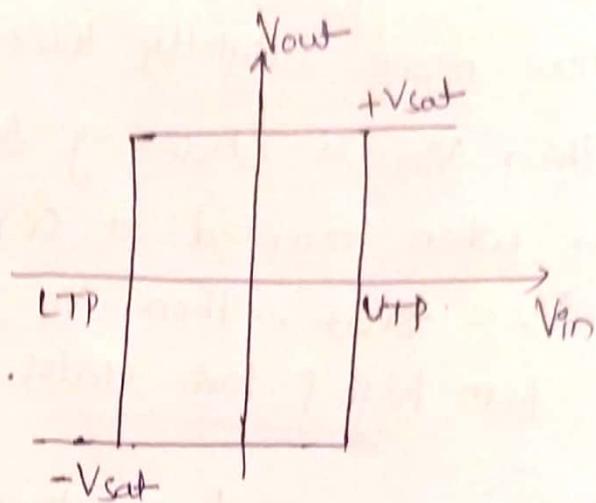


Fig. I/O Response,

- when  $V_o \rightarrow +ve$  saturated, the feedback voltage to NI input is +ve. which results in positive saturation.
- when  $V_o \rightarrow -ve$  saturated, the feedback to NI IP is -ve which results in -ve saturation.
- Here  $V_o$  is at -ve saturation until  $V_{in}$  becomes more +ve than UTP, but when  $V_{in} > UTP$  then O/p switches from -ve to +ve saturation.
- ⇒ When  $V_o = +ve$  saturation until  $V_{in} < LTP$  when  $V_{in}$  is less than LTP,  $V_o$  i.e- O/p changes from again +ve to -ve saturation.

$$UTP = \frac{R_1}{R_2} V_{sat}$$

$$LTP = -\frac{R_1}{R_2} V_{sat}$$

Ⓐ Oscillator ⚬

Ⓑ Theory of Sinusoidal oscillation ⚬

The sinusoidal oscillator is build by using an amplifier with positive feedback.


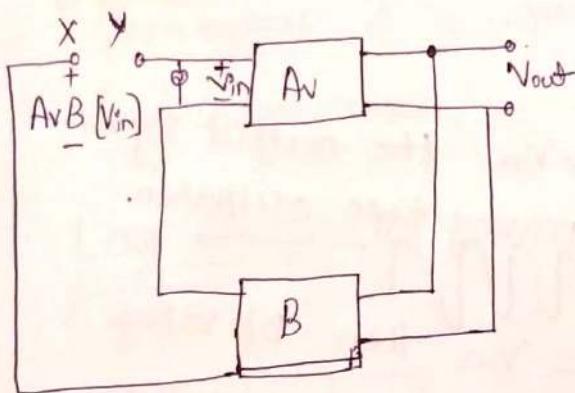


fig @ Feedback voltage returns to point 'x'.

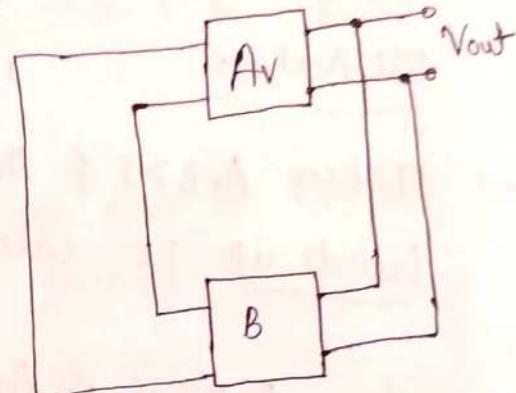

fig(b) connecting points x & y

→ Let consider an ac source driving the input terminals of an amplifier. i.e. fig. @.

The amplified op voltage is given by

$$V_{out} = Av(V_{in}) \quad \text{--- ①}$$

The feedback voltage returning to point 'x' is given by

$$V_f = Av B(V_{in}) \quad \text{--- ②}$$

where  $B$  is called as feedback factor.


If phase shift through amplifier & feedback is equivalent to  $0^\circ$ ,  $Av B(V_{in})$  is in phase with  $V_{in}$ .

→ when we connect point 'x' to point 'y' & simultaneously remove voltage source  $V_{in}$ . Then feedback voltage  $A_v B(V_{in})$  drives o/p of amplifier. i.e. fig ①

→ If when  $A_v B < 1$ , &  $A_v B(V_{in}) < V_{in}$  then o/p swing signal will die out, i.e. called at decaying oscillation.

→ When  $A_v B > 1$  &  $A_v B(V_{in}) > V_{in}$ , the output signal builds up, i.e. called at growing type oscillation.

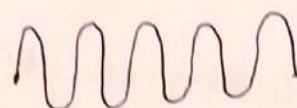→ When  $A_v B = 1$  &  $A_v B(V_{in}) = V_{in}$  then o/p voltage is Steady Sine wave i.e. called at sustained oscillation.




④ Starting voltage is thermal noise or  
As we know that resistors contains free electrons, due to, due to ambient temperature, these free electrons move randomly in different directions. & generate noise voltage across resistors. The motion is so random that it contains frequencies to over 1000 GHz. Hence each resistor as a small ac voltage source producing all frequencies.

## ④ Wein bridge oscillator

- Wein bridge oscillator circuit is a standard oscillator ckt for low to moderate frequencies, in the range of 5 Hz to 1 MHz.
- It is almost always used in commercial audio generators & is usually preferred for other low freq. applications.

## Lag circuit

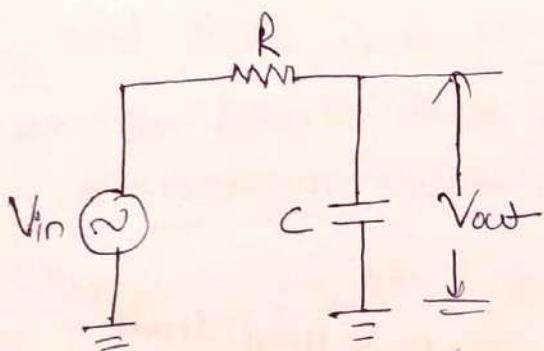

The voltage gain of by pass ckt is given by


$$\frac{V_{out}}{V_{in}} = \frac{X_C}{\sqrt{R^2 + X_C^2}}$$

& phase angle

$$\phi = -\arctan \frac{R}{X_C}$$

where  $\phi$  is the phase angle between O/P & I/P.

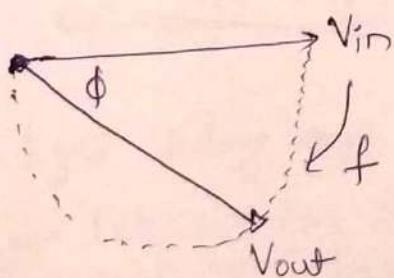where -ve sign indicates O/P Voltage lags I/P voltage



→ In this fig. half circle shows the possible positions of o/p phaser voltage.

→ This indicates that o/p phaser can lag i/p phaser by an angle b/w of  $-90^\circ$ .

Lead Ckt :-

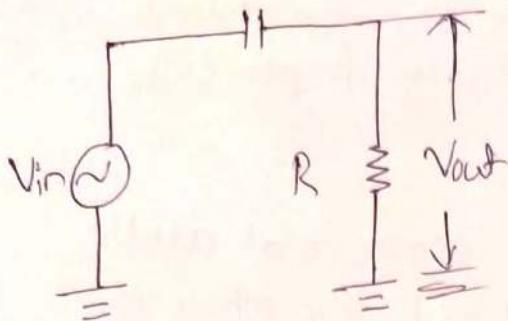


fig @ coupling ckt

Let consider coupling ckt,  
above ckt is given by

$$\frac{V_{out}}{V_{in}} = \frac{R}{\sqrt{R^2 + X_c^2}}$$

$$\text{& } \phi = \arctan \frac{X_c}{R}$$

Here phase angle is +ve hence O/P voltage leads input voltage

→ The half circle shows the possible positions of O/P phasor voltage. This implies that O/P phasor can lead the input phasor by an angle b/w 0° & +90°.

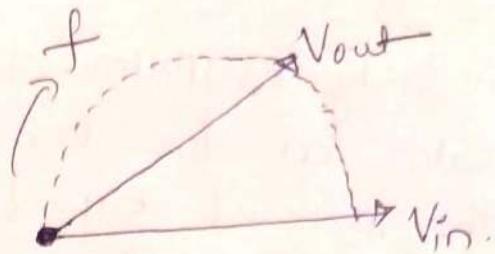


fig. ⑥ phasor diagram.

the voltage gain of

## Lead-lag circuit or

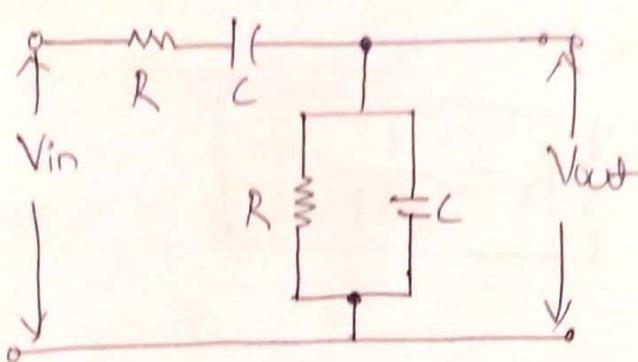


Fig: lead lag ckt.

when wein-bridge oscillator uses a resonant feedback ckt called as lead-lag ckt.

→ at low freq the series capacitor acts as open to i/p signal, & there is no output signal.

- At high freq, the shunt capacitor looks shorted and there is a no output.
- In between these extremes, the output voltage reaches a maximum value.

Resonant freq or The frequency where the output is maximum. At this freq, the feedback fraction B reaches a maximum value of 1/3.

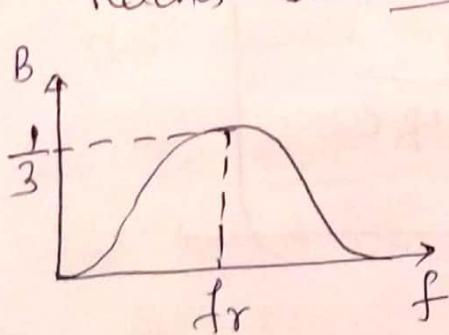


fig @ Voltage gain


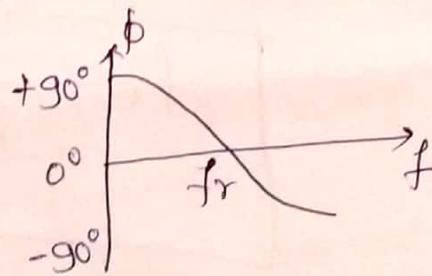


fig @ phase response.

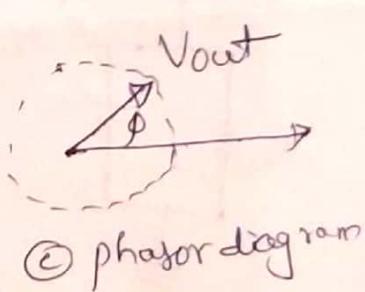

④ phasor diagram

Let consider fig it indicates that phase angle of O/P

- Let consider fig it indicates that phase angle of O/P
- Voltage vs input voltage.
- At low freq the phase angle is positive
- At high freq " " " Negative.
- At resonant freq the phase shift is 0°.


at resonant freq  $\underline{x_c = R}$

$$\therefore \frac{1}{2\pi f_r C} = R$$

$$\boxed{\therefore R = \frac{1}{2\pi f_r C}}$$

OR

$$\boxed{f_r = \frac{1}{2\pi R C}}$$

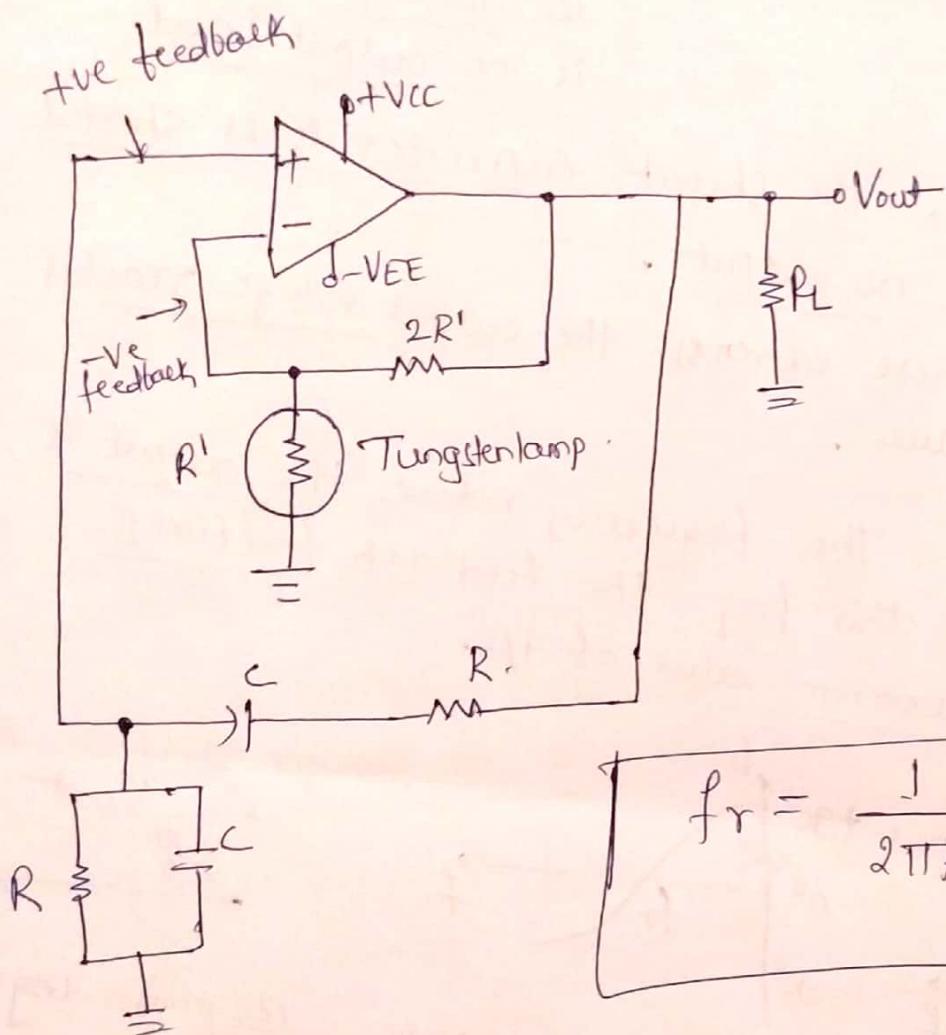

$$\boxed{f_r = \frac{1}{2\pi R C}}$$

RC oscillators &c.

① Twin-T oscillator.

② Phase-shift oscillator.

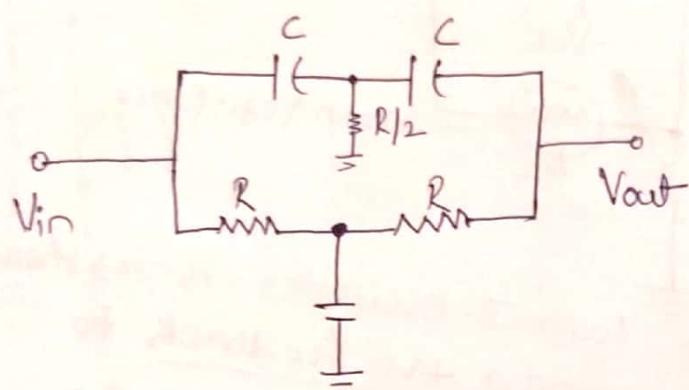
1. Twin-T oscillator

Fig. Twin-T filter

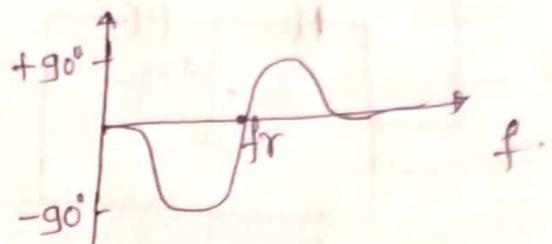


fig. ⑥ phase response.

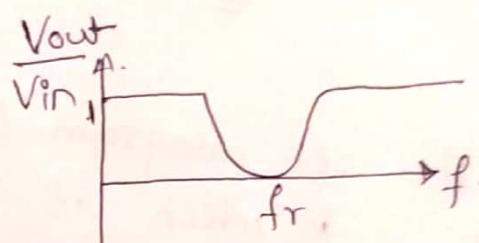


fig. ⑦ Frequency Response.

→ A twin-T filter acts like a lead lag circuit with a changing phase angle.

→ Let consider resonant frequency  $f_r$  where phase shift equals to  $0^\circ$ . as shown in fig. ⑥.

→ In twin-T filter the voltage gain is equal to 1 at low & high frequencies.

betw low & high freq, resonant frequency available at which voltage gain drops to 0. fig. ⑦.

$$f_r = \frac{1}{2\pi RC}$$


Key points :-

$\phi = 0$  at resonant freq.

$A_v = 1$  at low & high freq  
= 0 at  $f_r$ .

## Twin-T oscillator


key point

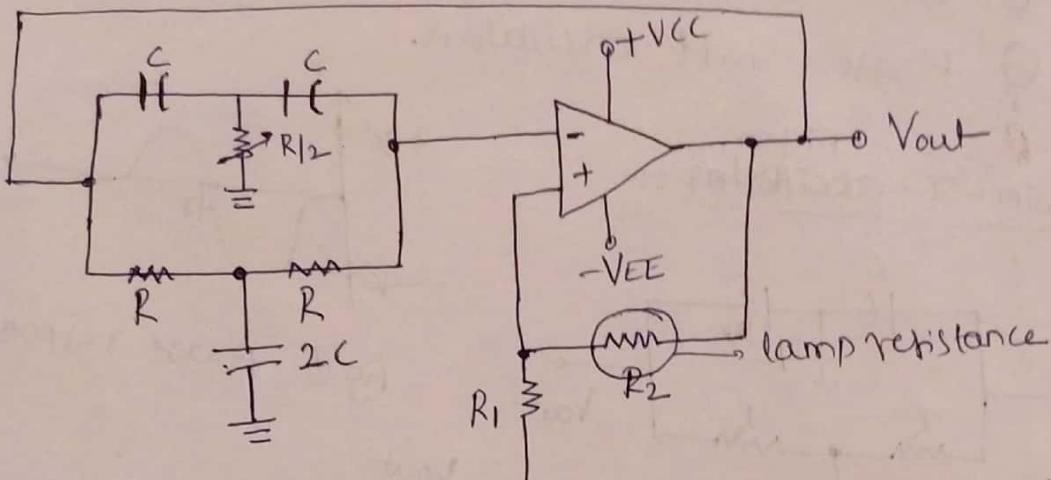

- The circuit diagram for twin-T oscillator is as shown in fig., in which it is having a +ve feedback to the non inverting input through voltage divider  $R_1$  &  $R_2$ .
- Using a -ve feedback through twin-T filter.
- when power is turned on the lamp resistance  $R_2$  is low. & +ve feedback is more or maximum. But as oscillations buildup lamp resistance increases whereas +ve feedback decreases.
- As feedback decreases, the oscillations level off & become constant.
- In twin-T filter resistance  $R/2$  is adjusted it is necessary because the circuit oscillates at a frequency slightly different from ideal resonant frequency.

key point :- +ve feed back at NI & -ve feedback at Twin T-filter.  
→ when power ON -  $R_2$  is low +ve feed back but as oscillation increase  $R_2$  is less +ve feed decreases & lamp resistance increases.

→ Problem 8

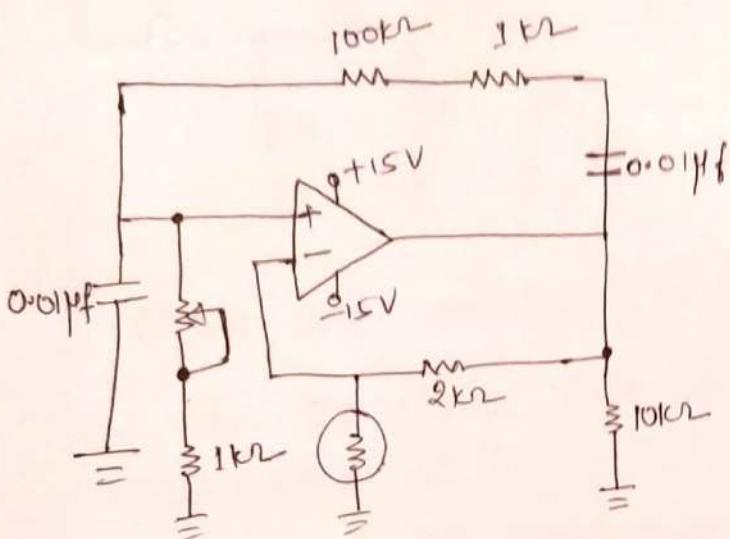

For the shown circuit calculate minimum & maximum frequencies. The two Variable resistors are ganged, which means that they change together & have the same value for any wiper position.

$$\text{Soln} \rightarrow R = 100\text{k}\Omega \text{ & } R = 1\text{k}\Omega \\ f = \frac{1}{2\pi RC}$$

The minimum freq. of oscillation is


$$f_{\min} = \frac{1}{2\pi R C} = \frac{1}{2\pi [10\text{k}\Omega] [0.01 \times 10^{-6}]} = 158\text{Hz}$$

The maximum freq. of oscillation is

$$f_{\max} = \frac{1}{2\pi R C} = \frac{1}{2\pi [1\text{k}\Omega] (0.01 \times 10^{-6})} = 15.9\text{kHz}$$

## ② Phase shift oscillator

EP-M3-17

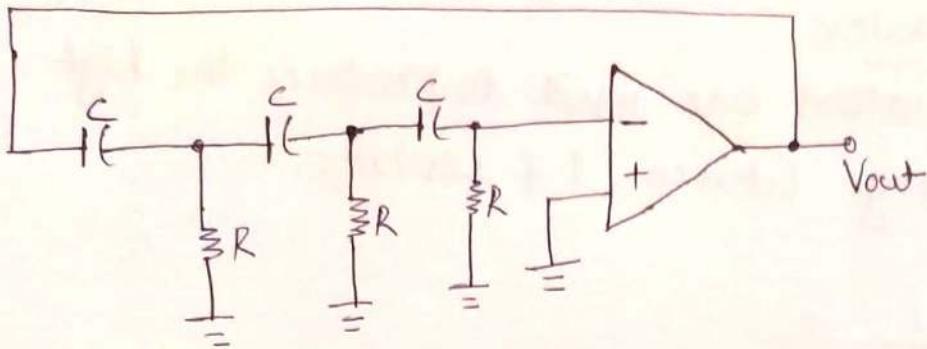

phase shift oscillator with three lead ckt.

- In RC phase shift oscillator there is a three combinations of  $R & C$  in feedback path.
- a lead ckt produces a phase shift from  $0^\circ$  to  $90^\circ$ .
- Hence in the above ckt each combination of  $R & C$  produces  $60^\circ$  of phase shift hence total phase shift around ckt is  $180^\circ$  & amplifier produces  $180^\circ$  of phase shift hence total phase shift =  $360^\circ$ .  
→  $|A_{vB}| > 1$  ckt produces required oscillation.

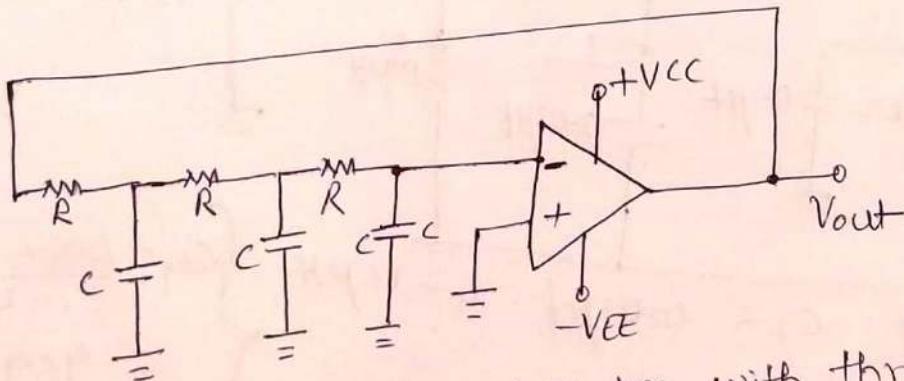


fig. Phase shift oscillator with three lag ckt.

→ amp. produces  $\rightarrow 180^\circ$  phase shift

→ 3  $R & C$  combination  $\rightarrow -180^\circ$  "  $0^\circ$  phaseshift

$|A_{vB}| > 1$ , ckt produces oscillation.

## The Colpits oscillator

LC oscillators are used to produce the high frequency range between 1 & 500 MHz.


$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$C = \frac{C_1 C_2}{C_1 + C_2}$$

$$B = \frac{C_1}{C_2}$$

$$A_V(\text{min}) = \frac{C_2}{C_1}$$

$\Rightarrow$  Problem

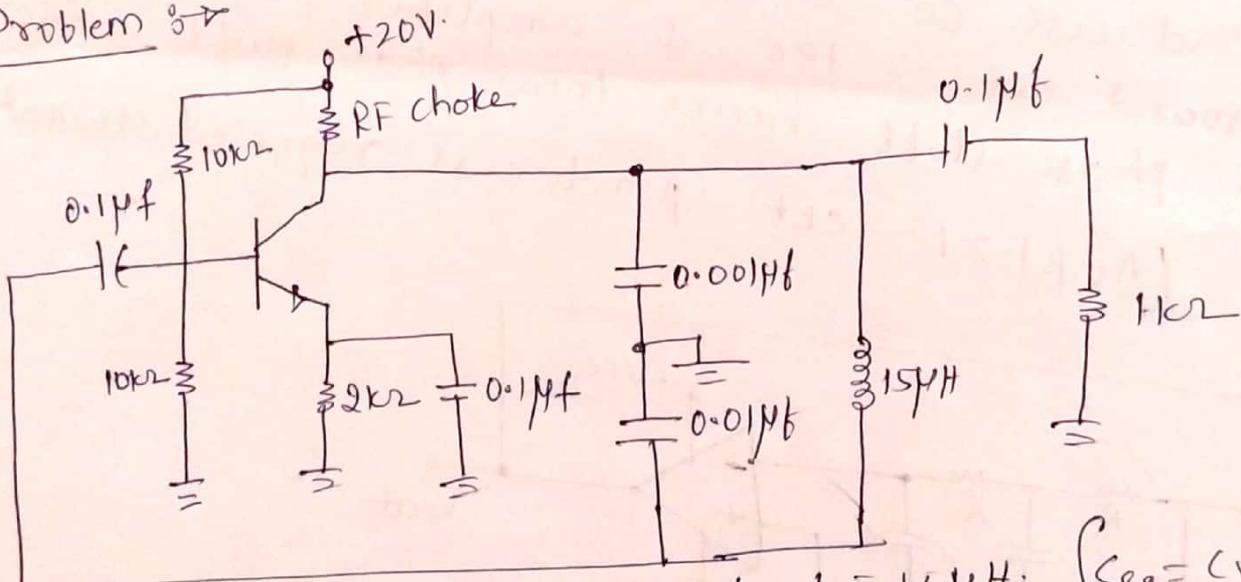

Given  $C_1 = 0.001\mu F$ ,  $C_2 = 0.01\mu F$ ,  $L = 15\mu H$ .  $\left\{ C_{eq} = \frac{C_1 C_2}{C_1 + C_2} = 909\text{pF} \right.$

$$f_r = \frac{1}{2\pi\sqrt{(15\mu H)(909\text{pF})}} = 1.36\text{MHz}$$

$$B = \frac{C_1}{C_2} = \frac{0.001 \times 10^{-6}}{0.01 \times 10^{-6}} = 0.1$$

$$A_V(\text{min}) = \frac{0.01 \times 10^{-6}}{0.001 \times 10^{-6}} = 10$$

Barkhausen criterion or The condition for Sustained Oscillations is derived from German scientist Barkhausen hence it is called as Barkhausen criterion.

Let consider a inverting amplifier circuit with an open loop gain  $A$ . As the amplifier is inverting it produces a phase shift of  $180^\circ$  between input & output.

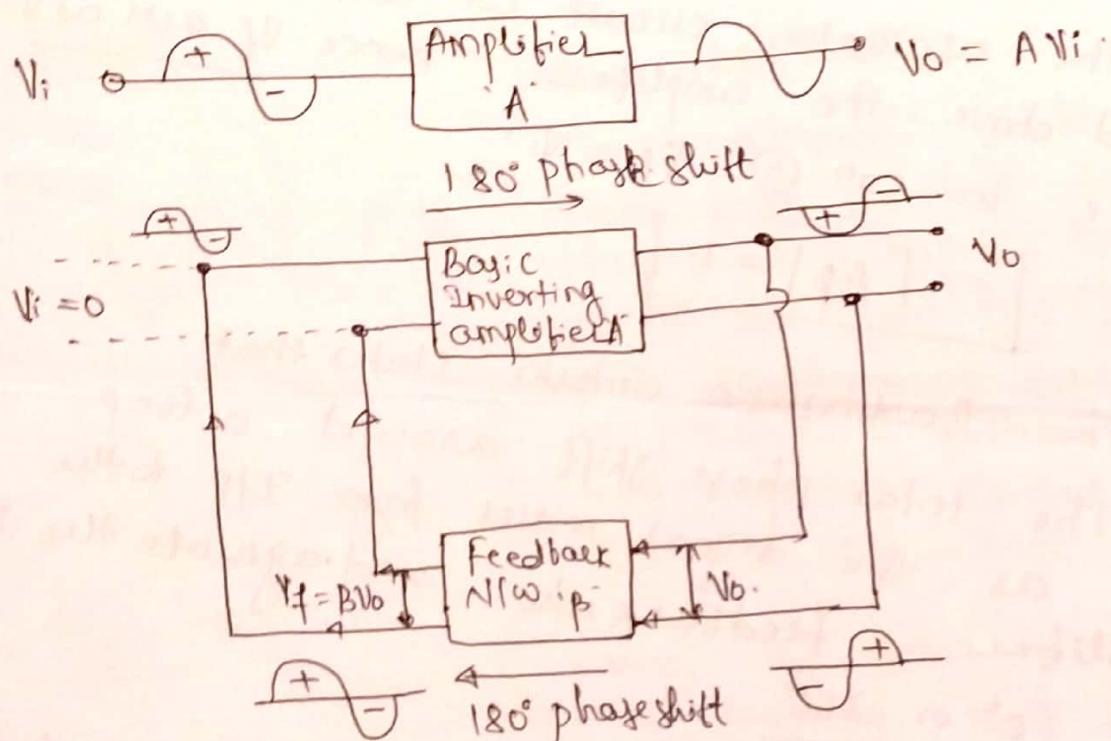


fig: Basic block diagram of oscillator circuit

- In the above fig. the feedback used is the feed back - i.e. the output voltage is in phase with input voltage.
- As here we are using the inverting amplifier then it produces the phase shift of  $180^\circ$  and the feedback  $Nlw$  introduce a phase shift of  $180^\circ$  so that the phase shift around a loop is  $360^\circ$ .

Let consider a input voltage  $V_i$  is applied at the input of amplifier

$$V_o = A V_i \quad \text{--- ①}$$

The feedback voltage  $V_f$  is given by

$$V_f = \beta V_o \quad \text{--- ②}$$

put eqn ① in ②

$$V_f = \beta A V_i \quad \text{--- ③}$$

For the oscillator circuit we want that feedback should drive the amplifier hence  $V_f$  acts as  $V_i$

hence in eqn ③  $V_f = V_i$ .

$$\boxed{\therefore |A\beta| = 1.}$$

→ The Barkhausen criteria states that


- ① The total phase shift around a loop i.e. as the signal moves from I/P to the amplifier, feedback N/w and again to the I/P is  $0^\circ$  or  $360^\circ$ .

- ② The magnitude of the product of open loop gain of amplifier ( $A$ ) & the magnitude of the feedback factor  $\beta$  is unity  $|A\beta| = 1$ .

By satisfying these conditions the circuit works as an oscillator by producing the sustained oscillations of constant amplitude & frequency.

## Different cases of $|AB|$

①  $|AB| > 1$  :-

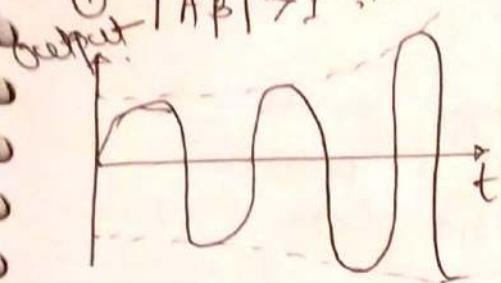


when the total phase-shift around a loop is  $0^\circ$  or  $360^\circ$  and  $|AB| > 1$  then it produces output oscillates & the oscillations are of growing type. i.e. the amplitude of oscillations are growing.

when  $|AB| = 1$  :-

The Barkhausen criterion states that when total phase shift around a loop is  $0^\circ$  or  $360^\circ$  and having a file feedback &  $|AB| = 1$  then it produces a constant frequency and amplitude called as sustained oscillations.


②  $|AB| < 1$

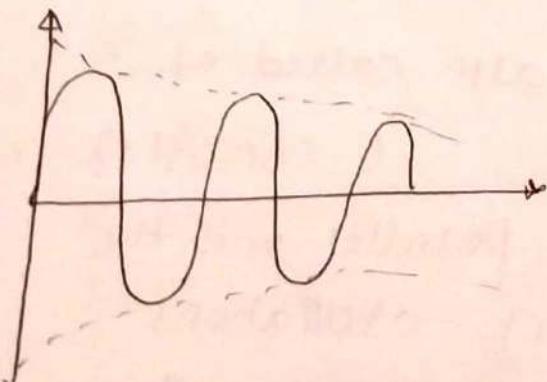

when the total phase shift around loop is  $0^\circ$  or  $360^\circ$  but  $|AB| < 1$  then the oscillations are decaying type i.e. the amplitude decreases exponentially and oscillations finally cease. so that the circuit works as amplifier without oscillations.

Q
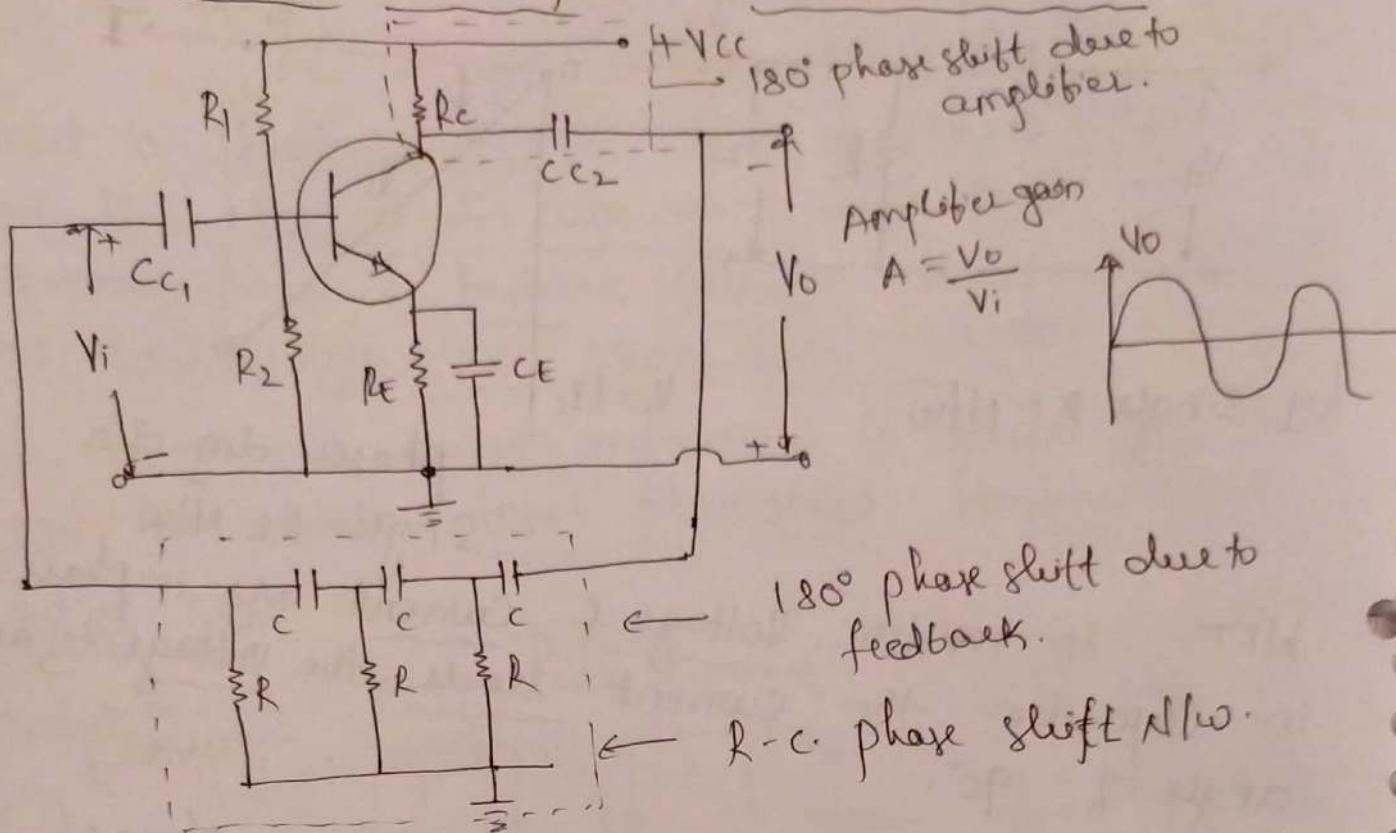
## Transistorized RC phase shift oscillator circuit



- In this circuit a transistor used as active element of amplifier stage.
- Here this circuit consist of the common emitter (CE) amplifier transistor as amplifier and feedback N/w consisting of capacitor and resistors.
- CE :→ If IP is applied b/w the base & emitter and o/p is taken b/w emitter & collector is called as CE circuit.
- The resistor  $R_1, R_2$ , &  $R_E$  provides a necessary bias to the circuit, and capacitor  $CC_1$  &  $CC_2$  are Coupling capacitor.
- The feedback N/w consist of the three RC sections, each R-C section produces a phase-shift of  $60^\circ$  to get a total phase shift of  $180^\circ$  we are using the three RC N/w's

→ In the RC phase shift oscillator the CE produces a phase shift of  $180^\circ$  and the RC NW produces a phase shift of  $180^\circ$  hence the total phase shift around the loop is  $360^\circ$  this satisfies the required condition for +ve feedback.

→ when feedback is adjusted such that  $|A_f| = 1$  the ckt works as oscillator.

The frequency of RC phase shift oscillator is given by

$$f = \frac{1}{2\pi RC \sqrt{6+4k}}$$

$$\text{where } k = \frac{RC}{R}$$

for the most of practical ckt the freq. of ckt can be calculated as

$$f = \frac{1}{2\pi \sqrt{6} R C}$$

The current gain ' $h_{fe}$ ' of the transistor must satisfy the condition

$$h_{fe} > 4k + 23 + \frac{29}{k}$$

Advantages :-



- The ckt is simple to design.
- ckt produces a sinusoidal output waveform.
- It is a fixed freq. oscillator

Disadvantages:-

- It is a fixed freq. oscillator.
- frequency stability is poor.
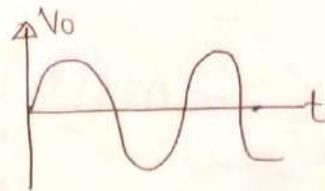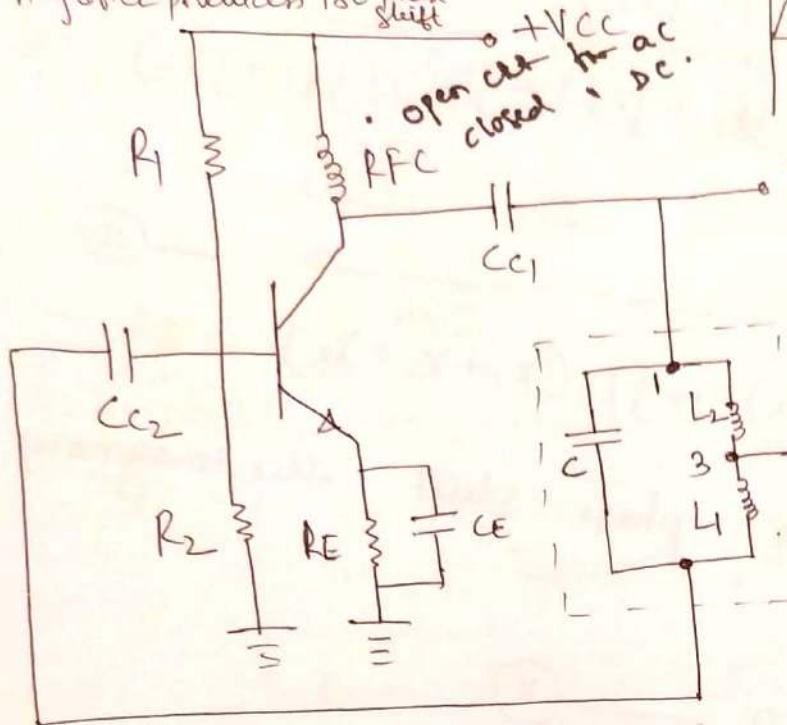
## Hartley Oscillator

Amplifier produces  $180^\circ$  phase shift



Tank ckt adds  
 $180^\circ$  phase shift.

→ Hartley oscillator ckt is a oscillator ckt which uses the two inductors and one capacitor in its tank ckt

→ The inductors  $L_1$  &  $L_2$  are connected in series and connected in parallel with 'C'. to complete a tank ckt.

→ The resistor  $R_1$ ,  $R_2$  &  $RE$  provides a necessary bias to the circuit. and capacitor  $C_{c1}$  &  $C_{c2}$  are Coupling capacitors.


→ Here the feedback ckt consist of the tank circuit made up of two inductor  $L_1$  &  $L_2$  and capacitor

→ It consist of radio frequency choke as a large inductor the main function of RFC is that it acts as open ckt for AC supply & closed ckt for DC supply.

- The main function of the RFC is to achieve the isolation b/w AC & DC condition.
- Here CE amplifier ckt produces a phase shift of  $180^\circ$  and tank ckt i.e. feedback ckt produces a phase shift of  $180^\circ$  hence net total phase shift around ckt is  $360^\circ$  or  $0^\circ$ .
- The feedback is adjusted in such a way that  $|A_f| = 1$ , then ckt works as oscillator ckt

oscillation in Hartley oscillator

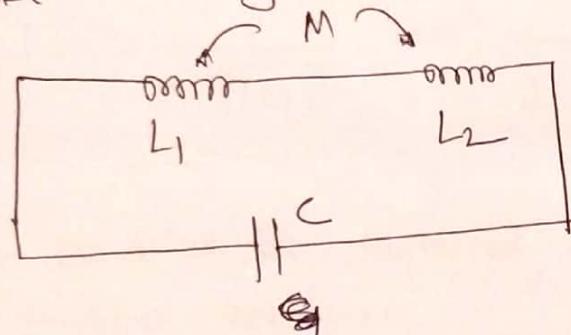Derivation for freq. of  
ckt is given by



In feedback ckt sum of all the 3 reactances must be equal to zero.

$$jX_{L_1} + jX_{L_2} + \frac{1}{jX_C} = 0$$

$$jX_{L_1} + jX_{L_2} - jX_C = 0$$

$$\sqrt{[X_{L_1} + X_{L_2}]} = \sqrt{X_C}$$

$$\omega_{L_1} + \omega_{L_2} = \frac{1}{\omega_C}$$

$$\omega [L_1 + L_2] = \frac{1}{\omega_C}$$

$$\omega^2 = \frac{1}{(L_1 + L_2)C}$$

$$\omega = \frac{1}{\sqrt{L_{eq}C}}$$

where  $L_{eq} = L_1 + L_2$

$$2\pi f = \frac{1}{2\pi\sqrt{L_{eq}C}} \Rightarrow$$

$$f = \frac{1}{2\pi\sqrt{L_{eq}C}}$$

The mutual Inductance is ~~considered~~ considered while determining the equivalent Inductance

$$L_{eq} = L_1 + L_2 + 2M.$$

→ The condition for sustained oscillation is given by

$$h_{fe} \geq \frac{L_1 + M}{L_2 + M}.$$

Neglecting mutual Inductance then

$$h_{fe} \geq \frac{L_1}{L_2}$$

Formulae

①  $f = \frac{1}{2\pi \sqrt{L_{eq} C}}$

$$L_{eq} = L_1 + L_2 + 2M$$

when  $M = 0$ .

$$L_{eq} = L_1 + L_2$$

② Condition for Sustained oscillation is given by

$$h_{fe} > \frac{L_1}{L_2}$$

- ① The following circuit parameter values are given for the Hartley oscillator  $L_1 = 750 \mu H$ ,  $L_2 = 750 \mu H$ ,  $M = 150 \mu H$
- ~~C<sub>1</sub>~~  $C_1 = 150 pF$ , ~~C<sub>2</sub>~~  $C_2 = 100 pF$ ,  $h_{fe} = 50$
- ② calculate the freq. of oscillations.
- ③ check to make sure that the condition for oscillation is satisfied.

SOP :  $h_{ikt}$   $f = \frac{1}{2\pi\sqrt{L_{eq}C}}$

$$L_{eq} = L_1 + L_2 + 2M$$

$$L_{eq} = 750 \mu H + 750 \mu H + 2(150 \times 10^{-6})$$

$$L_{eq} = 1800 \mu H$$

$$f = \frac{1}{2\pi\sqrt{L_{eq}C}} = \frac{1}{2\pi\sqrt{(1800 \mu H) \times 150 \times 10^{-9}}} = 306.25 \text{ kHz}$$

- ④ condition for sustained oscillation by considering the mutual inductance.

$$h_{fe} \geq \frac{L_1 + M}{L_2 + M}$$

$$h_{fe} \geq \frac{750 \times 10^{-6} + 150 \times 10^{-6}}{750 \times 10^{-6} + 150 \times 10^{-6}}$$

$$h_{fe} \geq 1$$

$h_{ikt} h_{fe} = 50$  > 1, hence the circuit oscillates  
here  $h_{fe}(50) > 1$ .

② In a transistor hartley oscillator,  $L_1 = 10 \mu H$ ,  $L_2 = 10 \mu H$  find the value of 'C' required for an oscillating freq. of 150 kHz.

SOP :-  $L_1 = 10 \mu H$ ,  $L_2 = 10 \mu H$   $f = 150 \text{ kHz}$ ,  $C = ?$

$$f = \frac{1}{2\pi\sqrt{L_{eq}C}}$$

$$L_{eq} = L_1 + L_2 + 2M. \quad \left\{ \begin{array}{l} \text{here } M \text{ is not given hence} \\ M=0 \end{array} \right\}$$

$$L_{eq} = 20 \mu H$$

$$\therefore f = \frac{1}{2\pi\sqrt{L_{eq}C}}$$

$$f^2 = \frac{1}{4\pi^2 (L_{eq}C)^2}$$

$$f^2 = \frac{1}{4\pi^2 L_{eq}C} = \frac{1}{4\pi^2 \times 20 \times 10^{-6} \times f^2}$$

$$C = \frac{1}{4\pi^2 \times 20 \times 10^{-6} \times (150 \times 10^3)^2}$$

$C = 56.28 \text{ nF}$

① In a ckt. two inductances  $L_1 = 30 \mu H$ ,  $L_2 = 21 \mu H$ . & mutual inductance is  $150 \mu H$ . and frequency of the ckt is  $\rightarrow 200 \text{ kHz}$  find value of C.

## Colpitts Oscillator

→ Amplifier produces a  $180^\circ$  phase-shift

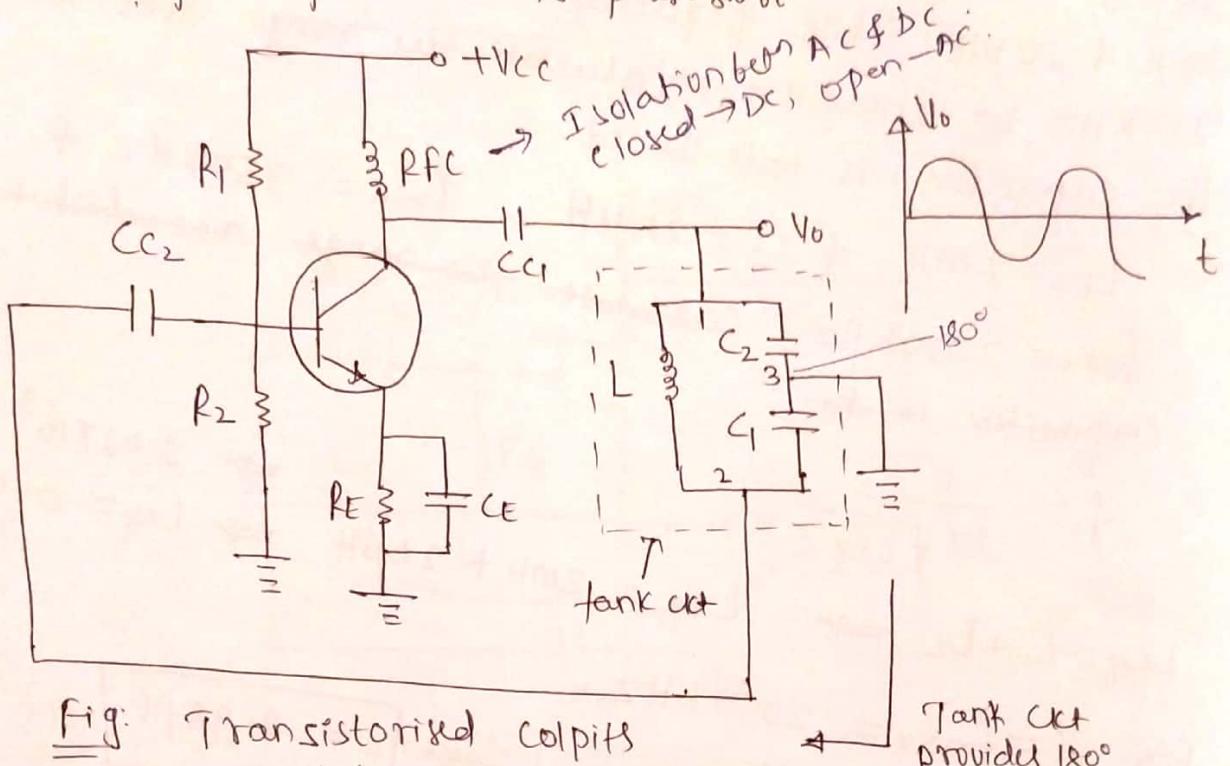


Fig: Transistorised Colpitts oscillator.

Tank ckt provides  $180^\circ$  phase-shift.

"The oscillator circuit, in which tank circuit consist of a two capacitors  $C_1$  &  $C_2$  are in series, and also it consist of Inductor 'L' which is in parallel with two capacitors  $C_1$  &  $C_2$ ".

→ The resistor "R<sub>1</sub>, R<sub>2</sub> & R<sub>E</sub>" provides a necessary bias to the circuit and "R<sub>E</sub>" performs the dual function i.e. it acts as emitter resistance & as well as the Colpitts oscillator component.

→ Here the capacitor C<sub>C1</sub> & C<sub>C2</sub> are coupling capacitors

→ The "Radio frequency choke" is used to achieve the isolation b/w AC & DC conditions.

④ The RFC allows the dc current to pass through it easily i.e. acts as a short circuit for the d.c. current.

⑤ Acts as open ckt for the A.C. current.

→ when the switch is ON then the current flows in the tank circuit and produces a voltage across  $C_1$  &  $C_2$ . i.e. Tank circuit provides a  $180^\circ$  of phase shift & CE amplifier provides a phase shift of  $180^\circ$  hence the total phase shift around the ckt is  $360^\circ$ .

→ and when the feedback is adjusted such that  $|A_{PL}| = 1$  then the ckt works as oscillator. The o/p of the ckt is coupled to the load through a transformer.

The transformer coupling has following advantages

- ① It provides an electrical oscillations b/w the oscillator o/p & the load.
- ② It provides an impedance matching b/w oscillator o/p & load

The frequency of oscillation is given by

$$f = \frac{1}{2\pi\sqrt{LC_{eq}}}$$

$$\text{where } C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

The condition for sustained oscillation is given by

$$h_{fe} \geq \frac{C_2}{C_1}$$

Formulas:-

$$f = \frac{1}{2\pi\sqrt{LC_{eq}}}$$


$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$h_{fe} > C_2/C_1$$

This document is available free of charge on



## Derivation for Colpits oscillator

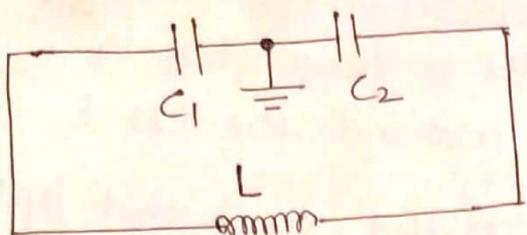

The sum of all three reactances must be equal to zero.

$$\frac{1}{jX_C_1} + \frac{1}{jX_C_2} + jXL = 0$$

$$-jX_C_1 - jX_C_2 + jXL = 0$$

$$jXL = jX_C_1 + jX_C_2$$

$$XL = X_C_1 + X_C_2$$

$$\omega_L = \frac{1}{\omega_C_1} + \frac{1}{\omega_C_2}$$

$$\omega_L = \frac{1}{\omega} \left[ \frac{1}{C_1} + \frac{1}{C_2} \right]$$

$$\omega^2 = \frac{1}{L} \left[ \frac{1}{C_1} + \frac{1}{C_2} \right]$$


$$\omega^2 = \frac{1}{L} \left[ \frac{C_1 + C_2}{C_1 C_2} \right] \Rightarrow \omega^2 = \frac{C_1 + C_2}{L[C_1 C_2]}$$

$$(2\pi f)^2 = \frac{1}{L \left[ \frac{C_1 C_2}{C_1 + C_2} \right]}$$

$$(2\pi f)^2 = \frac{1}{L C_{eq}} \quad \therefore C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$2\pi f = \frac{1}{\sqrt{L C_{eq}}}$$

$$f = \frac{1}{2\pi \sqrt{L C_{eq}}}$$

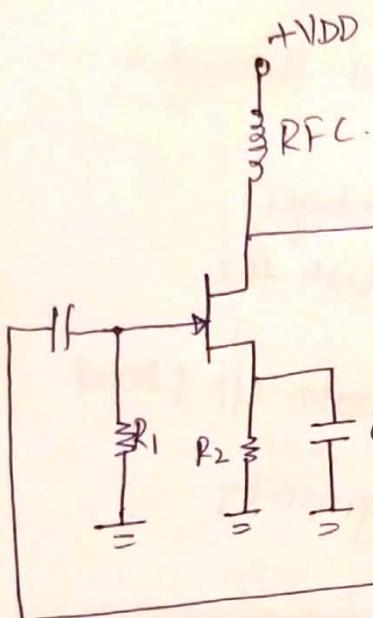

FET Colpits oscillator.

$$C_{eq} = \frac{C_1 + C_2}{L[C_1 C_2]}$$

$$\omega^2 = \frac{1}{L \left[ \frac{C_1 C_2}{C_1 + C_2} \right]}$$

① The following data are available for the Colpits oscillator  $C_1 = 1\text{nf}$ ,  $C_2 = 99\text{nF}$ ,  $L = 1.5\text{mH}$

$L_{RFC} = 0.5\text{mH}$ ,  $C_c = 10\mu\text{f}$ ,  $h_{fe} = 110$

① calculate the freq. of oscillation.

② check to make sure that the condition for oscillation is satisfied.

$C_1 = 1\text{nf}$ ,  $C_2 = 99\text{nF}$ ,  $L = 1.5\text{mH}$ , &  $h_{fe} = 110$ .

$$\text{WKT } C_{eq} = \frac{C_1 C_2}{C_1 + C_2} = \frac{(1 \times 10^{-9}) \times (99 \times 10^{-9})}{(1 \times 10^{-9}) + 99 \times 10^{-9}} = 0.99\text{nF}$$

$$f = \frac{1}{2\pi\sqrt{LC_{eq}}} = \frac{1}{2\pi\sqrt{(1.5 \times 10^{-3}) \times (0.99 \times 10^{-9})}}$$

$$\boxed{f = 130.6\text{kHz}}$$

⑥ condition for sustained oscillation is

$$h_{fe} = \frac{C_2}{C_1}$$

$$\frac{110}{C_2} = \frac{99 \times f}{10^6}$$

$$\boxed{110 = 99}$$

∴ The circuit produces required oscillations.

⑦ In a transistor Colpits oscillator  $C_1 = 1\text{nf}$  &  $L$  for a freq. of 100kHz.

Given:  $C_2 = 100\text{nF}$  find the value of  $f = 100\text{kHz}$   $L = ?$

$$\text{WKT: } C_{eq} = \frac{C_1 C_2}{C_1 + C_2} = \frac{(1 \times 10^{-9}) \times (100 \times 10^{-9})}{(1 \times 10^{-9}) + (100 \times 10^{-9})} = 0.99\text{nF}$$

$$\text{WKT } f = \frac{1}{2\pi\sqrt{C_{eq}L}}$$

$$f^2 = \frac{1}{4\pi^2(C_{eq}L)^2} \Rightarrow L = \frac{1}{4\pi^2 f^2 C_{eq}} = \frac{1}{4\pi^2 \times (100\text{kHz})^2 \times (0.99 \times 10^{-9})}$$

$$L = 2.55\text{mH}$$

③ In a Colpits oscillator  $C_1 = C_2 = C$  &  $L = 100 \mu H$   
 The frequency of oscillation is 500kHz, Determine the  
 Value of 'C'.

SOP  $L = 100 \mu H, C_1 = C_2 = C, f = 500 \text{ kHz}$

$$\text{WKT} \quad f = \frac{1}{2\pi\sqrt{L \cdot C_{eq}}}$$

$$f^2 = \frac{1}{4\pi^2 (L \cdot C_{eq})^2} \Rightarrow C_{eq} = \frac{1}{4\pi^2 f^2 L}$$

$$C_{eq} = \frac{1}{4\pi^2 \times (500 \times 10^3)^2 \times 100 \times 10^{-6}} \Rightarrow 1$$

$$C_{eq} = 1.0132 \times 10^{-9} F$$

$$\text{but } C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$\text{Given: } C_1 = C_2 = C$$

$$\therefore C_{eq} = \frac{(C) \times (C)}{C + C} \Rightarrow \frac{C^2}{2C}$$

$$C_{eq} = \frac{C}{2}$$

$$C = 2C_{eq} \Rightarrow C = 2 \times 1.0132 \times 10^{-9}$$

$$C = 2.026 \text{ nF}$$

④ Find the frequency of oscillations of transistorised  
 Colpits oscillator having tank circuit parameters as  
 $C_1 = 150 \text{ pF}, C_2 = 1.5 \text{ nF}$ , &  $L = 150 \mu H$

$$136.363 \times 10^{12} \text{ F}$$

SOP  $C_{eq} = \frac{C_1 C_2}{C_1 + C_2} \Rightarrow$

$$f = \frac{1}{2\pi\sqrt{L C_{eq}}} \Rightarrow f = \frac{1}{2\pi\sqrt{(150 \times 10^{-6}) \times (136.363 \times 10^{-12})}}$$

$$f = 1.927 \text{ MHz}$$

## Crystal oscillator

"The ckt in which the tank ckt is replaced by using crystal for the purpose of frequency stability". It employs the piezo-electric effect of a crystal.

Piezo electric effect :- The crystals of certain materials like quartz, rock salt etc are having a property of generating the alternating voltage between pair of opposite faces when an alternating pressure is applied ~~on~~ on the other pair of faces perpendicular to the first pair

→ "i.e when an voltage is applied across the one face then another face starts to vibrate"

The oscillatory frequency of crystal depends on the thickness of crystal.

$$f \propto \frac{1}{\text{thickness of crystal}}$$

→ The Quartz crystals are most commonly used in the crystal oscillators because of it is a tough and stable material and it is inexpensive and easily available in Nature.

→ Crystal oscillators generates a frequency in the range of 50KHz to 50MHz.

## Construction details


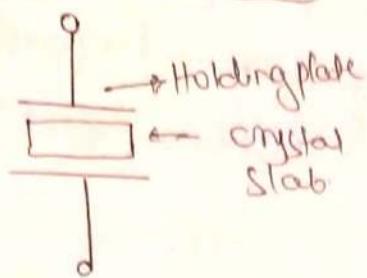


Fig. Symbolic representation of crystal.

The Natural shape of the Quartz crystal is the hexagonal prism but for practical use it is cut into the rectangular slab.

→ The rectangular slab is held betw two metallic plates called as holding plates.

## A.C. equivalent ckt

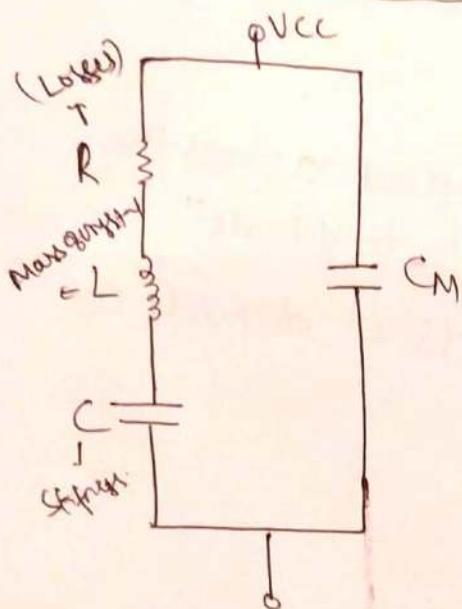

When the crystal is not vibrating, it is equivalent to capacitance due to mechanical mounting of crystal.

→ Here the two metallic plates are separated by dielectric material i.e. crystal slab is called as mounting capacitance 'C<sub>M</sub>'.

→ When the crystal is vibrating then the internal fractional losses are denoted by 'R'.

→ the mass of the crystal is represented by inductor 'L'.

→ In the vibrating condition it is having some stiffness it is represented by 'C'

The RLC forms a resonating ckt

$$f_r = \frac{1}{2\pi\sqrt{LC}} \sqrt{\frac{\theta^2}{1+\theta^2}}$$

where  $\Omega$  is quality factor of crystal.

$$\Omega = \frac{\omega L}{R}$$

$\Omega$  factor of crystal is very high i.e from 20,000 to  $10^6$   $\therefore \sqrt{\frac{\Omega^2}{1+\Omega^2}} = \text{unity}$

$$\therefore f_r = \frac{1}{2\pi\sqrt{LC}}$$

The crystal freq. is inversely proportional to the thickness of crystal.

$$f \propto \frac{1}{T}$$

#### ④ Frequency Response of crystal series Resonance

##### ① Series Resonance

When the frequency of A.C.

source (<sup>(eff)</sup>) is equal to the

frequency "f<sub>s</sub>" then the


current through the crystal

becomes maximum "I<sub>max</sub>"

this condition is called as "series Resonance" & "f<sub>s</sub>"

is called as the series resonant frequency.

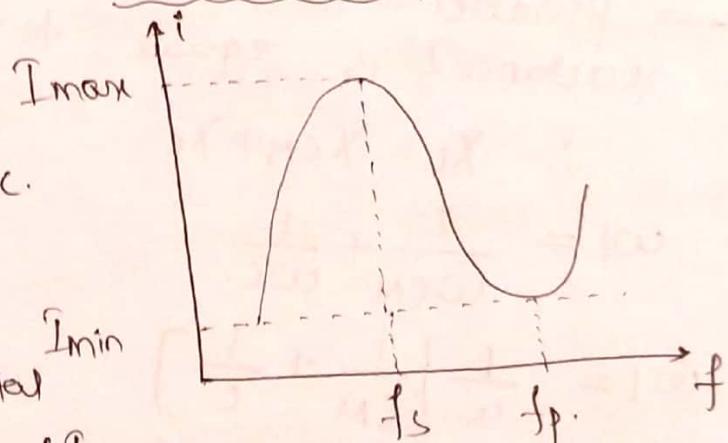The series resonance occurs when the reactance of 'L' is equal to the reactance of 'C' in series 'FLC' Branch



$$\text{i.e } X_L = X_C$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{LC}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$\therefore f = \boxed{\frac{1}{2\pi\sqrt{LC}}}$$

Note:- since the current is maximum, the impedance of the crystal is minimum.

### parallel resonance

when the frequency of A.C. source is equal to frequency "f<sub>p</sub> > f<sub>s</sub>" then the current through the crystal becomes minimum "I<sub>min</sub>" this condition is called parallel resonance & "f<sub>p</sub>" is called as parallel resonant frequency.

→ parallel resonance occurs when the inductive reactance 'L' is equal to the

capacitive ~~reactance~~ <sup>reactance</sup> ~~inductance~~

$$\therefore X_L = X_{CM} + X_C$$

$$\omega L = \frac{1}{\omega_{CM}} + \frac{1}{\omega C}$$

$$\omega L = \frac{1}{\omega} \left[ \frac{1}{CM} + \frac{1}{C} \right]$$

$$\omega^2 = \frac{1}{L} \left[ \frac{C + CM}{CM C} \right]$$

$$\omega^2 = \frac{1}{L \left[ \frac{CM C}{C + CM} \right]}$$

$$\omega^2 = \frac{1}{L C_p} \quad \left\{ C_p = \frac{CM C}{C + CM} \right\}$$

$$2\pi f = \frac{1}{\sqrt{L C_p}}$$

$$f = \frac{1}{2\pi\sqrt{L C_p}}$$

$$\therefore f = f_p = \frac{1}{2\pi\sqrt{L C_p}}$$

∴ when the current is minimum, the impedance of crystal is maximum.

A crystal has the following parameters  
 $C = 0.05 \text{ pF}$ ,  $R = 2 \text{ k}\Omega$ ,  $C_M = 10 \text{ pF}$  what are the  
series & parallel resonant freq. of crystal.

$\therefore f_s = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{3 \times 0.05 \times 10^{-12}}} = 410.931 \text{ kHz}$

$$f_p = \frac{1}{2\pi\sqrt{LC_p}}$$

$$C_p = \frac{C_m C_o}{C + C_m} = \frac{10 \times 10^{12} \times 0.05 \times 10^{-12}}{10 \times 10^{12} + 0.05 \times 10^{-12}} = \frac{5 \times 10^{25}}{1.005 \times 10^{14}}$$

$$C_p = 4.975 \times 10^{14}$$

$$\boxed{C_p = 0.0497 \times 10^{12}}$$

$$f_p = \frac{1}{2\pi\sqrt{3 \times 0.0497 \times 10^{12}}} \Rightarrow$$

$$f_p = \frac{1}{2\pi \times 3.863 \times 10^7}$$

$$\boxed{f_p = 411.962 \text{ kHz}}$$

A crystal oscillator circuit  $L = 0.4 \text{ H}$ ,  $C = 0.085 \text{ pF}$ ,  
 $C_M = 1 \text{ pF}$  with  $R = 5 \text{ k}\Omega$  find.

@ series & parallel resonant freq.

⑥ By what factor does the parallel resonant frequency exceeds the series resonant freq?

⑦ find Q factor of circuit

## The 555 Timer

The NE555, LM555 & CA555 are widely used IC timer. It is operated in two modes

### Monostable or Astable

- In monostable it can produce time delay from microseconds to hours.
- In astable mode it can produce rectangular waves with a variable duty cycle.

### Monostable operation

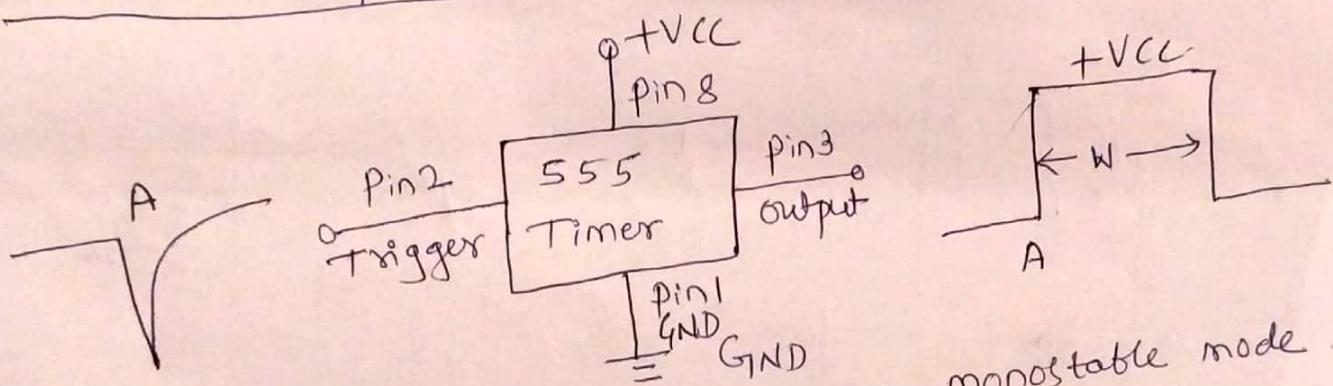


Fig. The 555 timer used in monostable mode.

- Initially 555 timer has low output voltage at which it can remain indefinitely.
- When 555 timer receives a trigger at point A in time, the output voltage switches from low to high.
- The output remains high for some period & then returns to low state after time delay of W.
- Output is in low state until it gets another trigger

— A manufacturer is in this Smith's  
that had been one of their Shaw's to him,  
when the Shaw's have sold the Shaw's ~~Shaw's~~  
to the Smith's all Shaw's will.  
— It's also called as you that manufacturer.

Module 1Assignment Questions.

- ① With a neat ckt diagram explain summing ckt & Averager circuit.
- ② With a ckt diagram & necessary equations explain Binary weighted D/A converter.
- ③ With a neat diagram explain inverting comparator ckt. & comparator with nonzero reference.
- ④ Explain INV Schmitt trigger & NINV Schmitt trigger.
- ⑤ With a neat diagram explain Barkhausen criteria ~~for~~
- ⑥ With a neat diagram explain theory of sinusoidal oscillation - Weinbridge oscillator with lead & lag N/W
- ⑦ With a neat ckt diagram explain Twin-T - oscillator
- ⑧ With a neat ckt diagram & necessary equations explain Hartely & Colpits oscillator. & crystal oscillator.
- ⑨ With a functional diagram explain 555 timer used a monostable & Astable multivibrator.