

MODULE 3


TRANSIENT BEHAVIOR AND INITIAL CONDITIONS

A network in which branch current & node voltages are not changing w.r.t. time is said to be in steady state.

- Even if the voltages & currents in the ckt. have constant amplitude & frequency throughout the time interval it is said to be steady state.
- The time interval required for a ckt. to switch from one condition to another by changing applied voltage (or) by changing branch currents & voltages from one value to new value is called transition period.
- The response (or) o/p. of n/w. during transition period is called transient response of n/w.
- If the n/w. condition is not disturbed after transition period, then the n/w. attains steady state at infinite time.

* Initial & final conditions in elements :-

i) The inductor :-

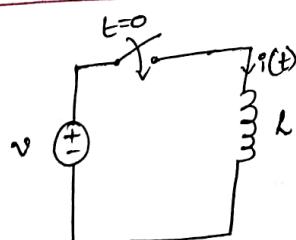

The switch is closed at $t=0$. Hence $t=0^-$ corresponds to the instant when the switch is just open & $t=0^+$ corresponds to the instant when the switch is just closed.

∴ The current through inductor is,

$$i = \frac{1}{L} \int_{-\infty}^t v dt$$

$$i = \frac{1}{L} \int_{-\infty}^0 v \, dc + \frac{1}{L} \int_0^t v \, dc$$

$$i(0) = i(0^-) + \frac{1}{L} \int_0^t v \, dc$$

put $t=0^+$ on both sides, we get

$$i(0^+) = i(0^-) + \frac{1}{L} \int_{0^-}^{0^+} v \, dc$$

$$\boxed{i(0^+) = i(0^-)}$$

From above eqn. it is clear that the current in an inductor cannot change instantaneously.

* If $i(0^-) = 0$, then $i(0^+) = 0$. This means at $t=0^+$, inductor acts as an open circuit, irrespective of the voltage across terminals.

* If $i(0^-) = I_0$, then $i(0^+) = I_0$, then the inductor can be thought of as a current source of I_0 A. The equivalent ckt. is shown below.



Equivalent ckt. at $t=0^+$



The initial condition equivalent ckt. of an inductor

The final condition equivalent ckt. of an inductor is derived from basic relationship,



$$v = L \frac{di}{dt}$$

Under steady state condition, $\frac{di}{dt} = 0$.

$$\therefore v = 0$$


Hence 'L' acts as short ckt. at $t = \infty$ [final or steady state]

Equivalent ckt. at $t = \infty$

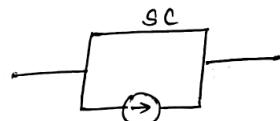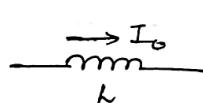

The final condition equivalent ckt. of an inductor

ii) The Capacitor :-

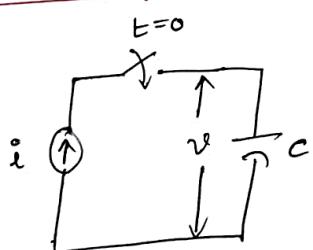

The voltage across capacitor is given by,

$$v = \frac{1}{C} \int_{-\infty}^t i \, dt$$

$$v(t) = \frac{1}{C} \int_{-\infty}^{0^-} i \, dt + \frac{1}{C} \int_{0^-}^t i \, dt$$

$$v(t) = v(0^-) + \frac{1}{C} \int_{0^-}^t i \, dt$$



At $t = 0^+$:

$$v(0^+) = v(0^-) + \frac{1}{C} \int_{0^-}^{0^+} i \, dt$$

$v(0^+) = v(0^-)$

\therefore Vtg. across a capacitor cannot change instantaneously

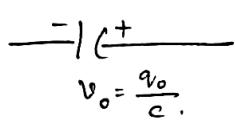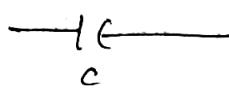- + If $v(0^-) = 0$, then $v(0^+) = 0$, then at $t=0^+$, capacitor acts as short ckt.
 - + If $v(0^-) = \frac{V_0}{C}$, then $v(0^+) = \frac{V_0}{C}$, then capacitor acts as voltage source of $\frac{V_0}{C}$ v.
- Equivalent ckt at $t=0^+$



Initial condition equivalent ckt's of a capacitor

\therefore The current through capacitor is given by,

$$i = C \frac{dv}{dt}$$




Under steady state condition,

$$\frac{dv}{dt} = 0$$

\therefore At $t=\infty$, $i=0$

i.e. At $t=\infty$ (or) steady state, capacitor acts as an open ckt.

Equivalent ckt. at $t=\infty$

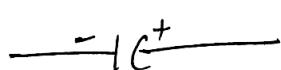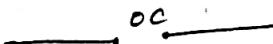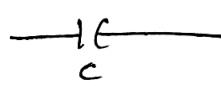

$$V_0 = \frac{V_0}{C}$$

Final condition equivalent ckt. of a capacitor

iii) The resistor :-

$$V = RI$$

Current through resistor will change instantaneously if voltage changes instantaneously. Similarly, voltage will change instantaneously if current changes instantaneously.

* Procedure for evaluating initial conditions:-

→ At first, the initial values of currents & voltages are found & then solve for the derivatives

→ For finding initial values of currents & voltages an equivalent n/w. of the original n/w. at $t=0^+$ is constructed using following rules:


1. Replace all inductors with open ckt. or with current sources having the value of current flowing at $t=0^+$

2. Replace all capacitors with short ckt. or with v.tg. sccs. of value $V_0 = \frac{q_0}{C}$ if there is an initial charge.

3. Resistors are left in the n/w. without any change.

1. Find $i_L(0^+)$ & $i_L(0^+)$. The ckt. is in steady state

for $t < 0$

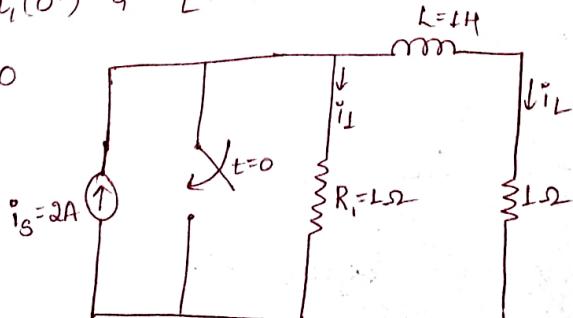

At $t = 0^+$:

$$0.15 \frac{dV_2(0^+)}{dt} + 0.05 \frac{d^2V_2(0^+)}{dt^2} = -0.1e^{-(0^+)} = -0.1$$

$$(0.15 \cdot 2) + 0.05 \frac{d^2V_2(0^+)}{dt^2} = -0.1$$

$$\therefore \boxed{\frac{d^2V_2(0^+)}{dt^2} = -8 \text{ V/sec}^2}$$

Diffr. (2) with 't'

$$0.15 \frac{d^2V_2}{dt^2} + 0.05 \frac{d^3V_2}{dt^3} = -0.1e^{-t}$$

At $t = 0^+$:

$$0.15 \frac{d^2V_2(0^+)}{dt^2} + 0.05 \frac{d^3V_2(0^+)}{dt^3} = 0.1e^{-(0^+)} = 0.1$$


$$0.15(-8) + 0.05 \frac{d^3V_2(0^+)}{dt^3} = 0.1$$

$$\boxed{\frac{d^3V_2(0^+)}{dt^3} = 26 \text{ V/sec}^3}$$



q. The circuit is in steady state with switch 'K' close.

✓ At $t = 0$, the switch is opened. Determine the vgs.

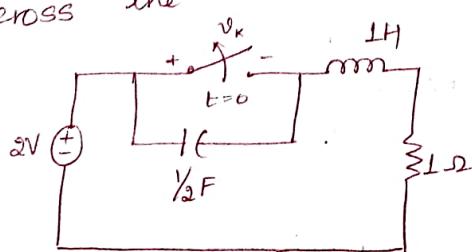across the switch v_K & $\frac{dv_K}{dt}$ at $t = 0^+$.



At $t = 0^+$: SW \Rightarrow open

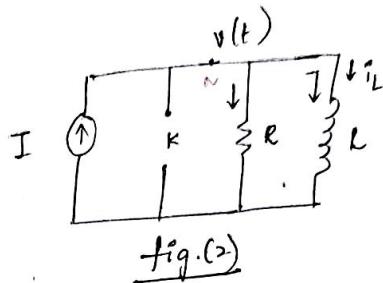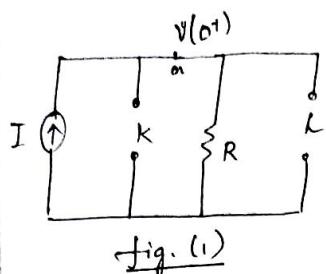


$$\therefore v(0^+) = I \times R = 2 \times 200$$

$$\boxed{v(0^+) = 400 \text{ V}}$$

At $t \geq 0^+$, KCL at 'a'
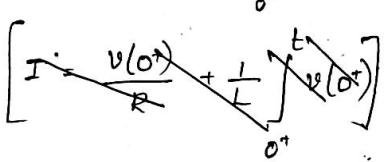
$$I = \frac{v(t)}{R} + \frac{1}{L} \int_{0^+}^t v(c) dc \rightarrow (1)$$



Diffr. (1) w.r.t 't'

$$0 = \frac{1}{R} \frac{dv}{dt} + \frac{1}{L} v(t) \rightarrow (2)$$

At $t = 0^+$,

$$0 = \frac{1}{R} \frac{dv(0^+)}{dt} + \frac{1}{L} v(0^+)$$

$$0 = \frac{1}{200} \cdot \frac{dv(0^+)}{dt} + \frac{400}{L}$$

$$\therefore \boxed{\frac{dv(0^+)}{dt} = 8 \times 10^4 \text{ V/sec.}}$$

Diffr. (2) w.r.t 't'

$$0 = \frac{1}{R} \frac{d^2v}{dt^2} + \frac{1}{L} \frac{dv}{dt}$$

At $t = 0^+$,


$$0 = \frac{1}{200} \cdot \frac{d^2v(0^+)}{dt^2} + \frac{1}{L} \cdot (8 \times 10^4)$$

$$\therefore \boxed{\frac{d^2v(0^+)}{dt^2} = 16 \times 10^6 \text{ V/sec}^2}$$

1 For the figure shown, (a) write the differential equation for the inductor current $i_L(t)$.

(b) Find $I_L(s)$ the Laplace transform of $i_L(t)$.

(c) Solve for $i_L(t)$

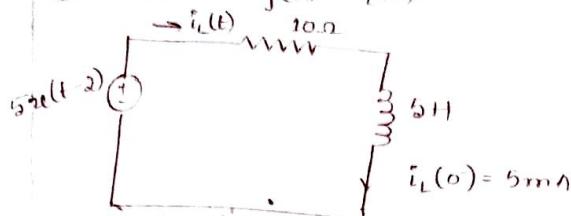

$$\Rightarrow \text{Apply KVL}, \quad 5u(t-2) - 10i_L(t) - 5 \frac{di_L(t)}{dt} = 0$$

$$\therefore 5u(t-2) = 10i_L(t) + 5 \frac{di_L(t)}{dt}$$

Apply L.T.

$$\frac{5e^{-2s}}{s} = 10I_L(s) + 5[sI_L(s) - i_L(0)] \quad u(t-2) \xrightarrow{\text{L.T.}} \frac{e^{-as}}{s}$$

$$\hookrightarrow = [10 + 5s] I_L(s) - 5i_L(0)$$

$$\frac{5e^{-2s}}{s} + 5 \times 5 \times 10^{-3} = (10 + 5s) I_L(s)$$

$$\therefore I_L(s) = \frac{\frac{5}{s} \left[e^{-2s} + 5 \times 10^{-3} s \right]}{5[s+2]} = \frac{e^{-2s} + 5 \times 10^{-3} s}{s(s+2)}$$

$$I_L(s) = \frac{e^{-2s}}{s(s+2)} + \frac{5 \times 10^{-3}}{s+2} = e^{-2s} \left[\frac{A}{s} + \frac{B}{s+2} \right] + \frac{5 \times 10^{-3}}{s+2}$$

$$\therefore 1 = A(s+2) + BS.$$

$$\text{Let } s=0; \quad 1 = A(2); \quad A = \frac{1}{2}$$


$$\text{Let } s=-2; \quad 1 = 0 + B(-2); \quad B = -\frac{1}{2}$$

$$\therefore I_L(s) = e^{-2s} \left[\frac{1/2}{s} - \frac{1/2}{s+2} \right] + \frac{5 \times 10^{-3}}{s+2}$$

Taking Inverse L.T.

$$i_L(t) = \frac{1}{2} u(t-2) - \frac{1}{2} e^{-2(t-2)} \cdot u(t-2) + 5 \times 10^{-3} e^{-2t} u(t)$$

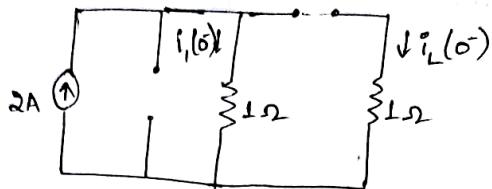At $t=0^-$; switch is open & ckt is in steady state & 'L' acts as short ckt



Using current division,

$$i_L(0^-) = \frac{1 \times 2}{1+1} = 1A,$$

Since the current in inductor will not change instantaneously,

$$i_L(0^-) = i_L(0^+) = 1A$$

At $t=0^+$, $i_L(0^+) = 2 - i_L(0^-)$

$$\Rightarrow = 2 - 1$$


$$i_L(0^+) = 1A$$

At $t=0^+$: switch is closed, the voltage drop across R_1 is zero.


$$\therefore i_L(0^+) = 0A$$

$\therefore i_L(0^+) = 0A; i_L(0^+) = 1A.$

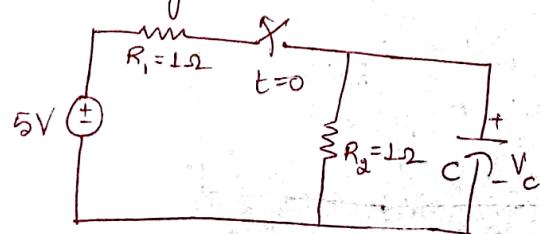2. Find $v_c(0^+)$. Assume that switch was in closed state for long time.



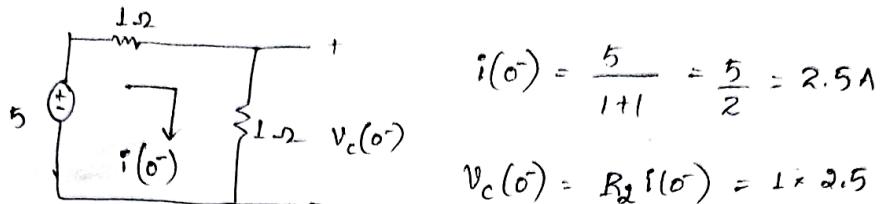⇒ Sol'n:- At $t=0^-$; switch is closed; G = open ckt




$$V_c(0^-) = 2.5 \text{ V}$$

Since voltage across capacitor will not change
instantaneously.

$$V_c(0^-) = V_c(0^+) = 2.5 \text{ V}$$

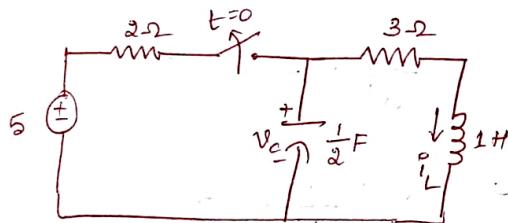3. Find $i_L(0^+)$ & $V_c(0^+)$. The ckt. is in steady state
with the switch in closed condition



⇒ Sol'n:- At $t=0^-$, switch is closed, G = open ckt
 L = short ckt




$$\therefore V_c(0^-) = \frac{3 \times 5}{2+3}$$

$$V_c(0^-) = 3 \text{ V}$$


$$\boxed{i_L(0^-) = i_L(0^+) = 1 \text{ A}}$$
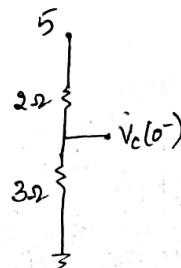
$$\boxed{V_c(0^-) = V_c(0^+) = 3 \text{ V.}}$$



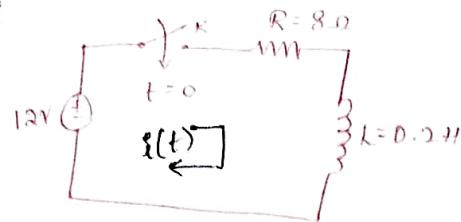4. In the given ckt. 'K' is closed at $t=0$ with zero current in the inductor. Find the values of

$i, \frac{di}{dt}, \frac{d^2i}{dt^2}$ at $t=0^+$. If $R=8\Omega$ & $L=0.2H$



→ Soln: At $t=0^-$, switch is open,

$$\therefore \boxed{i(0^-) = 0A = i(0^+)} \quad \{ \because \text{current through 'L'}. \}$$

At $t=0^+$, switch is closed.

$$8i + \frac{Ldi}{dt} = 12$$

$$8i + 0.2 \frac{di}{dt} = 12 \quad \rightarrow (1)$$

$$\text{At } t=0^+, \quad 8i(0^+) + 0.2 \frac{di(0^+)}{dt} = 12$$

$$0.2 \frac{di(0^+)}{dt} = 12 - 8i(0^+) \quad \Rightarrow 0$$

$$\frac{di(0^+)}{dt} = \frac{12}{0.2}$$

$$\therefore \boxed{\frac{di(0^+)}{dt} = 60 \text{ A/sec}}$$

Diffr. eqn. (1) w.r.t 't'

$$8 \frac{di}{dt} + 0.2 \frac{d^2i}{dt^2} = 0$$

$$\text{At } t=0^+: \quad 8 \frac{di(0^+)}{dt} + 0.2 \frac{d^2i(0^+)}{dt^2} = 0$$


$$0.2 \frac{d^2 i(0^+)}{dt^2} = -8 \times 60 = -480$$

$$\frac{d^2 i(0^+)}{dt^2} = \frac{-480}{0.2}$$

$$\boxed{\frac{d^2 i(0^+)}{dt^2} = -2400 \text{ A/sec}^2}$$

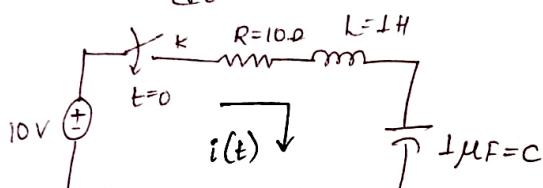5. In the n/w., the switch is closed at $t=0$, find

- ✓ 1. $\frac{di}{dt}$, $\frac{d^2 i}{dt^2}$ at $t=0^+$.



\Rightarrow Soln: At $t=0^-$; switch is open, $i(0^-)=0$ A = $i(0^+)$.

At $t=0^+$: switch is closed

$$10 = R i(t) + L \frac{di}{dt} + \frac{1}{C} \int_{0^+}^t i dt \rightarrow (1)$$

$$10 = 10i(t) + L \frac{di}{dt} + \frac{1}{10^{-6}} \int_{0^+}^t i dt$$

At $t=0^+$:

~~$$10 = 10i(0^+) + L \frac{di(0^+)}{dt} + 10^6 \int_{0^+}^t i(0^+) dt \approx 0$$~~

$$10 = \frac{di(0^+)}{dt}; \boxed{\frac{di(0^+)}{dt} = 10 \text{ A/sec}}$$

Diffr (1) wrt 't'

$$0 = R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{1}{C} i$$


At $t=0^+$.

$$R \frac{di(0^+)}{dt} + L \frac{d^2i(0^+)}{dt^2}, \frac{i(0^+)}{C} = 0$$


$$10 \cdot 10 + 1 \cdot \frac{d^2i(0^+)}{dt^2} = 0$$

$$\boxed{\frac{d^2i(0^+)}{dt^2} = -100 \text{ A/sec}^2}$$

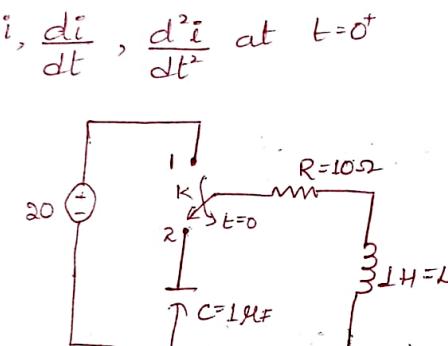6. The switch 'K' is changed from position 1 to position 2 at $t=0$. steady state condition having been reached at position 1. Find the values of $i, \frac{di}{dt}, \frac{d^2i}{dt^2}$ at $t=0^+$



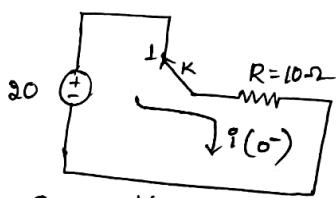→ Soln: At $t=0^-$: position 1 → steady state, $L = \text{short ckt}$, $C = \text{open ckt}$.





$$i(0^-) = \frac{20}{10} = 2 \text{ A}$$

$$\therefore \boxed{i(0^-) = i(0^+) = 2 \text{ A}}$$

Since there is no initial charge in the capacitor.

At $t=0^+$: position 2.
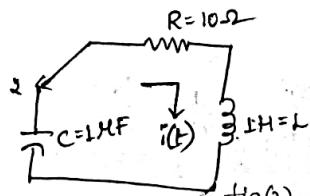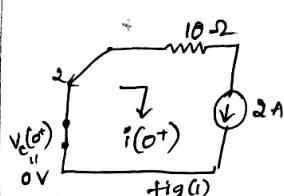
$$\boxed{v_c(0^-) = 0 \text{ V} = v_c(0^+)}$$



Apply KVL to fig.(i).

$$Ri(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int_{0^+}^t i(\tau) d\tau = 0 \rightarrow (1)$$

$$Ri(t) + L \frac{di(t)}{dt} + v_c(t) = 0 \rightarrow (2)$$

At $t=0^+$:

$$Ri(0^+) + L \frac{di(0^+)}{dt} + v_c(0^+) = 0.$$

$$10 \times 2 + 1 \cdot \frac{di(0^+)}{dt} = 0$$

$$\boxed{\frac{di(0^+)}{dt} = -20 \text{ A/sec.}}$$

Diff. eqn. (1) w.r.t. 't'

$$R \frac{di(t)}{dt} + L \frac{d^2i(t)}{dt^2} + \frac{1}{C} i(t) = 0$$

$$\text{At } t=0^+: R \frac{di(0^+)}{dt} + L \frac{d^2i(0^+)}{dt^2} + \frac{i(0^+)}{C} = 0$$

$$10 \times (-20) + 1 \times \frac{d^2i(0^+)}{dt^2} + \frac{2}{10^6} = 0$$


$$\therefore \boxed{\frac{d^2i(0^+)}{dt^2} = -2 \times 10^6 \text{ A/sec}^2}$$

✓ The switch is moved from position 1 to position 2 at $t=0$.


The steady state has been

reached before switching.

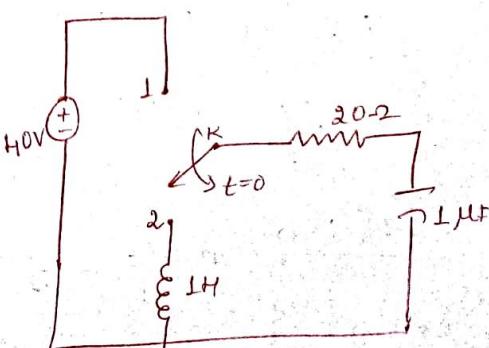Calculate i , $\frac{di}{dt}$ & $\frac{d^2i}{dt^2}$ at $t=0^+$



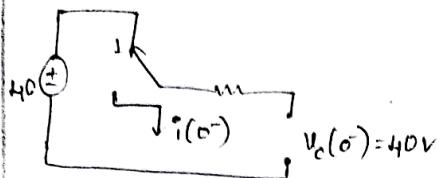\Rightarrow Soln: At $t=0^-$: switch \rightarrow position 1 \rightarrow steady state
 $L \rightarrow$ short ckt; $C \rightarrow$ open ckt.



$$\therefore \begin{cases} V_c(0^-) = 40V = V_c(0^+) \\ i(0^-) = 0A = i(0^+) \end{cases}$$

At $t \geq 0^+$: switch \rightarrow position 2

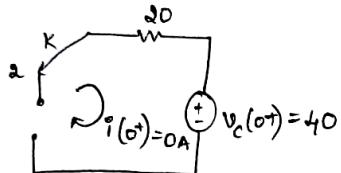


fig. (1)

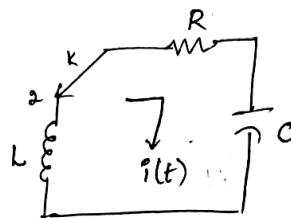


fig. (2)

Apply KVL to fig. (2).

$$Ri(t) + \frac{1}{C} \int_{0^+}^t i(t) dt + L \frac{di(t)}{dt} = 0 \rightarrow (1)$$

~~$$At \quad t=0^+: Ri(0^+) + V_c(0^+) + L \frac{di(0^+)}{dt} = 0$$~~

$$40 + 1 \cdot \frac{di(0^+)}{dt} = 0$$

$$\boxed{\frac{di(0^+)}{dt} = -40A/sec}$$

Dif. eqn. (1) w.r.t 't'

$$R \frac{di}{dt} + \frac{1}{C} i(t) + L \frac{d^2 i(t)}{dt^2} = 0$$


$$At \quad t=0^+: R \frac{di(0^+)}{dt} + \frac{1}{C} i(0^+) + L \frac{d^2 i(0^+)}{dt^2} = 0$$

$$20(-40) + 1 \cdot \frac{d^2 i(0^+)}{dt^2} = 0$$

$$\boxed{\frac{d^2 i(0^+)}{dt^2} = +800 \text{ A/sec}^2}$$

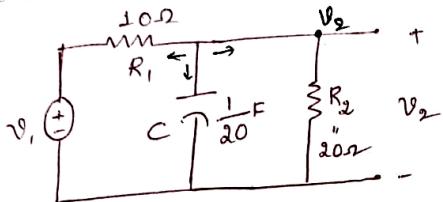* 8. In the w/o choice, $v_1(t) = e^t$ for $t \geq 0$ & zero for all uncharged.

✓ $t < 0$ If the capacitor is initially uncharged, determine the value of $\frac{d^2 v_2}{dt^2}$ & $\frac{d^3 v_2}{dt^3}$ at $t=0^+$.



\Rightarrow soln:- Since the capacitor is initially uncharged.

$$v_2(0^+) = 0.$$

Apply KCL.

$$\frac{v_2 - v_1}{R_1} + C \cdot \frac{dv_2}{dt} + \frac{v_2}{R_2} = 0.$$

$$\left[\frac{1}{R_1} + \frac{1}{R_2} \right] v_2 + C \frac{dv_2}{dt} = \frac{v_1}{R_1}$$

$$0.15v_2 + 0.05 \frac{dv_2}{dt} = 0.1e^{-t} \rightarrow (1)$$

$$\text{At } t=0^+: 0.15v_2(0^+) + 0.05 \frac{dv_2(0^+)}{dt} = 0.1e^{-(0^+)} = 0.1.$$


$$0.05 \frac{dv_2(0^+)}{dt} = 0.1$$

$$\therefore \boxed{\frac{dv_2(0^+)}{dt} = 2 \text{ V/sec}}$$

Diff. (1) w.r.t. 't'

$$0.15 \frac{dv_2}{dt} + 0.05 \frac{d^2 v_2}{dt^2} = -0.1e^{-t} \rightarrow (2)$$

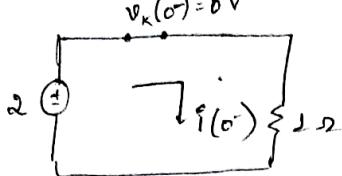
\Rightarrow solⁿ: At $t=0^-$: Switch \rightarrow closed \rightarrow steady state
 $L \rightarrow$ short ckt, $C \rightarrow$ open ckt



$$i(0^-) = \frac{2}{L} = 2A = i(0^+)$$

$$\therefore v_L(0^-) = 0V = v_L(0^+)$$

At $t=0^+$:

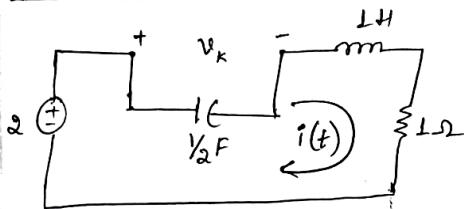

$$i_c(t) = C \cdot \frac{dv_K}{dt}$$

At $t=0^+$,

$$i_c(0^+) = C \cdot \frac{dv_K(0^+)}{dt}$$

$$0 = -v_K + L \frac{di}{dt} + I \cdot 2$$


$$0 = \frac{dV_K}{dt} + \frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt}$$

$$\frac{d}{dt} = \frac{dV_K(0^+)}{dt}$$

$$\therefore \frac{dV_K(0^+)}{dt} = \frac{2}{\frac{1}{2}} = 4V/\text{sec}$$

10. The switch 'K' is opened at $t=0$. At $t=0^+$ solve for the values of v , $\frac{dv}{dt}$ & $\frac{d^2v}{dt^2}$ if $I=2A$, $R=200\Omega$

$$L=1H$$

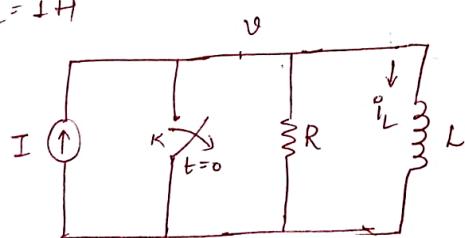


\Rightarrow solⁿ: At $t=0^-$: SW \rightarrow closed, $L \rightarrow$ short ckt.




$$\therefore i_L(0^-) = 0A = i_L(0^+)$$

- ii) In the circuit, a steady state is reached with switch 'K' open at $t=0^-$. The switch is closed. For element values given, determine the values of $v_a(0^-)$ & $v_a(0^+)$.

$$v_a(0^-) \text{ & } v_a(0^+)$$

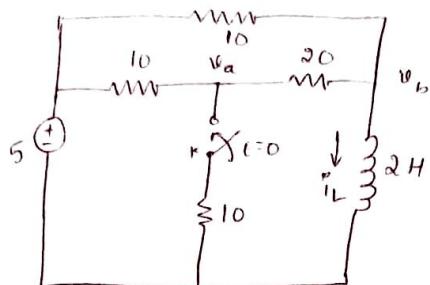

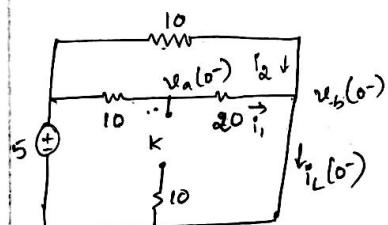Soln:- At $t=0^-$; SW \rightarrow open \rightarrow steady state, $L \rightarrow \infty$.




$$i_L = i_1 + i_2$$

$$i_L(0^-) = \frac{5}{30} + \frac{5}{10} = \frac{2}{3} \text{ A} = i_L(0^+)$$


Using voltage division.

$$v_a = \frac{20+5}{30}$$

$$\boxed{v_a(0^-) = \frac{10}{3} V}$$

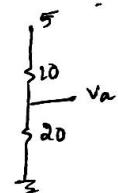

At $t=0^+$:

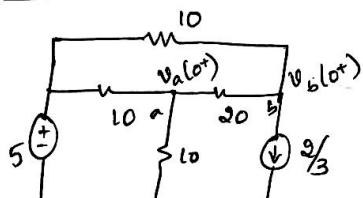

KCL at 'a'

$$\frac{v_a - 5}{10} + \frac{v_a(0^+) - v_b(0^+)}{10} + \frac{v_a(0^+) - v_b(0^+)}{20}$$

$$\left[\frac{1}{10} + \frac{1}{10} + \frac{1}{20} \right] v_a(0^+) - \frac{v_b(0^+)}{20} = \frac{5}{10} \rightarrow 0$$

KCL at 'b'


$$\frac{2}{3} + \frac{v_b(0^+) - 5}{10} + \frac{v_b(0^+) - v_a(0^+)}{20} = 0$$

$$-\frac{v_a(0^+)}{20} + \left[\frac{1}{10} + \frac{1}{20} \right] v_b(0^+) = \frac{5}{10} - \frac{2}{3} \rightarrow (2)$$


$$\therefore \boxed{v_a(0^+) = \frac{40}{21} V}$$

*12
✓

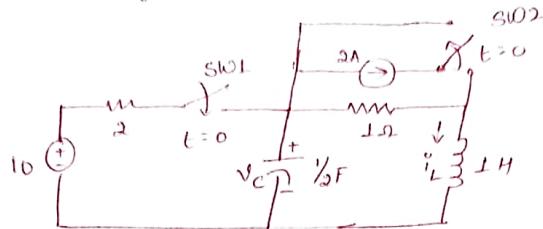Find $i_L(0^+)$, $v_C(0^+)$, $\frac{dv_C(0^+)}{dt}$, $\frac{di_L(0^+)}{dt}$. Assume that switch has been closed for a long time & steady state prevail at $t=0^-$



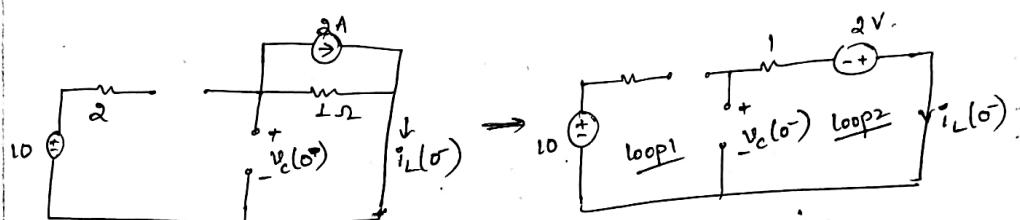→ Soln:- At $t=0^-$: SW1 → open ; SW2 → closed.
 $L \rightarrow S.C$; $C \rightarrow O.C.$




$$\therefore i_L(0^+) = 0A = i_L(0^+)$$

Apply KVL to loop 2,

$$v_C(0^-) - i_L(0^-) + 2 = 0$$

$$\boxed{v_C(0^-) = -2V = v_C(0^+)}$$

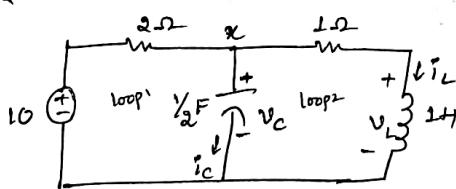At $t \geq 0^+$:- SW1 → closed, SW2 → open



Apply KVL to loop 2,

$$v_C(0^+) + i_L(0^+) - v_L(0^+) = 0$$

$$-2 - 0 - v_L(0^+) = 0$$

$$v_L(0^+) = \frac{L \frac{di_L(0^+)}{dt}}{dt} = -2$$

$$\therefore \boxed{\frac{di_L(0^+)}{dt} = -2A/sec}$$

Apply KCL at χ

$$\frac{v_c - 10}{2} + \dot{v}_c + i_L = 0$$

At $t=0^+$, $\frac{v_c(0^+)}{2} - 5 + \dot{v}_c(0^+) + i_L(0^+) = 0 ; \frac{-2}{2} - 5 + \dot{v}_c(0^+) + 0 = 0$
 $-6 + \dot{v}_c(0^+) = 0.$

$$\therefore \dot{v}_c(0^+) = 6 \text{ A.}$$

$$\therefore C \cdot \frac{dv_c(0^+)}{dt} = \dot{v}_c(0^+) = 6.$$

$$\therefore \frac{dv_c(0^+)}{dt} = \frac{6}{12}$$

$$\frac{dv_c(0^+)}{dt} = 12 \text{ V/sec}$$


* 13

Find


i) $i(0^+) \& v(0^+)$

ii) $\frac{di(0^+)}{dt} \& \frac{dv(0^+)}{dt}$

iii) $i(\infty) \& v(\infty)$

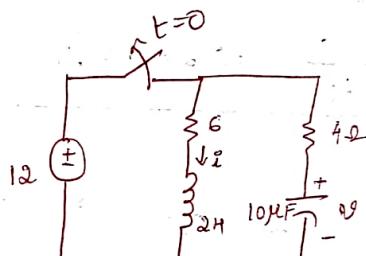

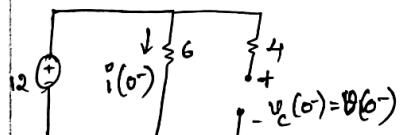
→ Soln:- At $t=0^-$: SW \rightarrow closed \rightarrow steady state, $L \rightarrow \text{s.c.}; C \rightarrow 0\text{C}$



$$i(0^-) = \frac{12}{6} = 2 \text{ A} = i(0^+)$$

$$v(0^-) = 12 \text{ V} = v(0^+) \quad \text{doubt}$$

At $t \geq 0^+$:- SW \rightarrow open.

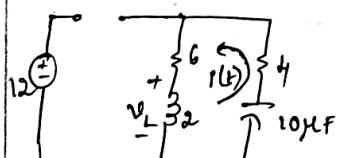

Apply KVL,

$$v_L + G i(t) + 4 i(t) - v = 0$$

At $t=0^+$,

$$v_L(0^+) + 10 i(0^+) - v(0^+) = 0.$$

$$v_L(0^+) + 20 - 12 = 0 ; v_L(0^+) = -8 \text{ V}$$

$$\therefore V_L = L \frac{di}{dt}$$

$$V_L(0^+) = L \frac{di(0^+)}{dt}$$

$$\frac{di(0^+)}{dt} = \frac{-8}{10}$$

$$\boxed{\frac{di(0^+)}{dt} = -8/10 \text{ A/sec}}$$

$$V_L = \frac{L}{dt}$$

$$= 2 \times (-4)$$

$$I_2 = -8 \text{ A}$$

$$\frac{di(0^+)}{dt} = \frac{V_L(0^+)}{L} = \frac{-8}{2}$$


$$I_2 = -4 \text{ A/sec}$$

$$III/4, i_C = C \frac{dv}{dt}$$

$$\frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C} = \frac{+i(0^+)}{C} = \frac{+0.2}{10 \times 10^{-6}}$$

$$\boxed{\frac{dv(0^+)}{dt} = +0.2 \times 10^6 \text{ V/sec}}$$

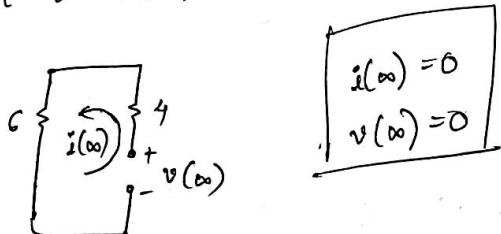(c) At $t \rightarrow \infty$, SW \rightarrow open & ckt attain steady state



* 4

Find,

a) $v(0^+)$ & $i(0^+)$


b) $\frac{dv(0^+)}{dt}$ & $\frac{di(0^+)}{dt}$

c) $v(\infty)$ & $i(\infty)$



\rightarrow soln:-

$$u(t) = \begin{cases} 1 & t \geq 0^+ \\ 0 & t \leq 0^- \end{cases}$$
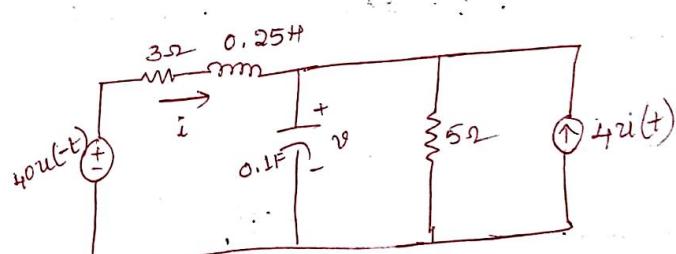
$$u(-t) = \begin{cases} 1 & t \leq 0^+ \\ 0 & t \geq 0^- \end{cases}$$



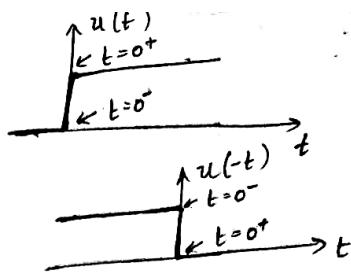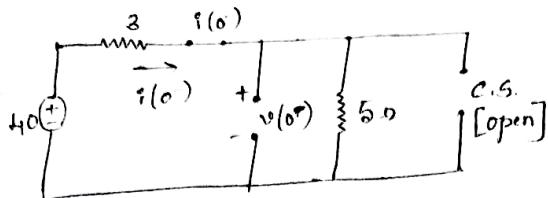
At $t = 0^-$ i.e. Independent C.S. is open
because $v(t) = 0$ at $t = 0^-$ &
the ckt. is in steady state



$$(a) \quad i(0^-) = \frac{40}{3+5} = 5A = i(0^+) \quad /$$

$$v(0^-) = 5i(0^-) = 5 \times 5 = 25V = v(0^+) \quad /$$
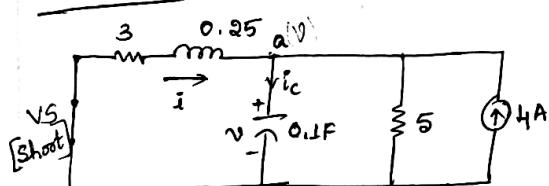
$$(b) \quad \text{At } t \geq 0^+: \quad u(-t) = 0 \quad [\text{vs} = 0 \{ \text{short ckt}\}]$$



Apply KCL at node a,
 $4 + i = C \frac{dv}{dt} + \frac{v}{5}$

$$\text{At } t = 0^+: \quad 4 + i(0^+) = C \frac{dv(0^+)}{dt} + \frac{v(0^+)}{5}$$

$$4 + 5 = 0.1 \frac{dv(0^+)}{dt} + \frac{25}{5}$$

$$\frac{9-5}{0.1} = \frac{dv(0^+)}{dt} ; \quad \boxed{\frac{dv(0^+)}{dt} = 40V/\text{sec}}$$

Apply KVL to loop 1.


$$3i + 0.25 \frac{di}{dt} + v = 0$$

$$\text{At } t = 0^+, \quad 3i(0^+) + 0.25 \frac{di(0^+)}{dt} + v(0^+) = 0$$

$$3 \times 5 + 0.25 \frac{di(0^+)}{dt} + 25 = 0$$

$$\therefore \boxed{\frac{di(0^+)}{dt} = -160A/\text{sec}}$$

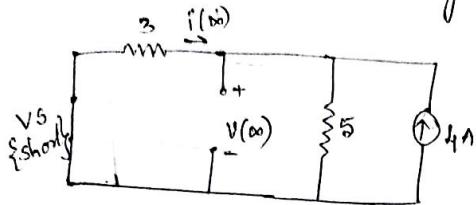(c) $t \rightarrow \infty$; dkt. \rightarrow steady state



$$u(t) = 0 \text{ at } t = \infty \therefore V_s = 0$$

$$i(\infty) = - \left[\frac{5 \times 4}{3+5} \right] = -2.5 \text{ A}$$


$$V(\infty) = \left[i(\infty) + \frac{1}{5} \right] 5 = \left[-2.5 + \frac{1}{5} \right] 5$$

$V(\infty) = 7.5 \text{ V}$

$$\begin{array}{r} 1.5 \\ 2.5 \\ \hline 7.5 \end{array}$$

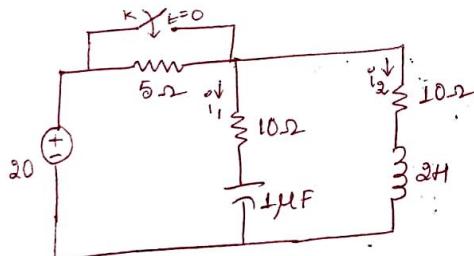
15. In the dkt., steady state is reached with switch 'K' open. The switch is closed at $t=0$. Find

$$i_1, i_2, \frac{di_1}{dt} \approx \frac{di_2}{dt} \text{ at } t=0^+$$



\Rightarrow soln: At $t=0^-$; K \rightarrow open \rightarrow steady state; $L \rightarrow SC; C \rightarrow 0.C.$
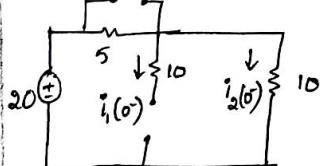
$$i_2(0^-) = \frac{20}{15} = 1.33 \text{ A} = i_2(0^+)$$



$$V_c(0^-) = 10 \times i_2(0^-) = 10 \times 1.33$$


$$V_c(0^-) = 13.3 \text{ V} = V_c(0^+)$$

$$i_1(0^-) = 0 \text{ A}$$

At $t \geq 0^+$: K \rightarrow closed

Apply KVL to loop 1.
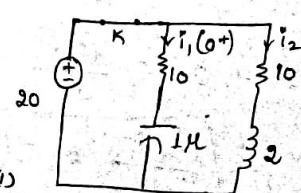
$$20 = 10i_1 + \frac{1}{C} \int_{0^+}^t i_1(\epsilon) d\epsilon \rightarrow 0$$



diff. eqn (1) was 't'

$$10 \frac{di_1}{dt} + \frac{1}{C} i_1 = 0$$

$$\text{At } t=0^+, 10 \frac{di_1(0^+)}{dt} + \frac{i_1(0^+)}{C} = 0$$

$$\text{But } i_1(0^+) = \frac{20 - 13.3}{10} = 0.67 A.$$

$$\frac{di_1(0^+)}{dt} = \frac{-0.67}{10^6 \times 10}$$

$$\boxed{\frac{di_1(0^+)}{dt} = -0.67 \times 10^5 \text{ A/sec.}}$$

Apply KVL to the path $20V \rightarrow K \rightarrow 10\Omega \rightarrow 2H$, we get,

$$20 = 10i_2 + 2 \frac{di_2}{dt}$$


$$\text{At } t=0^+: 20 = 10i_2(0^+) + 2 \frac{di_2(0^+)}{dt}$$

$$\frac{20 - 10(1.33)}{2} = \frac{di_2(0^+)}{dt}; \quad \boxed{\frac{di_2(0^+)}{dt} = 3.35 \text{ A/sec.}}$$

16

The switch 'K' is closed at $t=0$. Find:

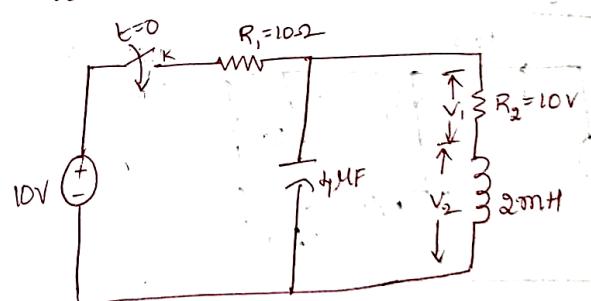- i) v_1 & v_2 at $t=0^+$
- ii) v_1 & v_2 at $t=\infty$
- iii) $\frac{dv_1}{dt}$ & $\frac{dv_2}{dt}$ at $t=0^+$
- iv) $\frac{d^2v_1}{dt^2}$ at $t=0^+$



\rightarrow soln:- a) At $t=0^-$: K → open, ckt. is not active & all the initial conditions are zero.

At $t=0^+$: K → closed, L → O.C.; C → S.C.


$$i_1(0^+) = \frac{10}{10} = 1A \quad \checkmark$$

$$\boxed{V_1(0^+) = 0}; i_2(0^+) = 0$$


Apply KVL to $10V \rightarrow 10\Omega \rightarrow 10\Omega \rightarrow 2mH$, yields

$$10 - 10i_1(0^+) - 10i_2(0^+) + V_2(0^+) = 0$$
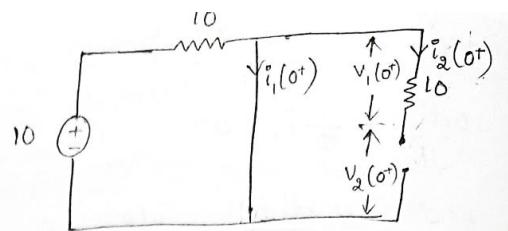
$$10 - 10 - V_2(0^+) = 0 \quad ; \quad \boxed{V_2(0^+) = 0V}$$



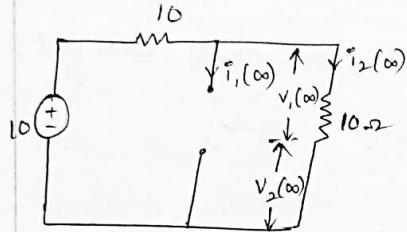b) At $t \rightarrow \infty$: $k \rightarrow$ closed ckt. $\xrightarrow{\text{steady state}}$. $L \rightarrow \text{s.c.}; C \rightarrow \infty$



$$i_1(\infty) = 0A$$


$$i_2(\infty) = \frac{10}{20} = 0.5A$$

$$V_1(\infty) = 10i_2(\infty) = 10 \times 0.5$$

$$V_1(\infty) = 5V$$

$$V_2(\infty) = 0V$$

c) $t \geq 0^+$:

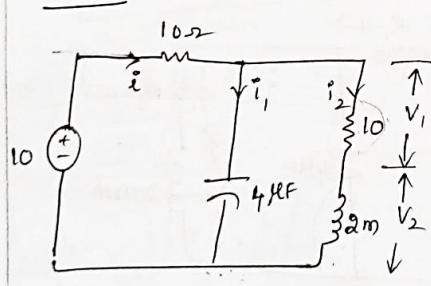

$$i_2 = \frac{1}{L} \int_{0^+}^t v_2(c) dc = \frac{v_1(t)}{R_2}$$

diff. w.r.t. 't'

$$\frac{v_2}{L} = \frac{1}{R_2} \times \frac{dv_1}{dt}$$

$$\text{At } t=0^+, \quad \frac{dv_1(0^+)}{dt} = \frac{R_2}{L} v_2(0^+)$$

$$\frac{dv_1(0^+)}{dt} = 0V/\text{sec}$$

Apply KVL to the path $10V \rightarrow K \rightarrow 10\Omega \rightarrow 4\mu F$

$$-10 + 10i + \frac{1}{C} \int_{0^+}^t [i(c) - i_2(c)] dc = 0$$

diff. w.r.t. 't'

$$10 \frac{di}{dt} + \frac{1}{C} [i - i_2] = 0$$

At $t=0^+$: $\frac{di(0^+)}{dt} = \frac{i_2(0^+) - i(0^+)}{C \times 10}$

$$\begin{aligned} i(0^+) &= i_1(0^+) + i_2(0^+) \\ &= 1 + 0 \\ \hookrightarrow &= 1 A \end{aligned}$$

$$\Rightarrow = -25000A/\text{sec} \downarrow$$

Apply KVL to $10V \rightarrow K \rightarrow 10\Omega \rightarrow 10\Omega \rightarrow 2mH$

$$-10 + 10i + 10i_2 + v_2 = 0 \quad + 10 - 10i - \cancel{(10i_2)} - v_2 = 0$$

$$\underline{10i + v_1 + v_2 = 10}$$

diff. w.r.t. 't'

$$10 \frac{di}{dt} + \frac{dv_1}{dt} + \frac{dv_2}{dt} = 0$$

At $t=0^+$: $10 \cancel{\left(\frac{di(0^+)}{dt}\right)} + \cancel{\frac{dv_1(0^+)}{dt}} + \frac{dv_2(0^+)}{dt} = 0$

$$10(-25000) + 0 + \frac{dv_2(0^+)}{dt} = 0$$

$$\frac{dv_2(0^+)}{dt} = 25 \times 10^4 V/\text{sec} \downarrow$$

d) $\frac{1}{L} \int_{0^+}^t v_2(c) dc = \frac{v_1}{10}$

diff. w.r.t. 't' twice,


$$\frac{1}{L} \frac{dv_2}{dt} = \frac{1}{10} \frac{d^2 v_1}{dt^2}$$

$$\text{At } t=0^+, \quad \frac{1}{L} \frac{dV_L(0^+)}{dt} = \frac{1}{10} \frac{d^2 V_L(0^+)}{dt^2}$$

$$\frac{d^2 V_L(0^+)}{dt^2} = 125 \times 10^7 \text{ V/sec}^2$$

17. The switch 'K' is closed at $t=0$. Find (a) $\frac{di_1(0^+)}{dt}$


(b) $\frac{di_2(0^+)}{dt}$

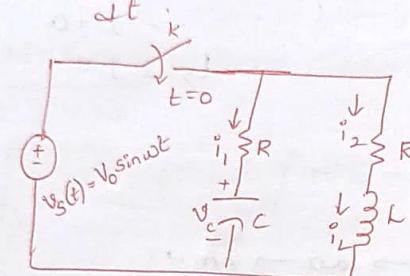


\rightarrow Soln:- At $t=0^-$; K \rightarrow open; ckt is inactive.

$$\therefore \dot{e}_L(0^-) = i_2(0^-) = 0 \text{ A}; \quad v_C(0^-) = 0 \text{ V}; \quad i_2(0^+) = 0 = i_L(0^+)$$

At $t=0^+$:

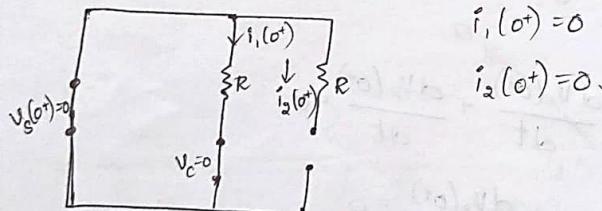

At $t \geq 0^+$:

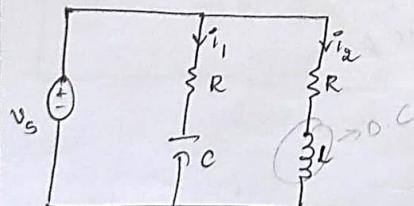

$$V_0 \sin wt = R \dot{i}_1 + \frac{1}{C} \int_{0^+}^t \dot{i}_1 dt$$

diff wt 't'

$$V_0 w \cos wt = \frac{R \dot{i}_1}{dt} + \frac{\dot{i}_1}{C}$$

At $t=0^+$

$$\omega V_0(1) = R \frac{di_1(0^+)}{dt} + \frac{i_1(0^+)}{C}$$

$$\left[\frac{di_1(0^+)}{dt} = \frac{V_0 w}{R} \text{ A/sec} \right]$$

Also,

$$V_0 \sin wt = i_2 R + L \frac{di_2}{dt}$$

At $t=0^+$

$$V_0(0^+) = i_2(0^+)R + L \frac{di_2(0^+)}{dt}$$

$$\left[\frac{di_2(0^+)}{dt} = 0 \text{ A/sec.} \right]$$


- 18 In the n/w, the switch K is opened at $t=0$ after the n/w. has attained steady state with the switch closed.

(a) Find the expression for v_K at $t=0^+$


(b) If the parameters are adjusted such that

$i(0^+) = 1$ & $\frac{di(0^+)}{dt} = -1$, what is the value of the derivative of the vtg. across the switch at $t=0^+$,

$$\left[\frac{dv_K(0^+)}{dt} \right] ?$$

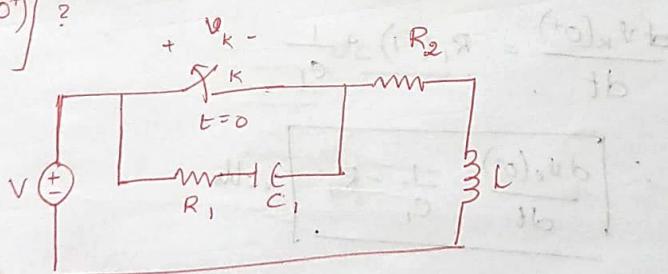

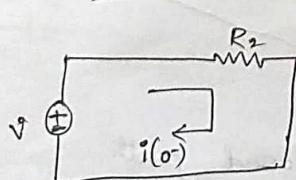
\Rightarrow Qd^n: (a) At $t=0^-$: K \rightarrow closed; ckt. \rightarrow steady state



$$i(0^-) = \frac{V}{R_2}$$

$$v_c(0^-) = 0V = v_c(0^+)$$

At $t \geq 0^+$: K → open.

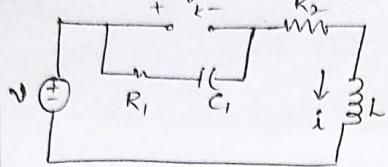

$$v_K = R_1 i + \frac{1}{C_1} \int_{0^+}^t \dot{i}(x) dx$$

$$v_K = R_1 i + v_C(t)$$

$$\text{At } t=0^+; v_K(0^+) = R_1 \dot{i}(0^+) + v_C(0^+)$$

$$v_K(0^+) = R_1 \frac{V}{R_2} \text{ volts}$$

(b)

$$v_K = R_1 \dot{i} + \frac{1}{C_1} \int_{0^+}^t \dot{i}(x) dx$$

diff. w.r.t 't'


$$\frac{dv_K}{dt} = R_1 \frac{d\dot{i}}{dt} + \frac{\dot{i}(t)}{C_1}$$

$$\text{At } t=0^+; \frac{dv_K(0^+)}{dt} = R_1 \frac{d\dot{i}(0^+)}{dt} + \frac{\dot{i}(0^+)}{C_1}$$


$$\frac{dv_K(0^+)}{dt} = R_1 (-i) + \frac{1}{C_1}$$

$$\therefore \boxed{\frac{dv_K(0^+)}{dt} = \frac{1}{C_1} - R_1} \text{ volts}$$

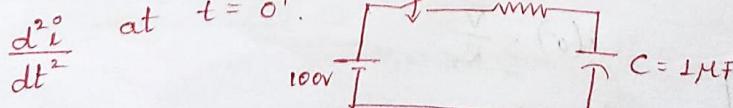19. For the given ckt. K is closed at $t > 0$, find $i, \frac{di}{dt}, \frac{d^2i}{dt^2}$



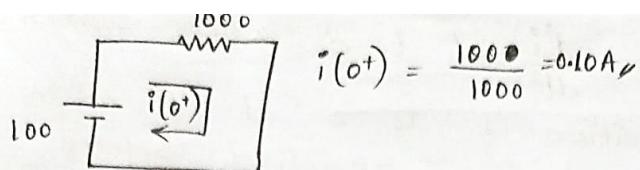Ques:- At $t=0^+$; capacitor acts as closed path.



Apply KVL to loop

$$V = RI + \frac{1}{C} \int i dt \rightarrow (1)$$

Dif. (1) w.r.t t


$$0 = R \frac{di}{dt} + \frac{1}{C} \cdot i \rightarrow (2)$$

At $t = 0^+$

$$0 = R \frac{di(0^+)}{dt} + \frac{1}{C} \cdot i(0^+)$$

$$\therefore R \frac{di(0^+)}{dt} = -\frac{0.1}{10^{-6}}$$
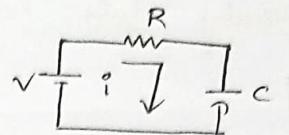
$$\therefore \boxed{\frac{di(0^+)}{dt} = -100A/\text{sec.}}$$



Dif. (2) w.r.t t'

$$0 = R \frac{d^2i}{dt^2} + \frac{1}{C} \frac{di}{dt}$$

At $t = 0^+$

$$0 = R \frac{d^2i(0^+)}{dt^2} + \frac{1}{C} \frac{di(0^+)}{dt}$$

$$\frac{d^2i(0^+)}{dt^2} = -\frac{1}{RC} \frac{di(0^+)}{dt}$$













$$\therefore \boxed{\frac{di(0^+)}{dt} = 100kA/\text{sec}^2}$$

* Summary:-


Elements

After excitation
 $t = 0^+$


Steady state
 $t \rightarrow \infty$

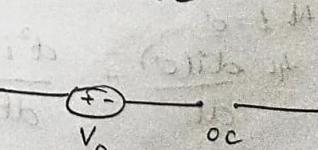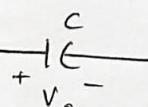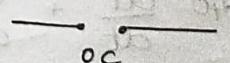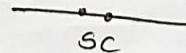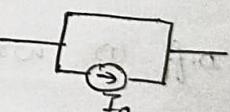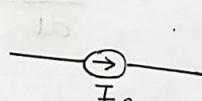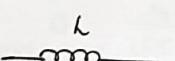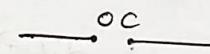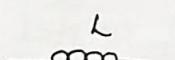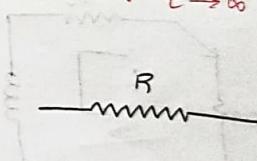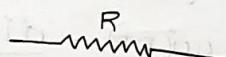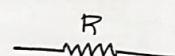

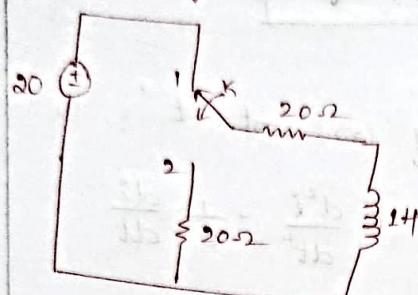Q. Determine i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t=0^+$ when switch K moved from position 1 to 2 at $t=0$ in the n/w, steady state having reached before switching.



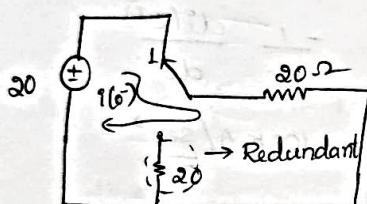
Soln:- At K in position 1: ckt is in steady state, L is short circuited.



$$i(0) = \frac{V}{R} = \frac{20}{20} = 1A$$

$$\therefore i(0^-) = 1A = i(0^+)$$

At K in position 2.

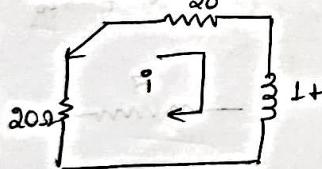

$$40i + 1 \cdot \frac{di}{dt} = 0 \rightarrow (1)$$

At $t=0^+$

$$40i(0^+) + \frac{di(0^+)}{dt} = 0$$

$$\therefore \frac{di(0^+)}{dt} = -40A/\text{sec}$$

Diff. (1) w.r.t 't'

$$40 \cdot \frac{di}{dt} + \frac{d^2i}{dt^2} = 0$$


At $t=0^+$

$$40 \frac{di(0^+)}{dt} + \frac{d^2i(0^+)}{dt^2} = 0$$

$$\therefore \frac{d^2i(0^+)}{dt^2} = -40 \cdot (-40)$$

$$\therefore = 1600A/\text{sec}^2$$

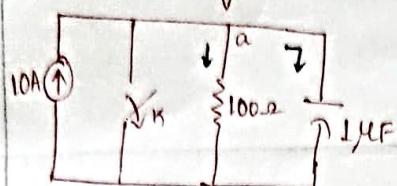21. In the ckt. given below 'K' is opened at $t=0$, find V , $\frac{dV}{dt}$, $\frac{d^2V}{dt^2}$ at $t=0^+$



\rightarrow At $t=0^-$, K is closed & current flows through the switch ignoring 'R' & 'c'. Hence v.tg. drop across capacitor is '0', $V_c(0^-) = 0$

$$\therefore V_c(0^-) = 0 = V_c(0^+), \quad V(0^-) = V(0^+)$$

At $t=0$, K is opened.

Applying KCL at node 'a'

$$10 = \frac{V_0}{100} + C \cdot \frac{dV}{dt} \rightarrow (1)$$

At $t=0^+$

$$10 = \frac{V_0(0^+)}{100} + C \cdot \frac{dV(0^+)}{dt}$$




$$\therefore \frac{10}{10^6} = \frac{dV(0^+)}{dt}; \quad \frac{dV(0^+)}{dt} = 10^7 \text{ V/sec}$$

Diffr (1) wrt 't'

$$0 = \frac{1}{100} \frac{dV}{dt} + C \frac{d^2V}{dt^2}$$

$$\text{At } t=0^+, \quad 0 = \frac{1}{100} \frac{dV(0^+)}{dt} + 10^6 \frac{d^2V(0^+)}{dt^2}$$

$$\therefore \frac{d^2V(0^+)}{dt^2} = -10^9 \text{ V/sec}^2$$

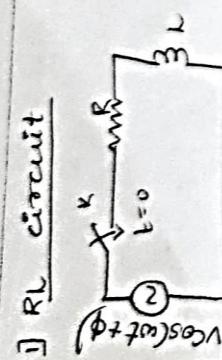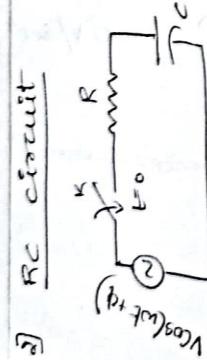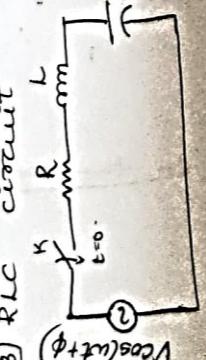
<u>Summary of AC excitation</u>	
Type of circuit	Solution
1) <u>RL circuit</u> 	$i = e^{-\frac{Rt}{L}} \left[\frac{-V}{R^2 + (\omega L)^2} \cos(\phi - \tan^{-1} \frac{\omega L}{R}) \right] + \frac{V}{\sqrt{R^2 + (\omega L)^2}} \left[\cos \omega t + \tan^{-1} \left(\frac{\omega L}{R} \right) \right]$
2) <u>RC circuit</u> 	$i = e^{-\frac{1}{RC} t} \left[\frac{V}{R} \cos \phi - \frac{V}{\sqrt{R^2 + (\omega C)^2}} \cos(\phi + \tan^{-1} \frac{\omega C}{R}) \right] + \frac{V}{\sqrt{R^2 + (\omega C)^2}} \cos(\omega t + \phi + \tan^{-1} \frac{\omega C}{R})$
3) <u>RLC circuit</u> 	$i_{PFF} = \frac{V}{\sqrt{R^2 + (\frac{1}{\omega C} - \omega L)^2}} \cos \left[\omega t + \phi + \tan^{-1} \frac{(\frac{1}{\omega C} - \omega L)}{R} \right]$ <p>i_{CF} & C.E. $P^2 + \frac{R}{L} P + \frac{1}{C} = 0$ $\boxed{i_{CF} = K_3 e^{(K_1 + K_2)t} + K_4 e^{(K_1 - K_2)t}}$</p> <p>$\boxed{K_1, K_2 \text{ are roots}}$</p>

AC excitation Problems

- 1) In the circuit shown, determine complete solution for current when switch 'K' is closed at $t=0$.

Applied voltage is $V(t)$ which is given as

$$100 \cos(10^3 t + \pi/2)$$

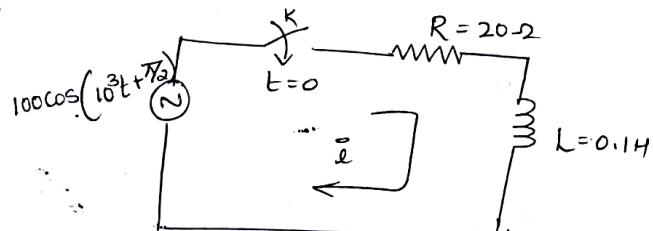

$$\text{Applying KVL, } 20i + 0.1 \frac{di}{dt} = 100 \cos(10^3 t + \pi/2)$$

$$\therefore \frac{di}{dt} + 200i = 1000 \cos(10^3 t + \pi/2)$$

\therefore It is in the form of Non-homogeneous eqn.

$$\therefore i = i_{CF} + i_{PI}$$

$$\therefore i_{CF} = K e^{-\alpha t} = K e^{-200t}$$

$$\therefore i_{PI} = \frac{V}{\sqrt{R^2 + (\omega L)^2}} \cos(\omega t + \phi - \tan^{-1} \frac{\omega L}{R})$$

$$\therefore D = 1000, \phi = \pi/2, V = 100, L = 0.1, R = 20$$

$$\therefore i_{PI} = \frac{100}{\sqrt{(20)^2 + (1000 \times 0.1)^2}} \cos\left(1000t + \pi/2 - \tan^{-1}\left(\frac{1000 \times 0.1}{20}\right)\right)$$

$$\therefore i_{PI} = 0.9805 \cos(1000t + \pi/2 - 78.6^\circ)$$

$$\therefore i = K e^{-200t} + 0.9805 \cos(1000t + \pi/2 - 78.6^\circ)$$


To find K , we use initial condition. At $t=0$, the current flowing through inductor is '0'.

$$0 = K e^0 + 0.9805 \cos(0 + \pi/2 - 78.6^\circ)$$

$$\therefore K = -0.98 \cos(\pi/2 - 78.6^\circ)$$

$$i = -0.98 \cos(\pi_2 - 78.6^\circ) e^{200t} + 0.98 \cos(1000t + \pi_2 - 78.6^\circ) A$$

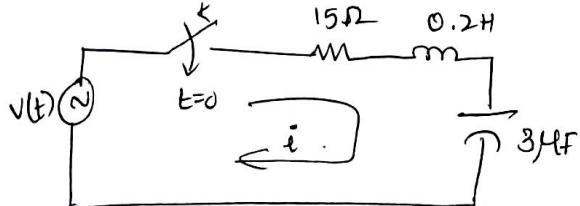2] Determine the complete solution for the current, when switch is closed at $t=0$. Applied voltage is $V(t) = 400 \cos(500t)$



$$0.2 \frac{di}{dt} + 15i + \frac{1}{3 \times 10^6} \int i dt = -400 \cos(500t + \pi_4) \rightarrow \textcircled{1}$$

diff. w.r.t. 't'

$$0.2 \frac{d^2i}{dt^2} + 15 \frac{di}{dt} + \frac{i}{3 \times 10^6} = -\frac{400 \times 500}{2 \times 10^6} \sin(500t + \pi_4)$$

$$\frac{d^2i}{dt^2} + 75 \frac{di}{dt} + 16.67 \times 10^5 i = -2 \times 10^5 \sin(500t + \pi_4).$$

This eqn can be written as -

$$(P^2 + 75P + 16.67 \times 10^5) i = -2 \times 10^5 \sin(500t + \pi_4)$$

\therefore Roots of the eqn is, $P_1 = -37.5 + j1290 \Rightarrow \begin{cases} K_1 = -37.5 \\ K_2 = 1290 \end{cases}$

When roots are complex conjugate, $P_2 = -37.5 - j1290$

\therefore The CF is, $i_{CF} = e^{-37.5t} (K_3 \cos K_2 t + K_4 \sin K_2 t)$

$$\therefore \text{The PS is, } i_{PI} = \frac{V}{\sqrt{R^2 + \left(\frac{1}{\omega C} - \omega L\right)^2}} \cos \left[\omega t + \phi + \tan^{-1} \left(\frac{1}{\omega R C} - \frac{\omega L}{R} \right) \right]$$

$$\therefore V = 400V, R = 15, L = 0.2H, \omega = 500 \text{ rad/sec}, C = 3 \times 10^{-6} F$$

$$\therefore i_{PI} = 0.705 \cos(500t + \pi_4 + 88.48^\circ)$$

$$i = i_{CF} + i_{PI}$$

$$i = e^{-37.5t} \left[K_3 \cos 1290t + K_4 \sin 1290t \right] + 0.705 \cos(500t + \pi_4 + 88.48^\circ) \quad \rightarrow (1)$$

To find K_1 & K_2 :-

At $t=0$, $i=0$: $0 = e^0 [K_3 \cos 0] + 0.705 \cos(133.48^\circ)$

$$K_3 = -0.705 \cos(133.48) = 0.485$$

diff. (1) w.r.t 't'.

$$\frac{di}{dt} = e^{-37.5t} \left[-1290K_3 \sin 1290t + 1290K_4 \cos 1290t \right] - 37.5e^{-37.5t}$$

$$\left[K_3 \cos 1290t + K_4 \sin 1290t \right] - 0.705 \times 500 \overset{\text{sin}}{\cancel{[500t + \pi_4 + 88.48]}}$$

$$\rightarrow (2)$$

But at $t=0$ in (2),

$$15 \times 0 + 0.2 \frac{di(0^+)}{dt} = 400 \cos(0 + \pi/4).$$

$$\frac{di(0^+)}{dt} = 1414 \text{ A/sec.}$$

Subs. $\frac{di}{dt}$ in (2)

$$1414 = e^0 [0 + 1290K_4] - 37.5 \times e^0 \cdot K_3 - 0.705 \times 500 \times \sin(133.5^\circ)$$

$$1414 = 1290K_4 - 37.5K_3 - 255.6$$

$$K_4 = 1.3$$

The complete soln. is,

$$i = e^{-37.5t} [0.485 \cos 1290t + 1.3 \sin 1290t] + 0.705 \cos(500t + 133.5^\circ)$$