

MODULE 2

NETWORK THEOREMS

Mesh & nodal analysis are general analysis which can be used for detailed analysis of a given n/w. In many application it may be necessary to find current & voltage in particular branch, in such cases n/w. theorems are used.


1. RECIPROCITY THEOREM :-

This theorem is applicable only to single src. n/w.

Statement :- In a single src linear bilateral n/w the ratio of response to excitation remains the same when the positions of src. & responses are interchanged.


Proof :- Consider the linear n/w. shown below,

Let the response be ' I_x'

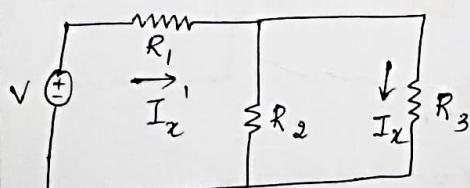

$$I_2 = \frac{R_2 \times I_x'}{R_2 + R_3}$$


$$\text{But, } I_x' = \frac{V}{R_1 + (R_2 || R_3)}$$

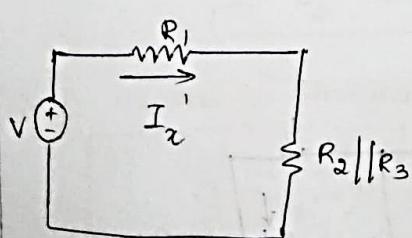

$$\therefore I_x = \frac{R_2}{R_2 + R_3} \cdot \frac{V}{R_1 + \frac{R_2 R_3}{R_2 + R_3}}$$

$$I_x = \frac{R_2 V}{R_1 R_2 + R_1 R_3 + R_2 R_3}, \rightarrow \text{QD}$$

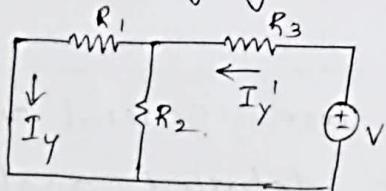Interchanging the positions of src & response




* NOTE:-

Independent V.S.
should be replaced
by short ckt. &
C.S. by open ckt.

$$I_y = \frac{R_2 \cdot I_y'}{R_1 + R_2}$$
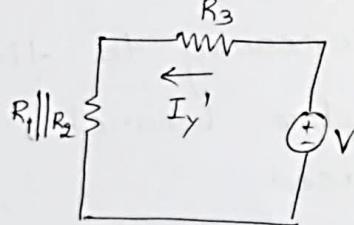
$$\text{But } I_y' = \frac{V}{R_3 + (R_1 \parallel R_2)}$$




$$I_y = \frac{R_2}{R_1 + R_2} \cdot \frac{V}{R_3 + \frac{R_1 R_2}{R_1 + R_2}}$$

$$b = \frac{R_2 V}{R_1 R_2 + R_1 R_3 + R_2 R_3} \rightarrow (2)$$

$$\therefore \text{From (1) \& (2)} \quad \boxed{I_x = I_y}$$


1. Find current through 2Ω

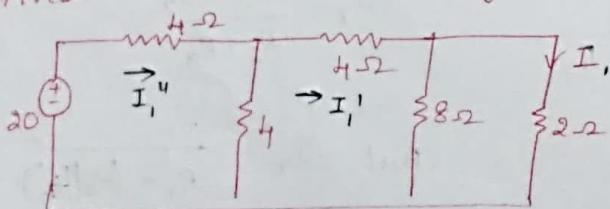


→ Case 1:

$$I_1 = \frac{8 \times I_1'}{10} \rightarrow (1)$$

$$8 \parallel 2 = 1.6$$

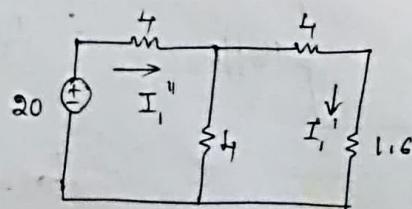
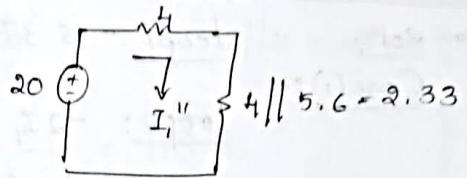
$$\therefore I_1' = \frac{4 \times I_1''}{7.6}$$




$$\therefore I_1'' = \frac{20}{4+2.33}$$

$$\therefore I_1 = 3.159 A$$

$$\therefore I_1' = \frac{4 \times 3.159}{7.6} = 1.3162 A$$


$$I_1 = \frac{8 \times 1.3162}{10} = 1.053 A$$

Case(2):

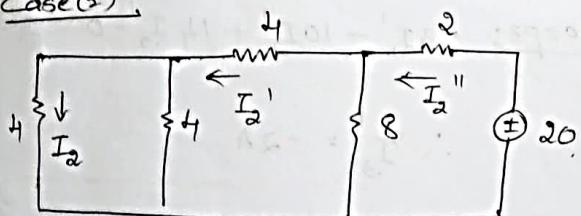

$$I_2 = \frac{4 \times I_2'}{8}$$


$$4//4 = 2\Omega$$

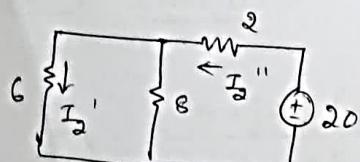

$$I_2' = \frac{8 \times I_2''}{8+6}$$

$$6//8 = 3.42$$
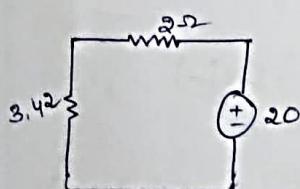
$$\therefore I_2'' = \frac{20}{2+3.42} = 3.69 A$$




$$\therefore I_2' = \frac{8 \times 3.69}{8+6} = 4.10 A$$

$$I_2 = \frac{4 \times 2.10}{8} = 1.05 A$$

$$\therefore I_1 = I_2 = 1.05 A$$

(i) Find current through 1.375Ω .

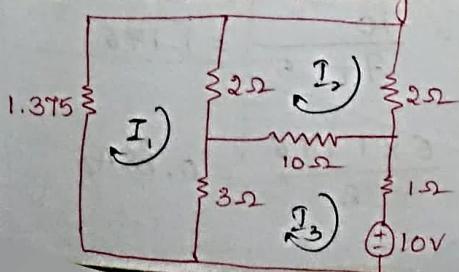


$\Rightarrow \underline{\text{Soln}}:-$ loop 1: $6.375I_1 - 2I_2 - 3I_3 = 0 \rightarrow (1)$

Case(1) :-

loop 2: $-2I_1 + 14I_2 - 10I_3 = 0 \rightarrow (2)$

loop 3: $-3I_1 - 10I_2 + 14I_3 = -10 \rightarrow (3)$

$$\therefore I_1 = -2A$$

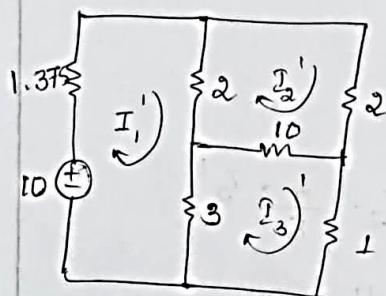Case(2) :-

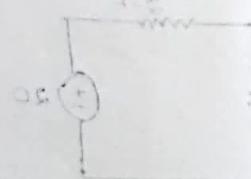
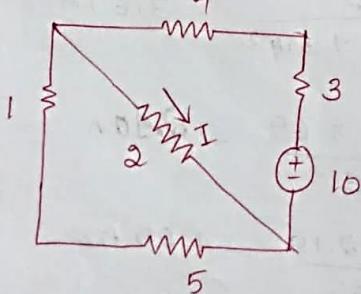
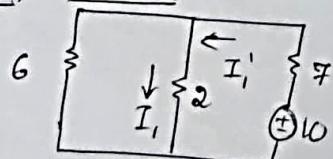
loop 1: $6.375I_1' - 2I_2' - 3I_3' = 10 \rightarrow (1)$

loop 2: $-2I_1' + 14I_2' - 10I_3' = 0 \rightarrow (2)$

loop 3: $-3I_1' - 10I_2' + 14I_3' = 0 \rightarrow (3)$

$$\therefore I_3' = -2A$$

$$\therefore I_1 = I_3' = -2A$$

3. Find I'  $\Rightarrow \underline{\text{Soln}}:-$ Case(1) :-

$$I_1 = \frac{6 \times I_1'}{8}$$

$$6//2 = 1.5$$

$$\text{But } I_1' = \frac{10}{7+1.5} = 1.176$$

$$\therefore I_1 = \frac{6 \times 1.176}{8} = 0.88A$$

Case (2) :-


$$I_2 = \frac{6 \times I_2'}{7+6}$$

$$I_2' = \frac{10}{2+3.23} = 1.911$$

$$I_2 = \frac{6 \times 1.911}{13} = 0.882 A.$$

$$\therefore \boxed{I_1 = I_2 = 0.882 A} = I$$

+ Find 'Vx'

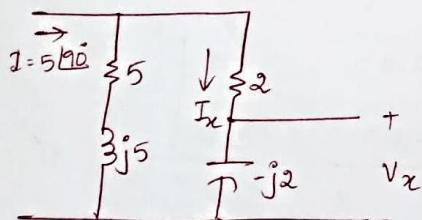


\Rightarrow soln:- Case (1) :- $V_x = (-j2) I_x$

$$I_x = \frac{(5+j5)(5[90^\circ])}{7+3j} = 4.6424 [111.801 A]$$

$$V_x = (-j2)(4.6424 [111.801]) = 9.2848 [21.8^\circ] V$$


Case (2) :-

$$V_y = (5+j5) I_y.$$

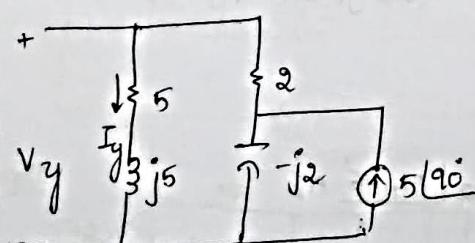


$$I_y = \frac{-j2}{7+j3} \times 5[90^\circ]$$

$$I_y = 1.313 [-23.198] A$$

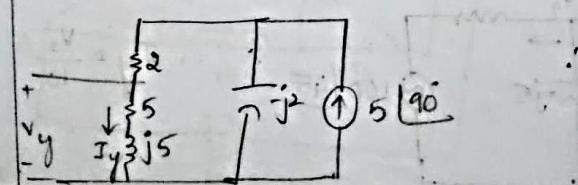

$$\therefore V_y = 9.2848 [21.8^\circ] V$$

$$\therefore \boxed{V_x = V_y}$$

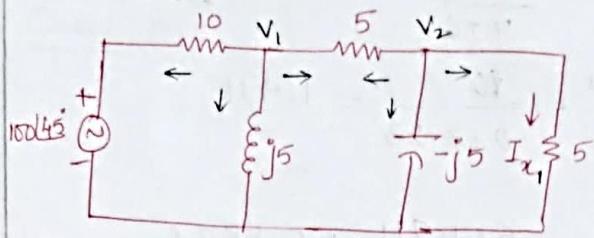5. Find I_x 

$$I_{x_1} = \frac{V_2}{5}$$

→ Case(1):

Node(1):

$$\frac{V_1 - 100\angle 45^\circ}{10} + \frac{V_1}{j5} + \frac{V_1 - V_2}{5} = 0$$

$$(0.3 - j0.2)V_1 - 0.2V_2 = 10\angle 45^\circ \rightarrow (1)$$

Node(2):

$$\frac{V_2 - V_1}{5} + \frac{V_2}{-j5} + \frac{V_2}{5} = 0$$

$$-0.2V_1 + (0.4 + j0.2)V_2 = 0 \rightarrow (2)$$


$$\begin{bmatrix} (0.3 - j0.2) & -0.2 \\ -0.2 & (0.4 + j0.2) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 10\angle 45^\circ \\ 0 \end{bmatrix}$$

$$V_2 = \frac{\begin{vmatrix} 0.3 - j0.2 & 10\angle 45^\circ \\ -0.2 & 0 \end{vmatrix}}{\Delta} = \frac{2\angle 45^\circ}{(0.3 - j0.2)(0.4 + j0.2) - (0.2)^2}$$


$$V_2 = 16.66\angle 54.46^\circ V$$

$$\therefore I_{x_1} = \frac{16.66\angle 54.46^\circ}{5} = 3.332\angle 54.46^\circ A$$

Case(2):-

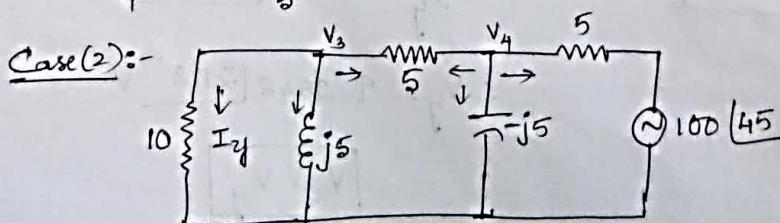

$$\therefore I_y = \frac{V_3}{10}$$

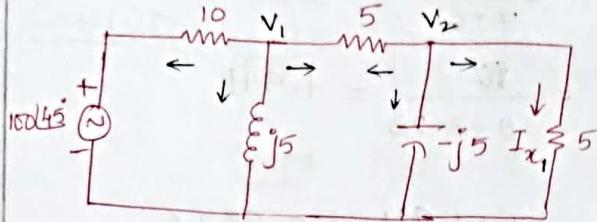5. Find I_x 

$$I_{x_1} = \frac{V_2}{5}$$

→ Case(1):

Node(1):

$$\frac{V_1 - 100\angle 45^\circ}{10} + \frac{V_1}{j5} + \frac{V_1 - V_2}{5} = 0$$

$$(0.3 - j0.2)V_1 - 0.2V_2 = 10\angle 45^\circ \quad \rightarrow (1)$$

Node(2):

$$\frac{V_2 - V_1}{5} + \frac{V_2}{-j5} + \frac{V_2}{5} = 0$$

$$-0.2V_1 + (0.4 + j0.2)V_2 = 0 \quad \rightarrow (2)$$


$$\begin{bmatrix} (0.3 - j0.2) & -0.2 \\ -0.2 & (0.4 + j0.2) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 10\angle 45^\circ \\ 0 \end{bmatrix}$$

$$V_2 = \frac{\begin{vmatrix} 0.3 - j0.2 & 10\angle 45^\circ \\ -0.2 & 0 \end{vmatrix}}{\Delta} = \frac{2\angle 45^\circ}{(0.3 - j0.2)(0.4 + j0.2) - (0.2)^2}$$

$$V_2 = 16.66\angle 54.46^\circ V$$

$$\therefore I_{x_1} = \frac{16.66\angle 54.46^\circ}{5} = 3.332\angle 54.46^\circ A$$

Case(2):-

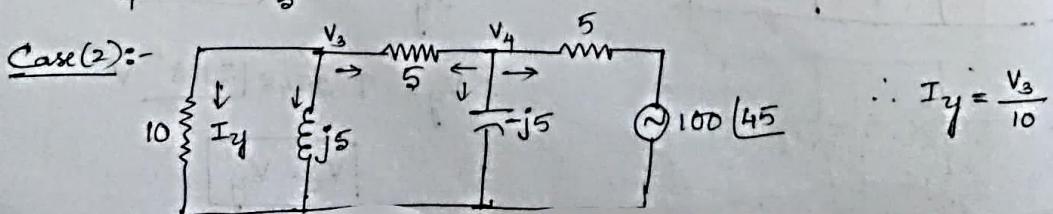

$$\therefore I_y = \frac{V_3}{10}$$

$$\text{Node 3: } \frac{V_3}{10} + \frac{V_3}{j5} + \frac{V_3 - V_4}{5} = 0$$

$$(0.3 - j0.2)V_3 - 0.2V_4 = 0 \rightarrow (3)$$

$$\text{Node 4: } \frac{V_4 - V_3}{5} + \frac{V_4}{-j5} + \frac{V_4 - 20\angle 45^\circ}{5} = 0$$

$$-0.2V_3 + (0.4 + j0.2)V_4 = 20\angle 45^\circ \rightarrow (4)$$

$$\begin{bmatrix} (0.3 - j0.2) & -0.2 \\ -0.2 & (0.4 + j0.2) \end{bmatrix} \begin{bmatrix} V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 20\angle 45^\circ \end{bmatrix}$$


$$V_3 = \frac{\begin{vmatrix} 0 & -0.2 \\ 20\angle 45^\circ & 0.4 + j0.2 \end{vmatrix}}{\Delta} = \frac{0.2 \times 20\angle 45^\circ}{(0.3 - j0.2)(0.4 + j0.2) - (-0.2)^2}$$

$$V_3 = 33.33 \angle 54.46^\circ \text{ V}$$

$$\therefore I_y = \frac{V_3}{10} = 3.333 \angle 54.46^\circ \text{ A}$$


$$\therefore I_x = I_y$$

6. Determine current through 10Ω

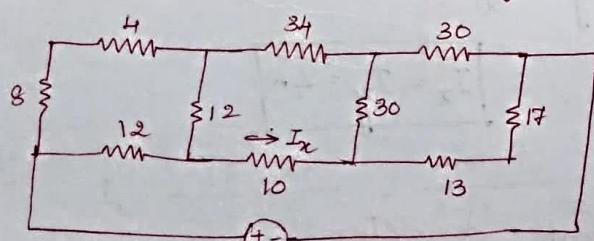


$$\Delta \xrightarrow{A \text{ to } Y} R_A = R_B = R_C$$
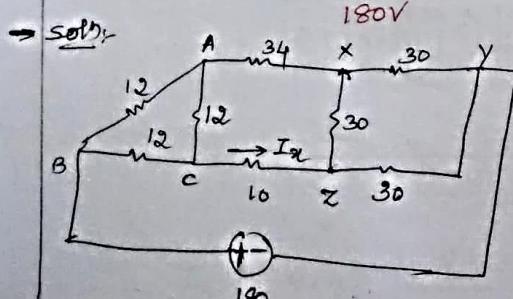
$$R_A = \frac{R_{AB}R_{AC}}{E_{RAB}} = \frac{12 \times 12}{36} = 4 \Omega$$



$$R_x = R_y = R_z$$

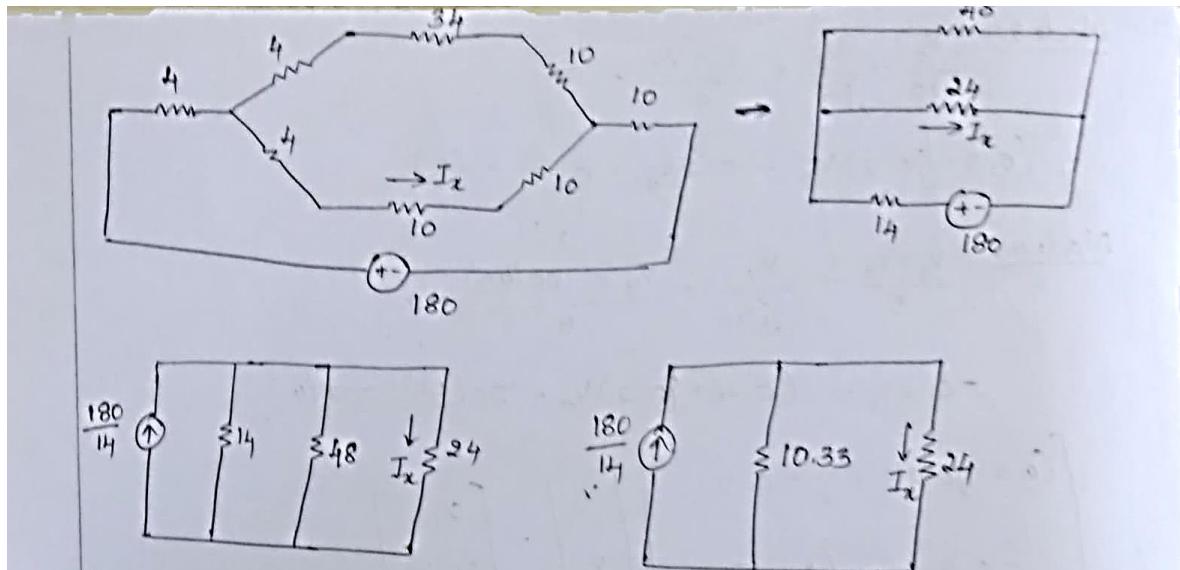
$$R_x = \frac{R_{xy}R_{xz}}{E_{Rxz}} = \frac{30 \times 30}{90} = 10 \Omega$$



$$14 \parallel 48 = 10.33$$

$$I_x = \frac{10.33 \times (180/14)}{34.33} ; \boxed{I_x = 4 \text{ A}}$$

Case(2):-

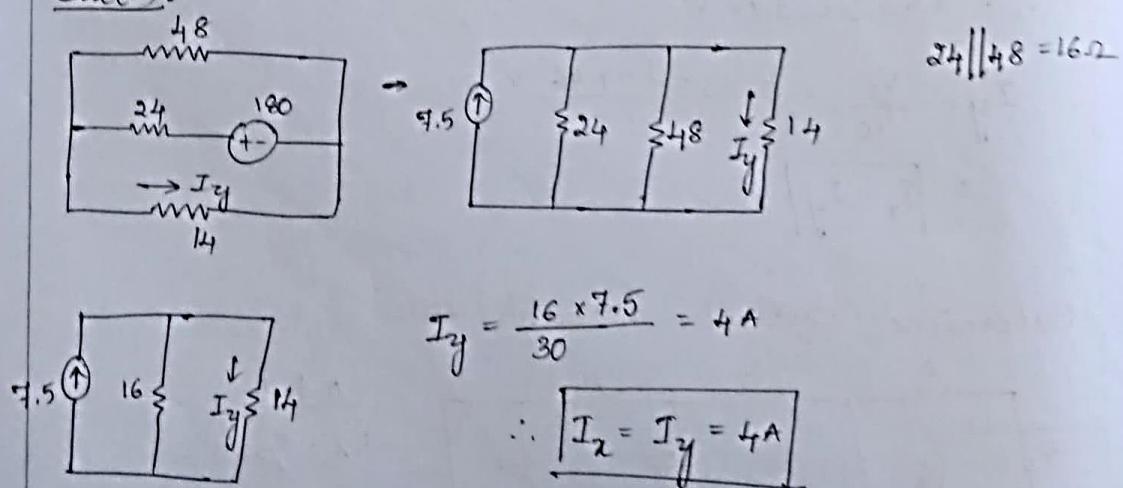

7. Find current through ammeter.



Soln: Case 1:
loop 1:-

$$16I_1 - I_2 - 10I_3 = 0 \rightarrow (1)$$

loop 2:- $-I_1 + 26I_2 - 20I_3 = 0 \rightarrow (2)$


loop 3:-

$$-10I_1 - 20I_2 + 30I_3 = 50 \rightarrow (3)$$

$$I_1 = 4.59A; I_2 = 5.41A$$

$$\therefore I_A = I_2 - I_1 = 0.82A$$

Case(2):

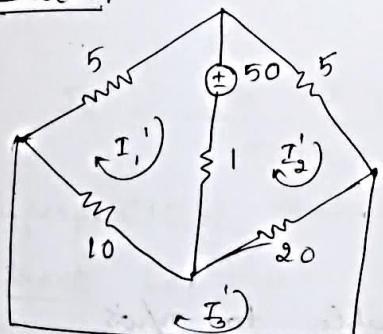

loop 1:

$$16I_1' - I_2' - 10I_3' = -50 \rightarrow (1)$$


$$\text{loop 2: } -I_1' + 26I_2' - 20I_3' = 50 \rightarrow (2)$$

$$\text{loop 3: } -10I_1' - 20I_2' + 30I_3' = 0 \rightarrow (3)$$

$$I_3' = 0.82A$$

$$\therefore I_A = I_3' = 0.82A$$

8. Find current I_x in j_{22} impedance.

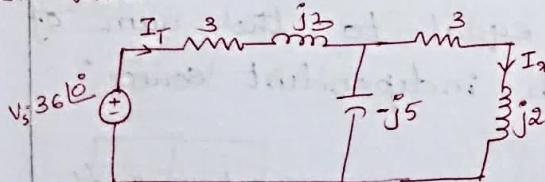


Soln:-

$$I_x = \frac{-j5 \times I_T}{-j5 + 3 + j2} = \frac{-j5 \cdot I_T}{3 - j3}$$

$$Z_T = (2 + j3) + [(-j5) \parallel (3 + j2)] = 6.537 \angle 19.36^\circ$$

$$\therefore I_T = \frac{36\angle 0^\circ}{6.537 \angle 19.36^\circ} = 5.507 \angle -19.36^\circ A$$
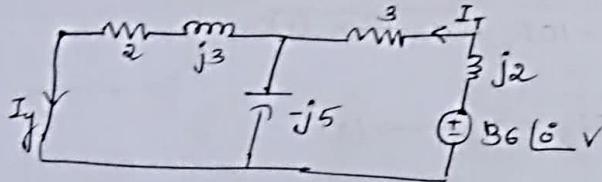
$$\therefore I_x = 6.49 \angle -64.36^\circ A$$



$$I_y = \frac{-j5}{2-j2} \cdot I_1'$$

$$\therefore I_1' = \frac{36 \angle 0^\circ}{Z_1'} = 3.672 \angle -19.36^\circ A$$

$$\therefore Z_1' = [(2+j3)/(P-j5)] + (3+j2)$$

$$\hookrightarrow = 9.804 \angle 19.36^\circ \Omega$$


$$\therefore I_y = 6.49 \angle -64.36^\circ A$$

2 SUPERPOSITION THEOREM

This theorem is applicable to n/w containing multiple srcs.

Statement:- Superposition theorem states that, "in a linear bilateral n/w. containing several independent ssrcs, the overall response at any time in the n/w. is equal to the sum of responses due to each independent source."

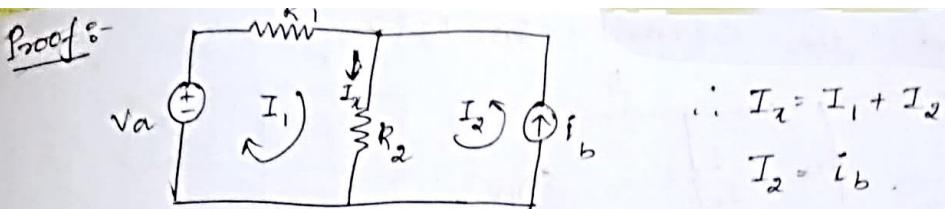Other than the source considered the remaining ssrcs are set to zero. i.e. independent Voltage ssrcs are replaced by short ckt. & independent current ssrcs are replaced by open ckt. Dependent ssrcs are left as they are.



$$\therefore V_a = R_1 I_1 + R_2 (I_1 + I_2) = (R_1 + R_2) I_1 + R_2 i_b$$

$$\therefore I_1 = \frac{V_a - R_2 i_b}{R_1 + R_2}$$


N.K.T.

$$I_x = I_1 + I_2 = \frac{V_a - R_2 i_b}{R_1 + R_2} + i_b$$


$$I_x = \frac{V_a + R_1 i_b}{R_1 + R_2} \rightarrow (1)$$

Superposition theorem method:

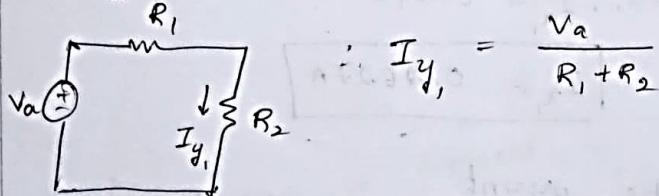Case (1): Let v.s. 'Va' be present & c.s. 'ib' be set to zero [open ckt.]



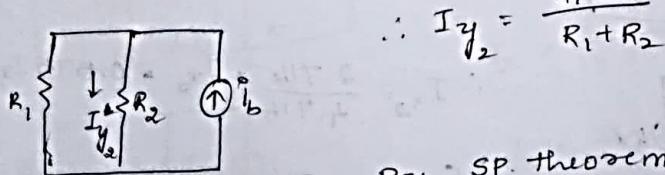Case (2): Let c.s. be present & v.s. be set to zero [short ckt.]




By SP. theorem, $I_y = I_{y_1} + I_{y_2}$

$$\therefore I_y = \frac{V_a}{R_1 + R_2} + \frac{R_1 i_b}{R_1 + R_2}$$

$$I_y = \frac{V_a + R_1 i_b}{R_1 + R_2} \rightarrow (2)$$

$\therefore (1) = (2); I_x = I_y$ Hence superposition theorem verified

1. Find the current in $R=2\Omega$

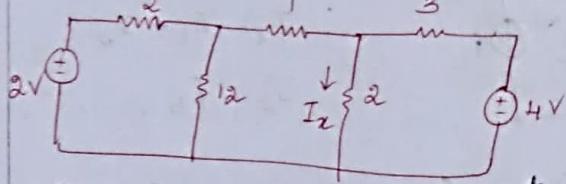

\Rightarrow ~~Case(1)~~: Let 2V be present

$I_{x_1} = \frac{3}{5} I_{x_1}' \leftarrow 0.6 I_{x_1}'$

$[2||3] + 1 = 2.2\Omega$

$I_{x_1}' = \frac{12 \times I_{x_1}''}{14 \cdot 2} = 0.845 I_{x_1}''$

$12||2.2 = \frac{12 \times 2.2}{14 \cdot 2}$


$\hookrightarrow = 1.859\Omega$

$I_{x_1}'' = \frac{2}{3.859} = 0.5182A$

$I_{x_1} = 0.845 \times 0.5182 =$


$I_{x_1} = 0.2627A$

Case(2): Let 4V be present.

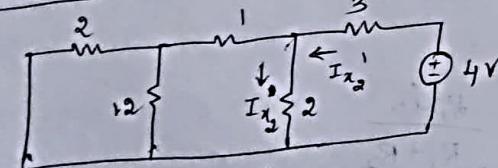


$[2||12] + 1 = \frac{24}{14} + 1$

$\hookrightarrow = 2.714$

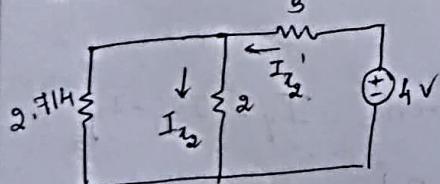

$I_{x_2} = \frac{2.714}{4.714} \times I_{x_2}' = 0.575 I_{x_2}'$

$[2||2.714] = 1.1512$

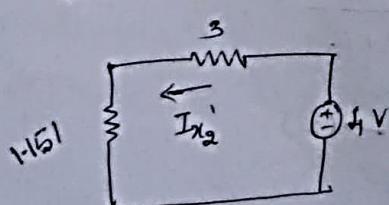


$I_{x_2}' = \frac{4}{4.151} = 0.9635A$

$I_{x_2} = 0.5540A$


$$I_x = I_{x_1} + I_{x_2} = 0.2627 + 0.5540$$

$$\boxed{I_x = 0.8167 \text{ A}}$$


2. Find the current through 10Ω

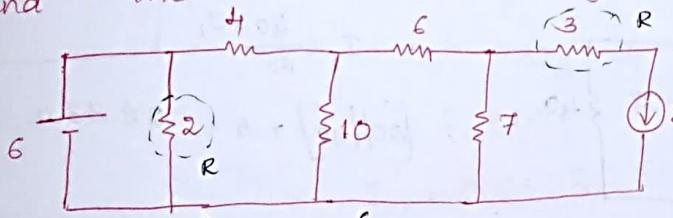

\Rightarrow sol'n.

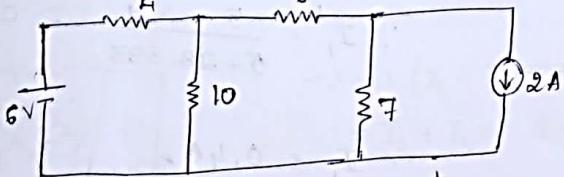

Case(1) :- Let 6V be present

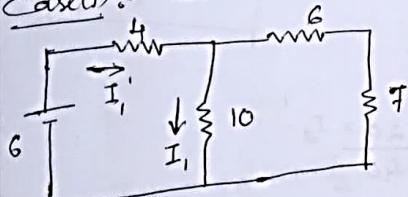

$$6 + 7 = 13$$


$$I_1' = \frac{13}{23} \times I_1 = 0.5652 I_1$$

$$13 \parallel 10 = 5.652$$

$$I_1' = \frac{6}{4 + 5.652} = 0.6216$$

$$I_1 = 0.3513 \text{ A}$$


Case(2) :- Let 2A be present

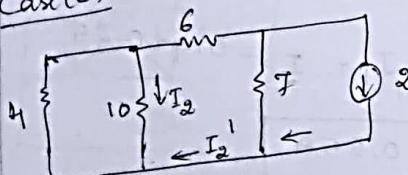

$$I_2' = \frac{4}{14} \times (-I_2)$$

$$[4 \parallel 10] + 6 = 8.857$$
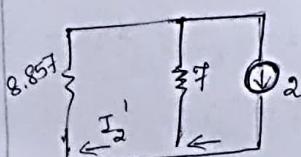
$$I_2' = \frac{7 \times 2}{15.857} = 0.8828$$




$$\therefore I_2 = -0.2522 \text{ A}$$


$$\therefore I = I_1 + I_2 = 0.3513 - 0.2522$$

$$\boxed{I = 0.099 \text{ A}}$$

3. Find current through R_L

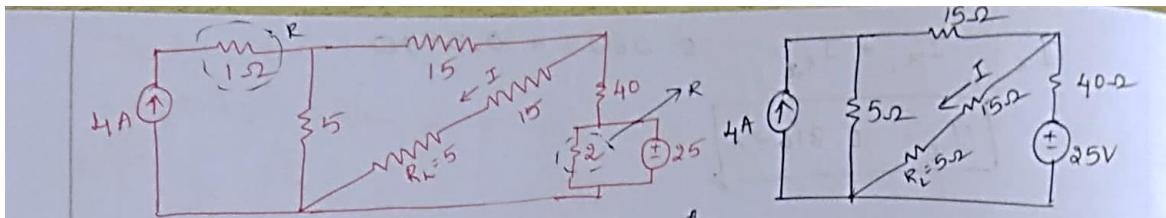


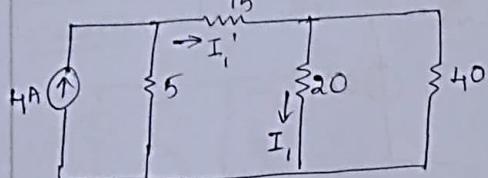\Rightarrow soln \rightarrow Case(1): Let 4A be present



$$\therefore I_1 = \frac{40 \times I_1}{60}$$

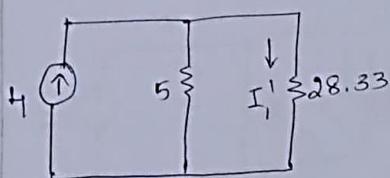
$$\therefore [20/40] + 15 = 28.33\Omega$$



$$\therefore I_1' = \frac{5 \times 4}{5 + 28.33} = 0.6$$

$$\therefore I_1 = 0.4A$$

Case(2): Let 25V be present

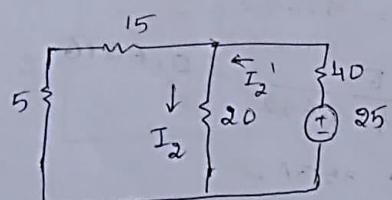


$$I_2 = \frac{20 \times I_2}{40}$$

$$20/40 = 10$$

$$I_2' = \frac{25}{50} = 0.5$$


$$\therefore I_2 = 0.25$$

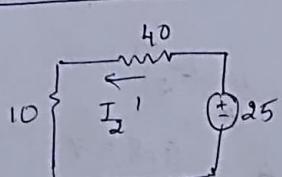


$$\therefore I = I_1 + I_2 = 0.4 + 0.25$$

$$\boxed{I = 0.65A}$$


4- Find the current through 2Ω

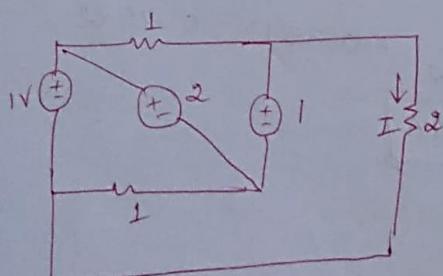

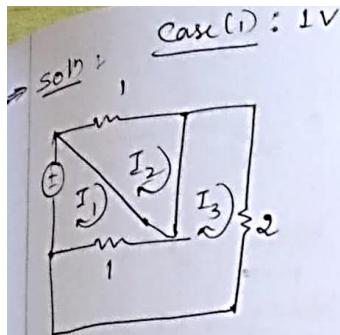

$$\begin{aligned} 1 - (I_1 - I_3) &= 0 \\ -I_1 + I_3 &= 1 \rightarrow (1) \\ I_2 &= 0 \\ -2I_3 - 1(I_3 - I_1) &= 0 \\ -3I_3 + I_1 &= 0 \rightarrow (2) \\ \therefore I_1 = 1.5A; I_2 = 0A; I_3 = 0.5A & \end{aligned}$$

Case (2): 2V

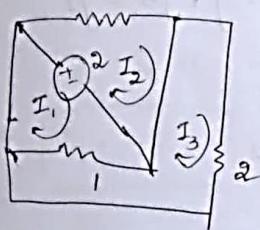


$$\begin{aligned} -2 - 1(I_1 - I_3) &= 0 \\ -I_1 + I_3 &= 2 \rightarrow (1) \\ 2 - I_2 &= 0; I_2 = 2 \\ -2I_3 - 1(I_3 - I_1) &= 0 \\ I_1 - 3I_3 &= 0 \rightarrow (2) \end{aligned}$$

$$I_1 = -3A; I_2 = 2A; I_3 = -1A$$

$$I_{22}'' = I_3 = -1$$

Case (3): 1V

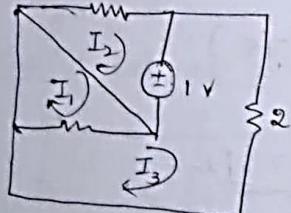

$$\begin{aligned} -I_1 + I_3 &= 0 \rightarrow (1) \\ -I_2 - 1 &= 0 \\ I_2 = -1 & \\ 1 - 2I_3 - (I_3 - I_1) &= 0 \\ I_1 - 3I_3 &= -1 \rightarrow (2) \end{aligned}$$


$$I_1 = 0.5; I_2 = -1A; I_3 = 0.5$$

$$\therefore I_{22}''' = I_3 = 0.5$$

$$\therefore I_{22} = I_{22}' + I_{22}'' + I_{22}''' = 0.5 - 1 + 0.5$$

$$\boxed{I_{22} = 0A}$$


5. Find V_x'

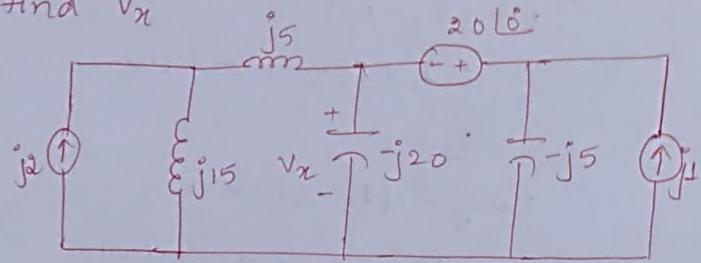

→ Soln:- Case(1): j_{2A} is present

$$\therefore I_{x_1}' = \frac{-j5 \times I_{x_1}'}{j25} = 0.2 I_{x_1}'$$

$$[(-j20) \parallel (-j5)] + j5 = j1$$

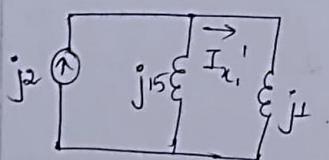


$$\therefore I_{x_1}' = \frac{j15 \times j2}{j16}$$

$$I_{x_1}' = j1.875 A$$

$$\therefore I_{x_1} = j0.375 A$$

Case(2): Let j_{1A} be present

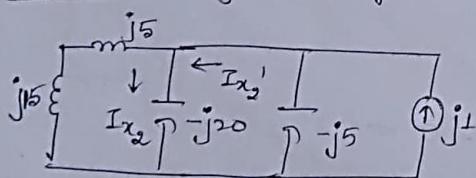


$$I_{x_2} = \frac{j20 \times I_{x_2}'}{j20 - j20} = \infty$$

so take the combination of
 $(j20) \parallel (-j5)$



$$\therefore j20 \parallel (-j5) = -j6.667$$
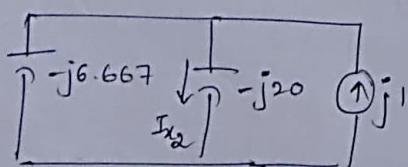
$$I_{x_2} = \frac{-j6.667 \times j1}{j26.67}$$



$$I_{x_2} = 0.247 j$$

Case(3): Let $20\angle0$ be present

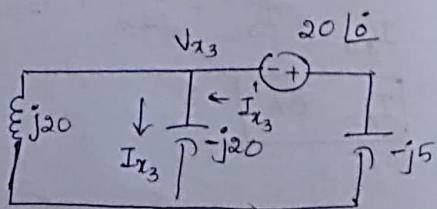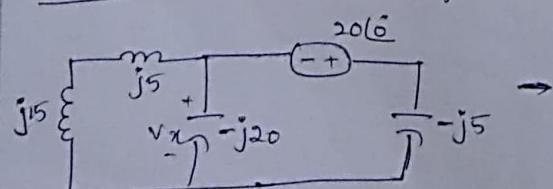

Node analysis,

$$\frac{V_{x_3} - 0}{j20} + \frac{V_{x_3}}{-j20} + \frac{V_{x_3} + 20\angle 0^\circ}{-j5} = 0$$

$$V_{x_3} = -20\angle 0^\circ$$

$$\therefore I_{x_3} = \frac{-20\angle 0^\circ}{-j20} = -j1$$


By superposition thm,

$$I_x = I_{x_1} + I_{x_2} + I_{x_3} = -j0.375A$$

$$\therefore V_x = I_x R = -j0.375 \times (-j20)$$


$$\boxed{V_x = -7.5V}$$

6. Find V_x

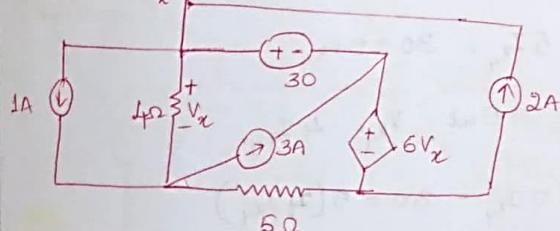

\Rightarrow soln. While applying SPT, dependent vars. are not set to zero.

Case(1): Let 1A c.s. be present

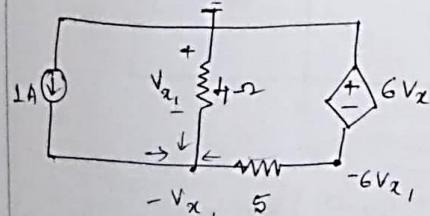



$$1 + \frac{0 - (-V_{x_1})}{4} + \frac{(-6V_{x_1}) + V_{x_1}}{5} = 0$$

$$1 + 0.25V_{x_1} - V_{x_1} = 0$$

$$1 - 0.75V_{x_1} = 0$$

$$V_{x_1} = 1.33V$$

Case(2): Let 3A be present

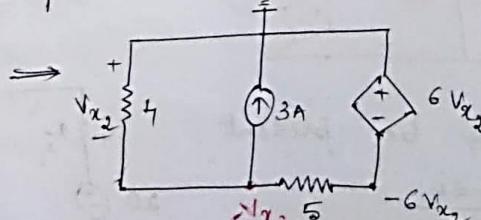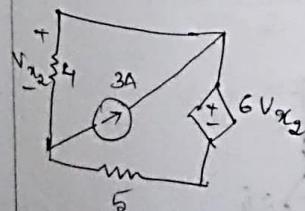


$$3 + \frac{-V_{x_2}}{4} + \frac{[-V_{x_2} - (-6V_{x_2})]}{5} = 0$$

$$3 - 0.25V_{x_2} + V_{x_2} = 0$$

$$3 + 0.75V_{x_2} = 0; V_{x_2} = -4V$$

Case(3) :- Let 2A C.S. be present.

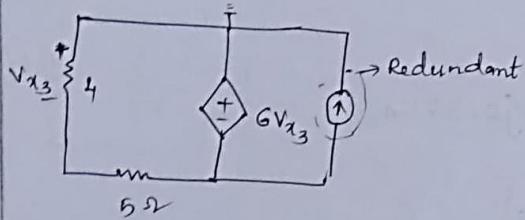


There is no independent src.

$$\therefore V_{x_3} = 0$$

[∴ Anything in ||le with V.S is redundant]

Case(4) :-

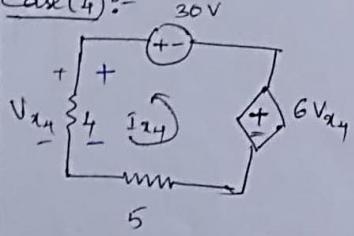

$$I_{x_4} = \frac{30 - V_{x_4} + 6V_{x_4}}{5} = \frac{30 + 5V_{x_4}}{5}$$

$$5I_{x_4} = 30 + 5V_{x_4}$$

$$\text{But } V_{x_4} = 4I_{x_4}$$

$$\therefore 5I_{x_4} = 30 + 5(4I_{x_4})$$


$$-15I_{x_4} = 30; I_{x_4} = -2A$$

$$\therefore V_{x_4} = 4I_{x_4} = -8V$$

By S.P.T.

$$V_x = V_{x_1} + V_{x_2} + V_{x_3} + V_{x_4} = -10.667V$$


7. Find current i

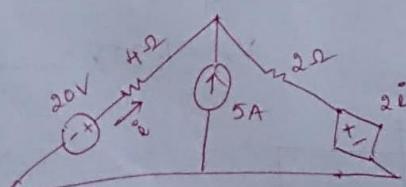


Soln:-
Case(1) :- Let 20V be present

$$i_1 = \frac{20 - 2i}{6}$$

$$\therefore i_1 = 2.5A$$

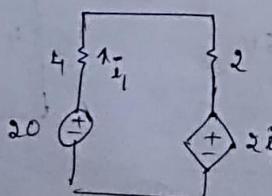

Case (2): Let 5A C.S. be present

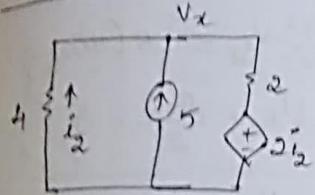

$$i_2 = \frac{0 - V_x}{4}$$

Node analysis.

$$5 + i_2 + \frac{2i_2 - V_x}{2} = 0$$

$$10 + 2i_2 + 2i_2 - V_x = 0$$

$$10 + 4i_2 - V_x = 0$$

$$10 + 4i_2 = V_x = -4i_2$$


$$\therefore 8i_2 = 10; i_2 = -1.25A$$

By SP.T,


$$i = i_1 + i_2 = 2.5 - 1.25$$

$$i = 1.25A$$

8. Find 'Vx'

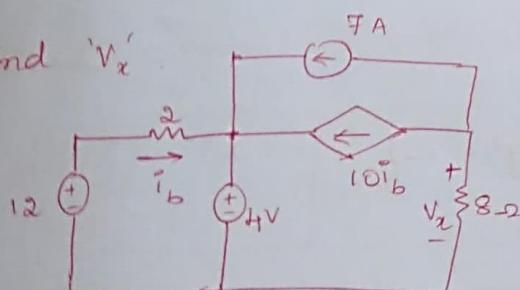

Sol: Case (1): Let 12V be present.

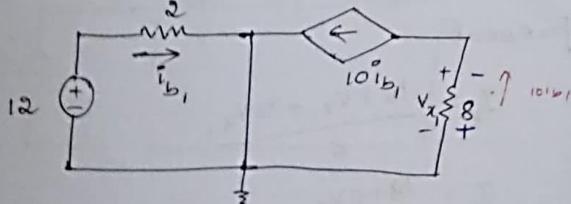


* NOTE: 8Ω connected across $10i_b$ is redundant in terms of current but not in terms of voltage

$$\therefore V_{x_1} = -8(10i_b) = -80i_b$$

$$i_{b_1} = \frac{12 - 0}{2} = 6A$$

$$\therefore V_{x_1} = -480V$$

Case(2): Let $4V$ V.S. be present

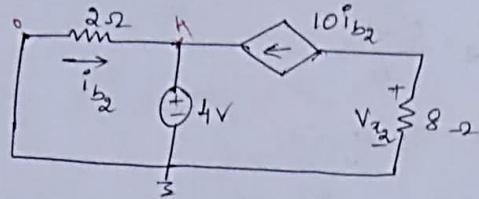


$$\therefore v_{x_2} = -8(10i_{b_2})$$

$$i_{b_2} = \frac{0-4}{2} = -2$$

$$v_{x_2} = +160V.$$

Case(3): Let $7A$ C.S. be present

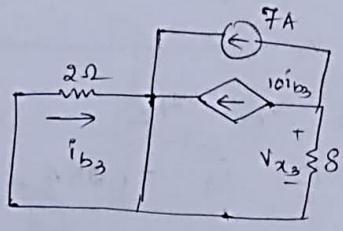

$$\therefore v_{x_3} = -8[10i_{b_3} + 7]$$

$$i_{b_3} = 0$$


$$v_{x_3} = -56V$$

By SPT.


$$V_x = v_{x_1} + v_{x_2} + v_{x_3}$$

$$\boxed{V_x = -376V}$$

Q. Find current through 6Ω

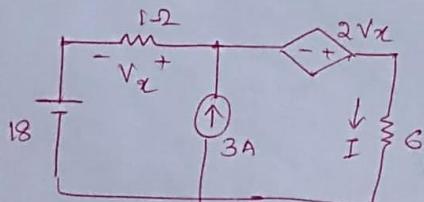

→ Soln: Case(1): $18V$ be present

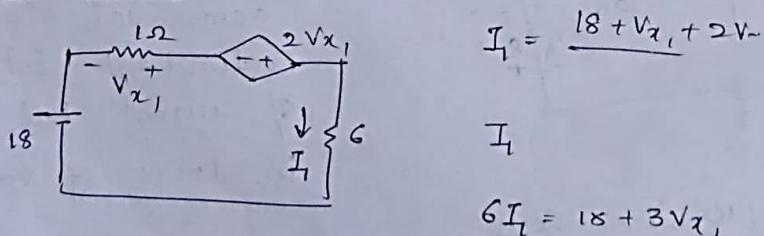

$$I_1 = \frac{18 + v_{x_1} + 2v_{x_1}}{6}$$

$$I_1$$

$$6I_1 = 18 + 3v_{x_1}$$


$$\text{But } v_{x_1} = -6I_1$$

$$\therefore 6I_1 = 18 + 3(-6I_1) = 18 - 18I_1$$

$$9I_1 = 18$$

$$I_1 = 2A$$

Case(2): Let $3A$ be present

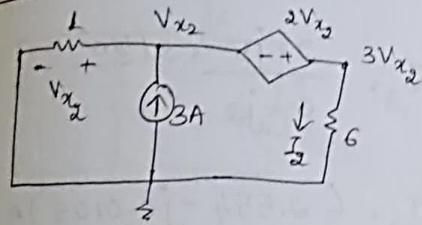

Hint:

If c.s. is present apply node analysis

$$3 + \frac{0 - V_{x2}}{1} + \frac{0 - 3V_{x2}}{6} = 0$$

$$3 - V_{x2} - 0.5V_{x2} = 0$$

$$3 - 1.5V_{x2} = 0$$

$$V_{x2} = 2V$$

$$\therefore I_2 = \frac{3V_{x2} - 0}{6}$$

$$\Rightarrow \frac{6 - 0}{6}$$

$$I_2 = 1A$$


By SPT,

$$I = I_1 + I_2$$


$$I = 3A$$

Find current through $(4+j3) \Omega$

10.

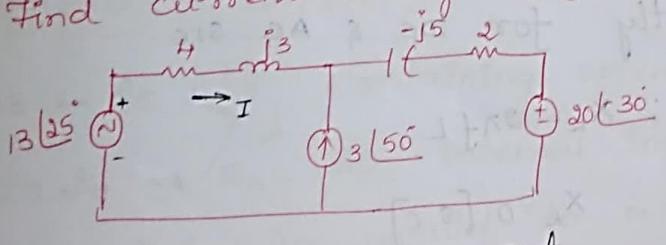

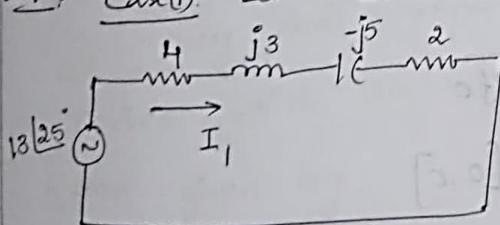
\Rightarrow Qd: Case(1): Let $13\angle 25^\circ$ be present



$$\therefore I_1 = \frac{13\angle 25^\circ}{6 + j3 - j5}$$

$$I_1 = (1.4925 + j1.4132) A$$

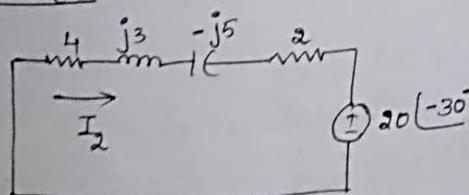
Case(2): Let $20\angle -30^\circ$ be present



$$I_2 = \frac{-20\angle -30^\circ}{6 - j2}$$

$$I_2 = (-3.098 + j0.6339) A$$

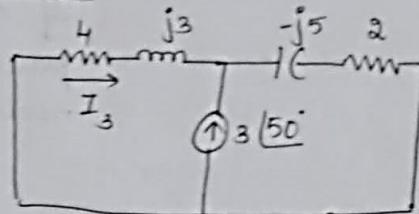Case(3): Let $3\angle 50^\circ A$ be present



$$I_3 = \frac{2-j5}{6-j2} \cdot 3\angle 50^\circ$$

$$I_3 = (2.554 - j0.0105) A$$

∴ By SPT,

$$I = I_1 + I_2 + I_3$$

$$I = (-4.1595 + j2.0366) A$$

* Practical application of superposition thm.:-

* NOTE: When a n/w. contain both AC & DC sources to find the response, SPT must be used because ckt. element behave differently for DC & AC src.

$$\text{---}^L \text{---} ; X_L = 2\pi f L$$

$$L \begin{cases} \nearrow \text{DC} \rightarrow \text{SC} \\ \searrow \text{AC} \rightarrow \text{OC} \end{cases}$$


$$\text{For } f_{dc}=0 : X_L=0 \text{ [s.c.]}$$

$$\text{---}^C \text{---} ; X_C = \frac{1}{2\pi f C}$$


$$C \begin{cases} \nearrow \text{DC} \rightarrow \text{OC} \\ \searrow \text{AC} \rightarrow \text{SC} \end{cases}$$

$$\text{For } f_{dc}=0 : X_C=\infty \text{ [o.c.]}$$

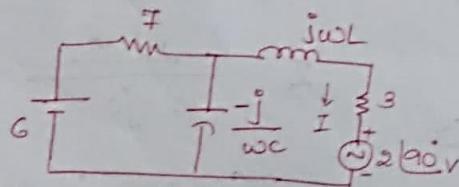ii. Find the current I through 3Ω . [Assume $w_2=1 \neq w_1$]




→ solt: Case(1): Let 6V be present

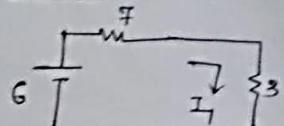


$$I_1 = \frac{6}{10} = 0.6A$$

Case(2) :- Let ωL be present

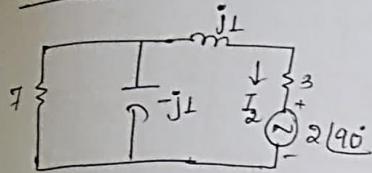

$$7 \parallel (jL) = 0.14 - j0.98$$

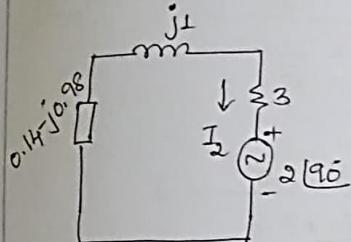

$$I_2 = \frac{-2L90}{0.14 - j0.98 + jL + 3}$$

$$I_2 = -0.00405 - j0.6369$$

$$\therefore \text{By SPT, } I = I_1 + I_2 = 0.6 - 0.00405 - j0.6369$$

$$\boxed{I = 0.59595 - j0.6369 \text{ A}}$$

3. MILLMAN'S THEOREM :-


A n/w. containing several independent v.s. E_1, E_2, \dots, E_n with internal impedance Z_1, Z_2, \dots, Z_n connected in parallel to a load impedance Z_L may be replaced by a single v.s. 'E' in series with an impedance 'Z'. Where E & Z are given by.

$$E = IZ = \frac{I}{Y} = \frac{I_1 + I_2 + \dots + I_n}{Y_1 + Y_2 + \dots + Y_n}$$



$$\Rightarrow Z = \frac{\frac{E_1}{Z_1} + \frac{E_2}{Z_2} + \dots + \frac{E_n}{Z_n}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n}}$$

$$\therefore Z = \frac{1}{Y} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n}}$$

Ques: Consider the net. given below.

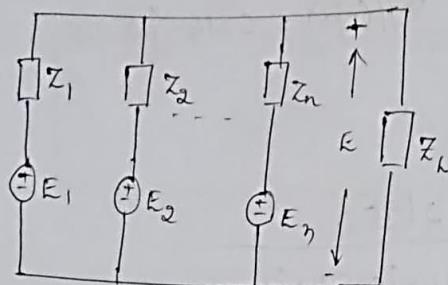


Converting v.s. to c.s.

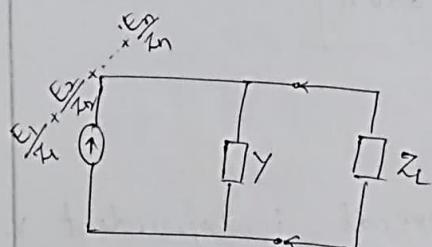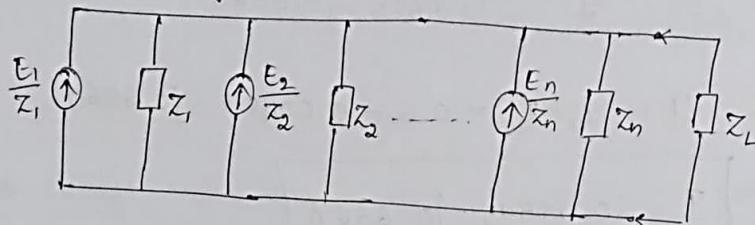

$$Y = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n}$$
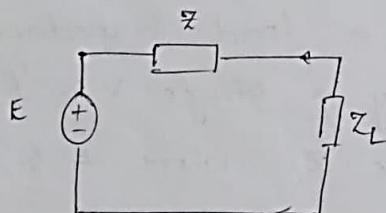
$$\therefore Z = \frac{1}{Y} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n}}$$



$$E = \frac{\frac{E_1}{Z_1} + \frac{E_2}{Z_2} + \dots + \frac{E_n}{Z_n}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n}}$$

Note:

With 3 srs.

$$E = \frac{\frac{E_1}{Z_1} + \frac{E_2}{Z_2} + \frac{E_3}{Z_3}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}}$$

1. Find v.t.g. V_x across $2k$ resistor by using Millman's theorem.

Soln: $E = \frac{\frac{E_1}{Z_1} + \frac{E_2}{Z_2} + \frac{E_3}{Z_3}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}} = \frac{\frac{50}{10,000} + \frac{50}{5000} + \frac{48}{4000}}{\frac{1}{10,000} + \frac{1}{5000} + \frac{1}{4000}}$

$$E = \frac{0.027}{5.5 \times 10^{-4}} = 49.09V$$

$$Z = \frac{1}{Y} = \frac{1}{5.5 \times 10^{-4}} = 1.818k\Omega$$
$$I_x = \frac{49.09}{3.818 \times 10^3} = 0.0129A$$

$$V_x = 2000 I_x = 2000 \times 0.0154$$

$$\boxed{V_x = 30.8V}$$

2. Using Millman's theorem, find current through $R_L = 10\Omega$

Soln: $R_L = 10\Omega$

$$R = \frac{\frac{E_1}{Z_1} + \frac{E_2}{Z_2} + \frac{E_3}{Z_3}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}} = \frac{\frac{20}{5} + \frac{5}{10} + \frac{10}{20}}{\frac{1}{5} + \frac{1}{10} + \frac{1}{20}} = \frac{14}{0.35}$$

$$E = 40V$$

$$Z = \frac{1}{Y} = \frac{1}{0.35} = 2.857\Omega$$


4

THEVENIN'S THEOREM :-

A linear bilateral n/w. however complicated the n/w. may be connected to a load impedance Z_L may be replaced by a single equivalent ckt. containing a voltage source in series with an impedance.


The voltage of voltage source is equal to open circuited voltage across load terminals.

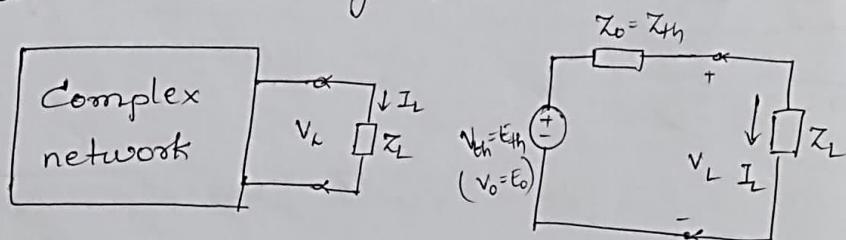The value of impedance is equal to equivalent impedance of the n/w. as viewed from the load terminals into the n/w replacing all independent voltage source by short ckt & current source by open ckt.



$$\therefore I_L = \frac{V_o}{Z_o + Z_L} ; \quad V_L = \frac{V_o \times Z_L}{Z_o + Z_L}$$

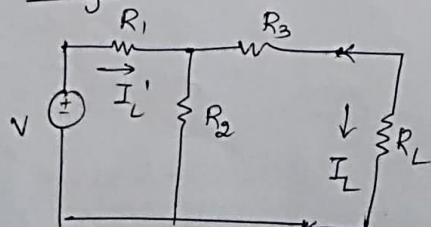Proof :- Consider a linear n/w. given below,



$$I_L = \frac{R_2 \times I'_L}{R_2 + R_3 + R_L}$$


$$\therefore I'_L = \frac{V}{R_1 + [R_3 \parallel (R_3 + R_L)]}$$

$$I_L = \frac{R_2}{R_2 + R_3 + R_L} \left[\frac{V}{R_1 + \frac{R_2(R_3 + R_L)}{R_2 + R_3 + R_L}} \right]$$

$$I_L = \frac{R_2 V}{R_1 R_2 + R_1 R_3 + R_2 R_3 + R_1 R_L + R_2 R_L} \rightarrow (1)$$

To find thevenin's equivalent :-


i) To find thevenin's vtg [V_o]:

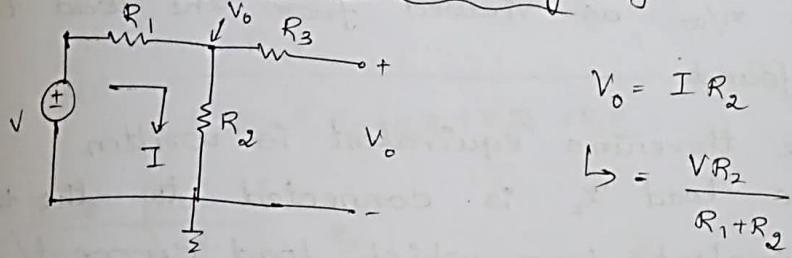

ii) To find thevenin's resistance 'R_o' :

$$R_o = [R_1 || R_2] + R_3 = \frac{R_1 R_2}{R_1 + R_2} + R_3$$
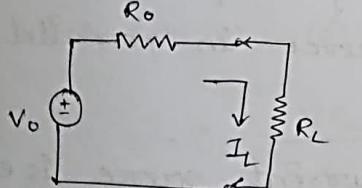
$$R_o = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1 + R_2}$$



$$I_L = \frac{V_o}{R_o + R_L}$$

$$I_L = \frac{\frac{V R_2}{R_1 + R_2}}{\frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1 + R_2} + R_L}$$

$$I_L = \frac{V R_2}{R_1 R_2 + R_2 R_3 + R_1 R_3 + R_1 R_L + R_2 R_L} \rightarrow (2)$$

$$(1) = (2)$$

Hence proved.

Procedure for solving a n/w. using thevenin's theorem

Step1:- The load impedance 'Z_L' through which voltage (or) current is to be found is removed & an open ckt. is created across load terminal.

Step2: The open ckted. vtg. ' V_o ' across load terminal is measured.

Step3: All the independent v.s. are replaced by short ckt. & independent c.s. by open ckt.

Step4: The equivalent impedance ' Z_e ' looking into the n/w. as viewed from the load terminal is found.

Step5: The thevenin's equivalent is written.


Step6: The load ' Z_L ' is connected to the thevenin equivalent from which load current/load vtg. can be found.

5. NORTON'S THEOREM:-

In a linear bilateral n/w. however complicated the n/w. may be connected to ' Z_L ' it maybe replaced by simple equivalent ckt. containing a current source in parallel with an impedance.

The current of the current source is equal to short ckt current flowing through load terminal & the value of ' Z ' is equal to the equivalent impedance of the n/w. as viewed from the load terminal into the n/w. replacing all independent v.s. by short ckt. & current src by open ckt.

Proof:-

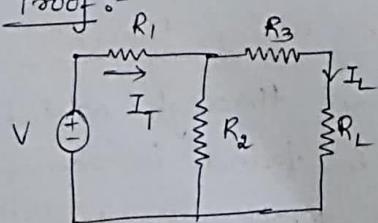

By current division,

$$I_L = \frac{R_2 \cdot I_T}{R_2 + R_3 + R_L} \rightarrow (1)$$


$$I_T = \frac{V}{R_T} \rightarrow (2)$$

$$R_T = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1 + R_1 R_L + R_2 R_L}{R_2 + R_3 + R_L} \rightarrow (3)$$

Subs. (3) in (2) & (2) in (1)

$$I_L = \frac{R_2 V}{R_1 R_2 + R_2 R_3 + R_3 R_1 + R_1 R_L + R_2 R_L} \rightarrow (4)$$

i) To find I_o :

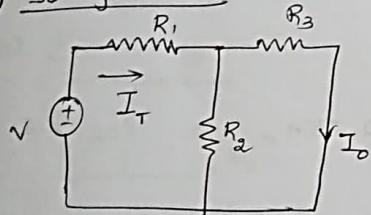

$$I_o = \frac{R_2 \cdot I_T}{R_2 + R_3} \rightarrow (5)$$


$$I_T = \frac{V}{R_T} \rightarrow (6)$$

$$R_T = R_1 + \frac{R_2 R_3}{R_2 + R_3} \rightarrow (7)$$

Subs. eqn. (7) in (6) & (6) in (5)

$$\therefore I_o = \frac{V R_2}{R_1 R_2 + R_2 R_3 + R_1 R_3} \rightarrow (8)$$


ii) To find R_o :

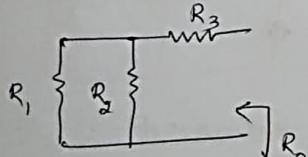

$$R_o = \frac{R_1 R_3 + R_2 R_3 + R_1 R_2}{R_1 + R_2} \rightarrow (9)$$

∴ Norton's eqn. ckt is,
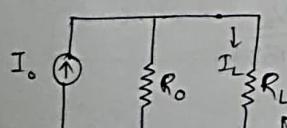
$$\therefore I_L = \frac{R_o \cdot I_o}{R_o + R_L} \rightarrow (10)$$




subs. (8) & (9) in (10),

$$I_L = \frac{V R_2}{R_1 R_2 + R_2 R_3 + R_3 R_1 + R_1 R_L + R_2 R_L} \rightarrow (11)$$


∴ Norton's thm. is proved.

i) For the network shown find,

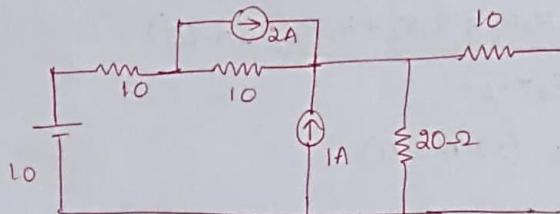(i) Thevenin's equivalent (ii) Norton's equivalent



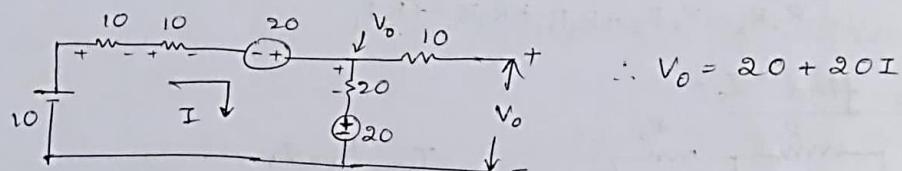Soln: i) Thevenin's equivalent :- (a) Thevenin's voltage :-




$$\therefore I = \frac{10 + 20 - 20}{10 + 10 + 20} = 0.25A$$

$$\therefore V_o = 20 + 20(0.25)$$

$$\boxed{V_o = 25V}$$


(b) Thevenin's resistance :-

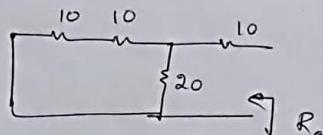

$$R_o = [20//20] + 10 = 10 + 10$$


$$R_o = 20\Omega$$

∴ Thevenin's equivalent,

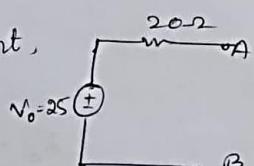

ii) Norton's equivalent :-

(a) I_o :-

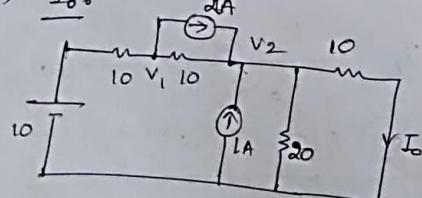

$$I_o = \frac{V_o}{10}$$

$$\text{Node L :- } \frac{10 - V_1}{10} + \frac{V_2 - V_1}{10} - 2 = 0$$

$$0.2V_1 - 0.1V_2 = -1 \rightarrow (1)$$


$$\text{Node(2)} \therefore 1 + 2 + \frac{V_1 - V_2}{10} + \frac{0 - V_2}{20} + \frac{0 - V_2}{10} = 0$$

$$-0.1V_1 + 0.25V_2 = 3 \rightarrow (2)$$

$$\begin{bmatrix} 0.2 & -0.1 \\ -0.1 & 0.25 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -1 \\ 3 \end{bmatrix}$$

$$\therefore V_1 = 1.25V \quad ; \quad V_2 = 12.5V$$


$$\therefore I_o = \frac{V_2}{10} = \frac{12.5}{10} ; \boxed{I_o = 1.25A}$$

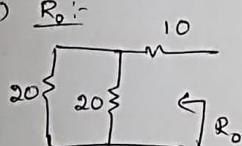(b) R_o :



$$R_o = [20\parallel 20] + 10$$

$$\hookrightarrow = 20\Omega$$

Norton's equivalent,

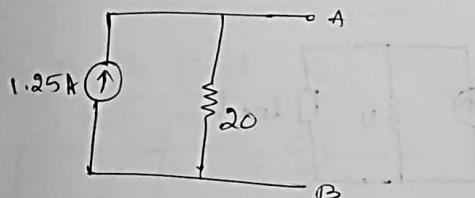

3. Find thevenin's & norton's equivalent ckt

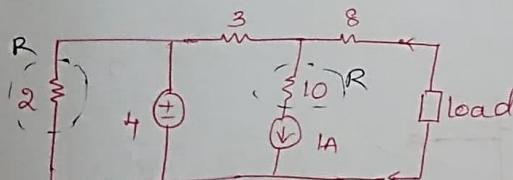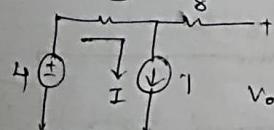→ soln:- i) thevenin's equivalent :-

$$V_o = 4 - 3 \cdot I$$


$$\text{(or)} \quad \frac{V_o - 4}{3} + 1 + 0 = 0$$

$$\text{But } I = 1A$$

$$3 + V_o - 4 = 0$$


$$\therefore V_o = 4 - 3 ; V_o = 1V$$

$$\boxed{V_o = 1V}$$

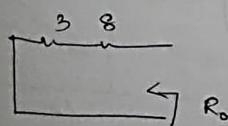


$$R_o = 3 + 8$$

$$\hookrightarrow = 11\Omega$$

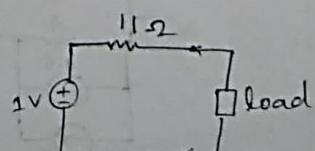

iii) Norton's equivalent :-

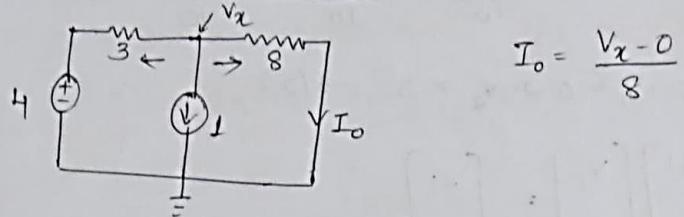


$$\text{Node analysis, } \frac{V_x - 4}{3} + 1 + \frac{V_x}{8} = 0$$


$$V_x = \frac{8}{11}$$

$$\therefore I_o = \frac{\frac{8}{11}}{8}$$

$$\boxed{I_o = \frac{1}{11} \text{ A}}$$

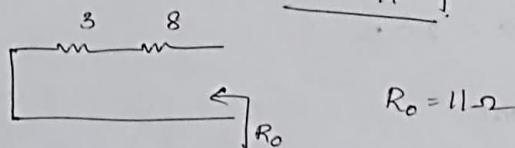


Norton's equivalent.


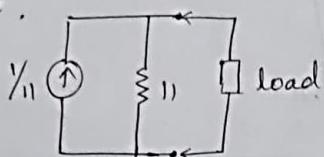



X X

3. Obtain T.E & NE

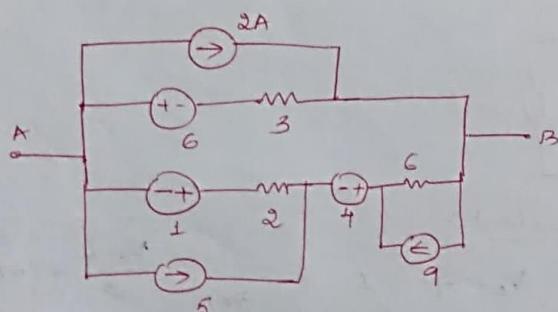


solt:-

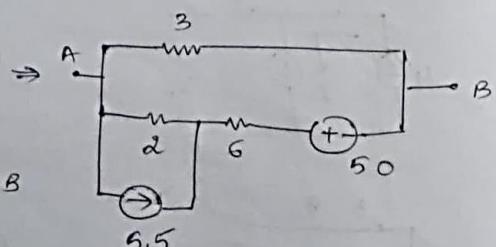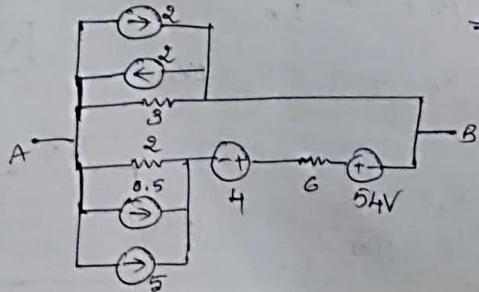


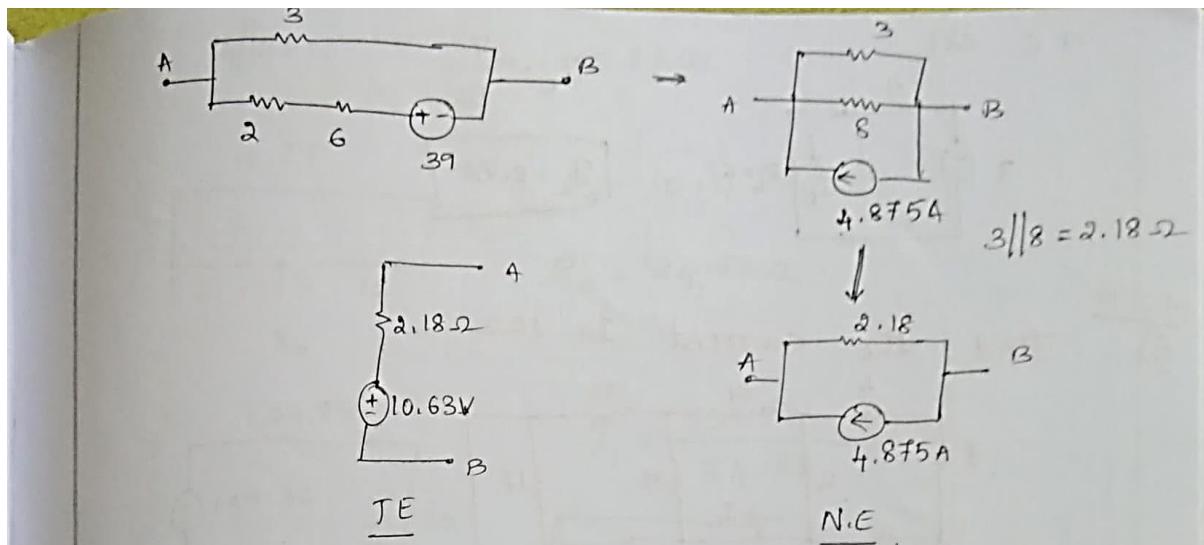

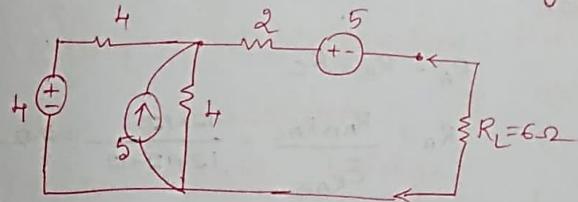4. find the current through $R_L = 6\Omega$



sold :- i) To find V_o :-

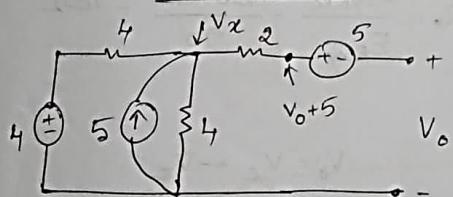

$$\therefore V_x = 5 + V_o$$

$$5 + \frac{4 - V_x}{4} + \frac{6 - V_x}{4} + 0 = 0$$

$$24 - 2V_x = 0$$

$$2V_x = 24$$


$$\boxed{V_x = 12}$$

$$\therefore V_x = 5 + V_o$$

$$V_o = V_x - 5 = 12 - 5$$


$$\boxed{V_o = 7V}$$

ii) To find R_o :-

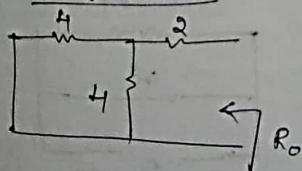

$$R_o = [4||4] + 2 = 4\Omega$$

Q. E. ckt,

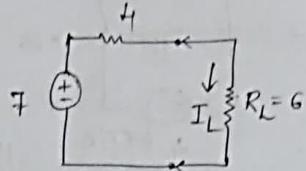


$$I_L = \frac{7}{10}$$


$$\boxed{I_L = 0.7A}$$

M-J-10
5)

Find the current in 10Ω

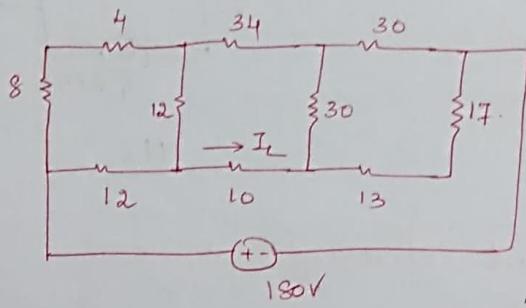

→ 8017:-

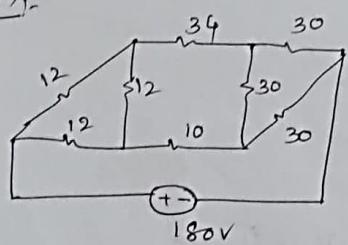


$$R_A = R_B = R_C$$

$$R_A = \frac{R_{AB} R_{AC}}{R_{AB} + R_{AC}} = \frac{12 \times 12}{12 + 12 + 12} = 4\Omega$$

$$R_x = R_y = R_z$$

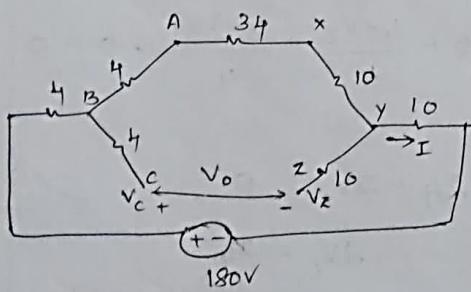
$$R_x = \frac{R_{xy} R_{xz}}{R_{xy} + R_{xz}} = \frac{30 \times 30}{90} = 10\Omega$$



$$V_o = V_C - V_Z$$

$$I = \frac{180}{4 + 4 + 34 + 10 + 10}$$

$$I = 2.903A$$

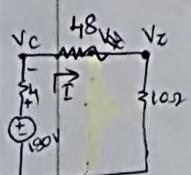

$$V_C = 180 - 4I = 168.39V$$



$$V_Z = 10I = 29.03V$$

$$\therefore V_o = 168.39 - 29.03$$


$$V_C = 180 - 4I$$

$$V_Z = 10I$$


$$\boxed{V_o = 139.36V}$$

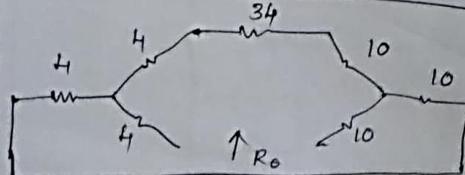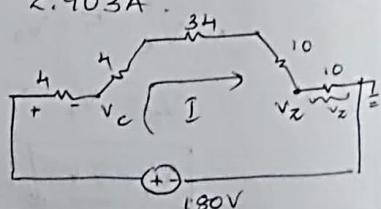

⇒

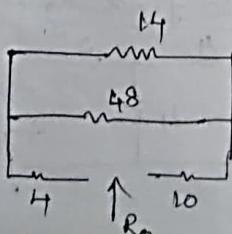

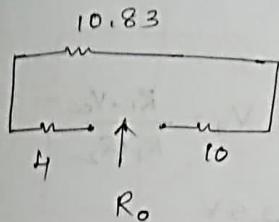
$$\frac{14}{14+48} = \frac{14 \times 48}{14 + 48} = 10.83\Omega$$



$$R_o = 10 + 4 + 10.83$$


$$R_o = 24.83\Omega$$

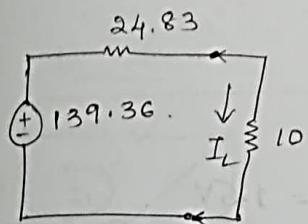

$$I_L = \frac{139.36}{34.83}$$

$$\boxed{I_L = 4A}$$

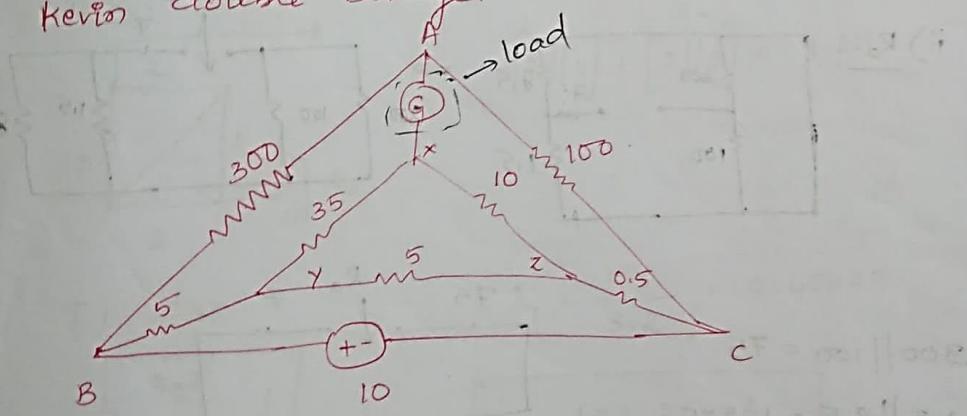Using T.T. determine the current through the galvanometer of 16Ω resistance in Kelvin double bridge.





\Rightarrow soln. $\frac{V_{o\circ}}{10V}$ Convert 'X' to 'Y'.

$$R_x = \frac{R_{xy} R_{xz}}{\Sigma R_{xx}} = \frac{35 \times 10}{50} = 7\Omega$$


$$R_y = \frac{5 \times 35}{10} = 3.5\Omega$$
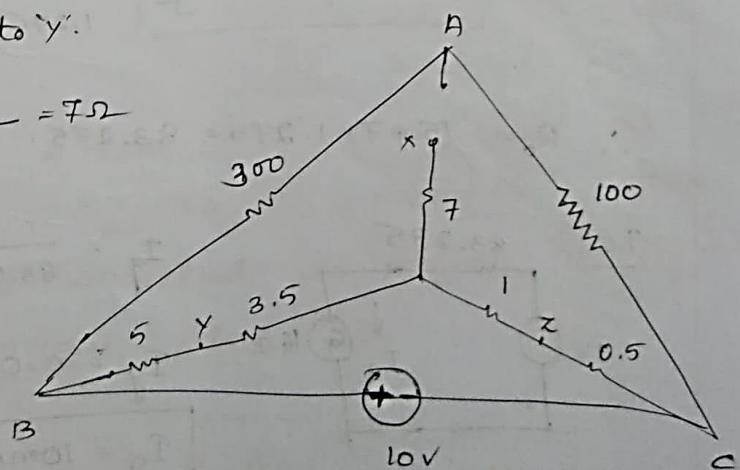
$$R_z = \frac{10 \times 5}{50} = 1\Omega$$




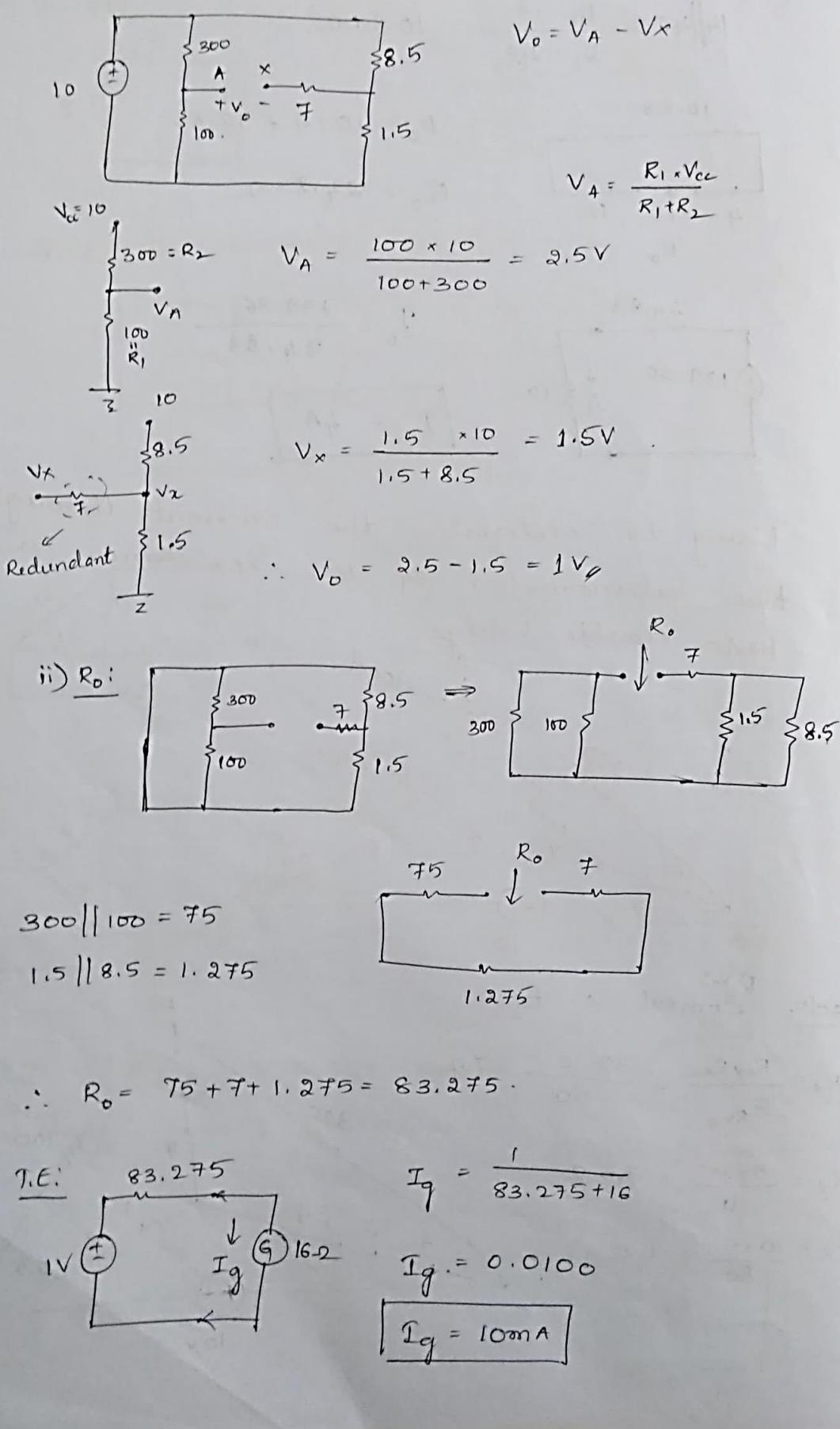

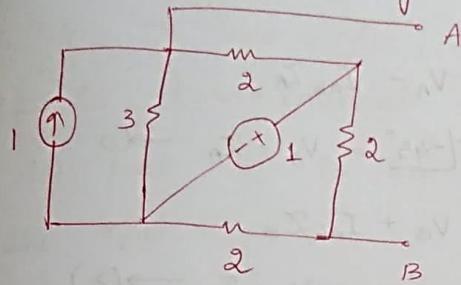Determine current through 1Ω resistor connected b/w A & B using T.T.



\Rightarrow Soln:- i) V_o :

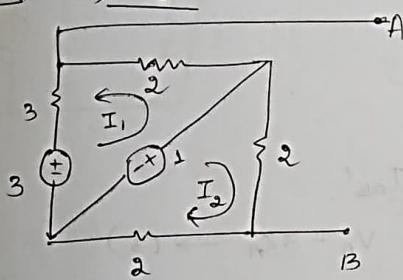

$$V_o = 2I_2 - 2I_1$$


$$I_1 = \frac{-3+1}{5} = -\frac{2}{5} = -0.4A$$

$$I_2 = \frac{1}{4} = 0.25A$$

$$V_o = (2 \times 0.25) - (2 \times (-0.4))$$

$$V_o = 1.3V$$


ii) R_o :

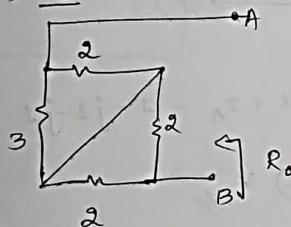

$$[2 \parallel 3] + [2 \parallel 2] = 1.2 + 1 = 2.2\Omega$$

T.E Ckt.


$$I_L = \frac{1.3}{3.2} = 0.40625$$

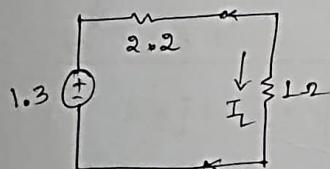


$$\boxed{I_L = 406.25mA}$$

When 2 n/w's A & B are connected as shown in fig(a). $I_{ab} = 1A$, $V_{aa'} = \sqrt{2} \angle -45^\circ V$. When the same n/w is connected as shown in fig(b)

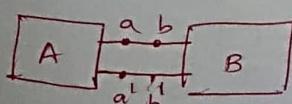$I_{a'b'} = 3A$, $V_{aa'} = \sqrt{2} \angle 45^\circ V$. Find T.E.




fig(a)

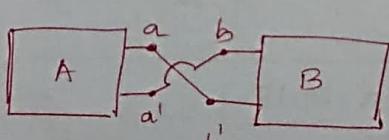

fig(b)

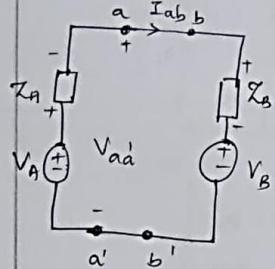→ Let the T.E of v.w A & B be V_A in series with Z_A & V_B in series with Z_B




$$V_{aa'} = V_A - I_{ab} Z_A$$

$$1 - j\omega = \sqrt{2} \angle -45^\circ = V_A - Z_A \rightarrow (1)$$

$$V_{bb'} = V_B + I_{ab} Z_B$$

$$V_{aa'} = V_{bb'} \quad [\text{Same v.tg.}]$$
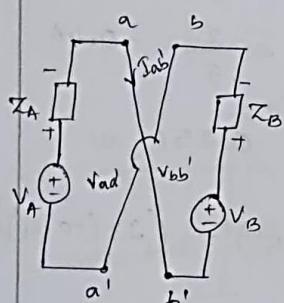
$$\sqrt{2} \angle 45^\circ = 1 + j\omega = V_B + Z_B \rightarrow (2)$$



$$V_{aa'} = -V_{bb'}$$

$$\therefore V_{aa'} = V_A - Z_A I_{ab'}$$

$$\sqrt{2} \angle 45^\circ = 1 + j\omega = V_A - 3Z_A \rightarrow (3)$$

$$V_{bb'} = V_B - 2Z_B = -\sqrt{2} \angle 45^\circ$$

$$-(1 + j\omega) = V_B - 2Z_B \rightarrow (4)$$

$$(1) - (3)$$

$$V_A - Z_A = 1 - j\omega$$

$$\therefore V_A = 1 - j\omega + Z_A = 1 - j\omega - jZ_A$$

$$V_A - 3Z_A = 1 + j\omega$$

$$V_A = (1 - j2) V$$

$$\frac{2Z_A = -j2}{2Z_A = -j2}$$

$$Z_A = -j1 \Omega$$

$$(2) - (4)$$

$$V_B + Z_B = 1 - j\omega$$

$$\therefore V_B = 1 - j\omega - Z_B$$

$$V_B - 3Z_B = -1 - j\omega$$

$$= 1 - j1 - 0.5$$


$$\frac{4Z_B = 2}{4Z_B = 2}$$

$$Z_B = 0.5 \Omega$$

$$\therefore V_B = (0.5 - j1) V$$

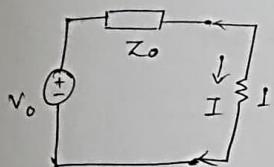9. A LTI η/ω . shown when terminated with
 (i) $R=1\Omega$, $I = 5 \angle -45^\circ$ A ; (ii) $X_C=1\Omega$, $I_C = 10 \angle -45^\circ$ A. Find
 the T.E. of the η/ω . what will be the current
 if it is terminated with $X_L=1\Omega$

\Rightarrow soln:- (i) Let ' V_o ' is in series with ' Z_0 ', the TE of
 the η/ω ,




$$I = \frac{V_o}{Z_0 + 1} = 5 \angle -45^\circ$$

$$Z_0 + 1 = \frac{V_o}{5 \angle -45^\circ}$$

$$Z_0 + 1 = 0.2 \angle 45^\circ V_o \rightarrow (1)$$

(ii)

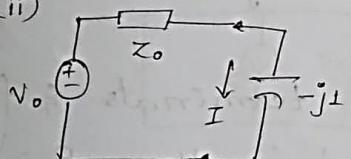

$$I = \frac{V_o}{Z_0 - j1} = 10 \angle -45^\circ$$

$$Z_0 - j1 = 0.1 \angle -45^\circ V_o \rightarrow (2)$$

Solve (1) & (2),


$$\begin{aligned} Z_0 + 1 &= 0.2 \angle 45^\circ V_o \\ Z_0 - j1 &= 0.1 \angle -45^\circ V_o \\ \hline 1 + j1 &= [0.2 \angle 45^\circ - 0.1 \angle -45^\circ] V_o. \end{aligned}$$

$$V_o = \frac{1 + j1}{0.2 \angle 45^\circ - 0.1 \angle -45^\circ} = 14.14 V$$


From eqn (1),
 $Z_0 = 0.2 \angle 45^\circ V_o - 1 = [0.2 \angle 45^\circ \times 14.14 - 1]$

$$Z_0 = (1 + j2) \Omega$$

$$I_L = \frac{14.14}{1 + j2 + j1}$$

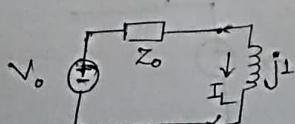
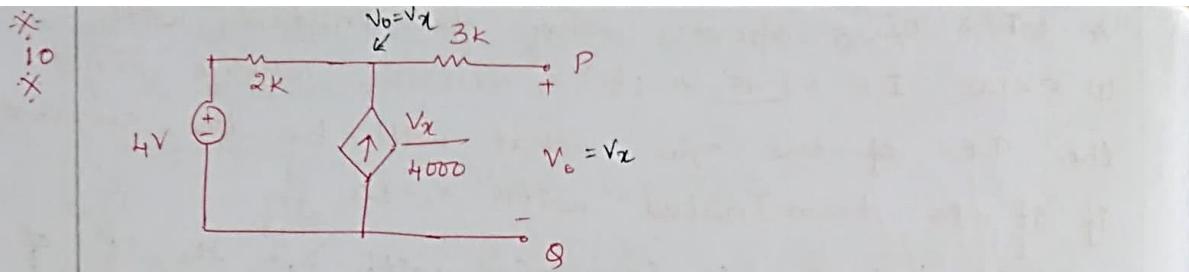
$$\boxed{I_L = 4.46 \angle -71.56^\circ A}$$



\Rightarrow Soln:- i) V_o :

$$\frac{V_x}{4000} + \frac{4 - V_x}{2000} + \frac{V_x - V_o}{3k} = 0$$

$$\boxed{V_x = 8V = V_o}$$

ii) R_o :- When a n/w. contains dependent src. to find $R_o [Z_o]$ the following techniques can be used,


1) Short ckt. the load terminals & find short ckted current 'I_o', then $R_o = \frac{V_o}{I_o}$.

2) Replace all independent v.s. by short ckt. & c.s. by open ckt. Connect a v.s. across the load terminals of value 'V' volt, 10V, 20V... etc, find the current 'I' drawn by the n/w. then $R_o = \frac{V}{I}, \frac{1}{I}, \frac{10}{I}$

I_o: When op terminals are short ckted. to find I_o, V_x becomes 0. This makes dependent c.s.


$$\frac{V_x}{4000} = 0 \quad [0.c]$$

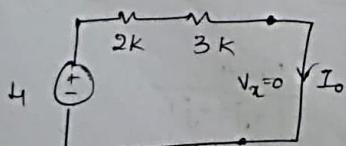
$$\therefore I_o = \frac{4}{5k} = 0.8mA$$



$$R_o = \frac{8}{0.8} = 10k\Omega$$

∴ TE is,

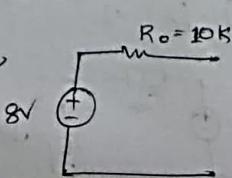

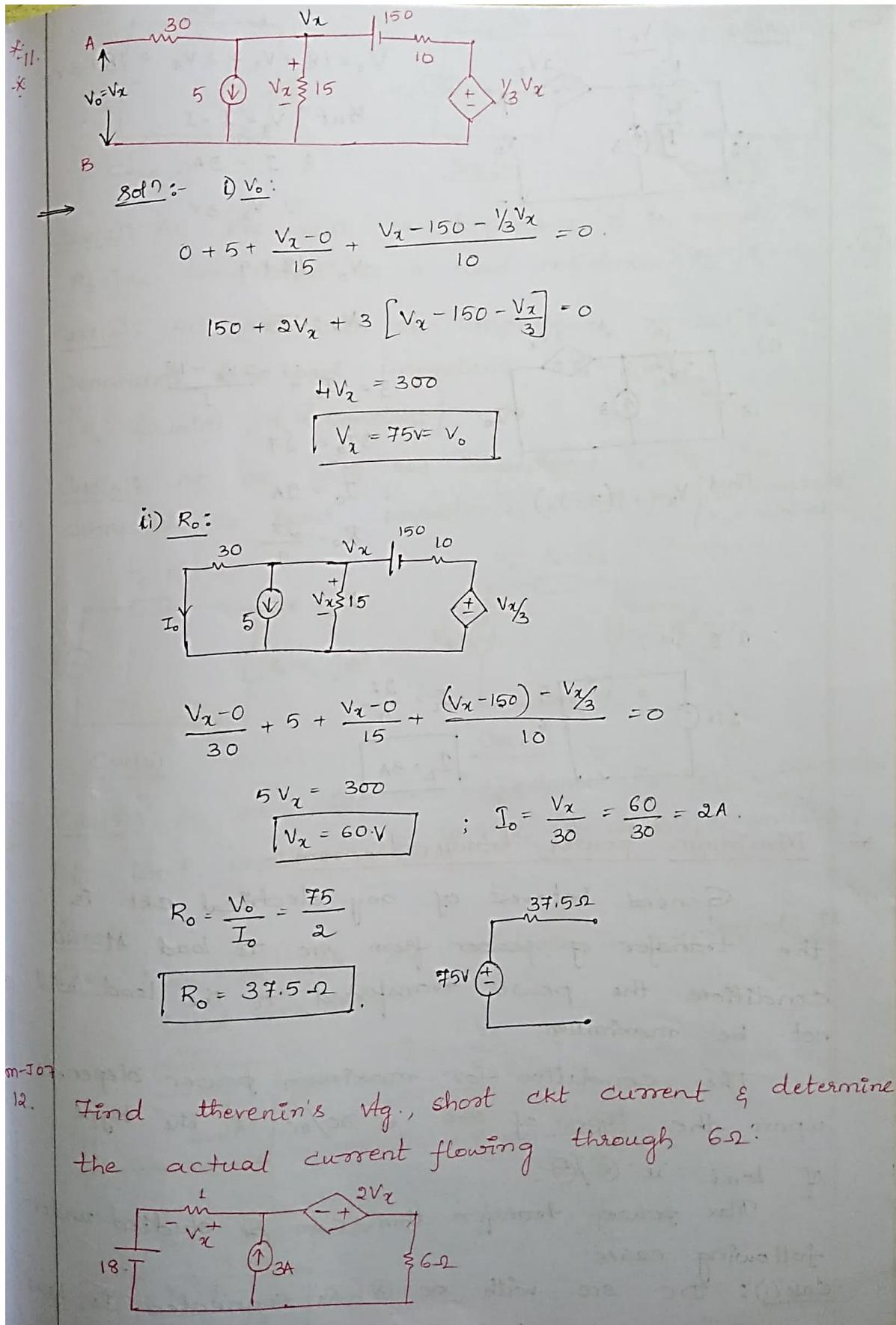

\Rightarrow soln :- i) V_o :

$$V_o = 18 + V_x + 2V_x = 18 + 3V_x$$

$$\text{But } V_x = 1 \times I$$

$$\& I = 3A$$

$$\therefore V_x = 3V$$

$$\therefore V_o = 18 + 9$$

$$V_o = 27V$$

ii) I_o :

$$I_o = I_0 + \frac{-2V_x - 18}{1}$$

$$3I_o = 27$$

$$I_o = 9A$$

$$R_o = \frac{27}{9}$$

$$R_o = 3\Omega$$

\therefore O.E is,

$$I_L = \frac{27}{9}$$

$$\boxed{I_L = 3A}$$


* Maximum power transfer theorem:-

General interest of any electrical ckt. is the transfer of power from src. to load. At all conditions the power transferred to the load will not be maximum.

The condition for maximum power depends upon the type of src. i.e. DC/AC & the type of load. i.e R/R .

Max. power transfer thm. can be studied under following cases.

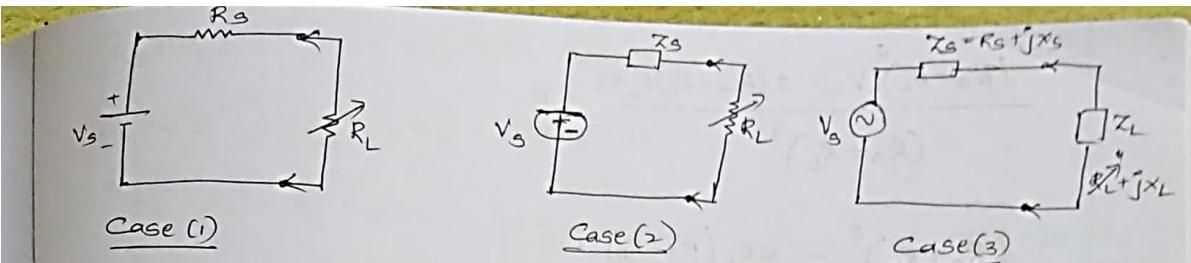
Case(i): DC src. with src. R_s connected to load resistance ' R_L ' [R_s is variable]



Case(2): AC Soc. with soc. impedance 'z' is equal to $R_s + jX_s$ connected to a load resistance ' R_L ' [R_L = Variable]

Case(3): AC Soc with soc impedance $Z_s = R_s + jX_s$ connected to a load impedance, $Z_L = R_L + jX_L$ [R_L = Variable, X_L = Constant]

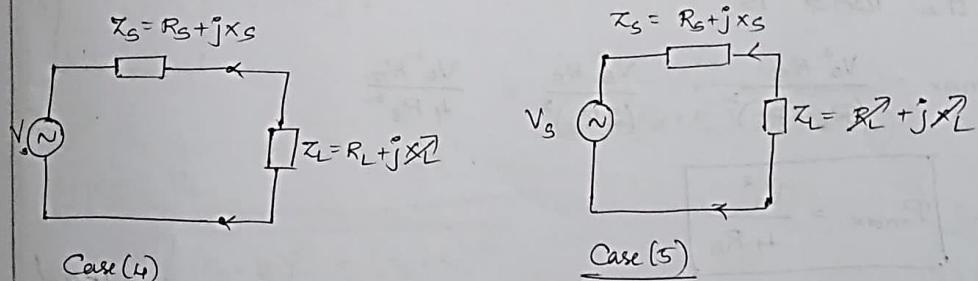
Case(4): AC soc with soc impedance $Z_s = R_s + jX_s$ connected to load impedance. $Z_L = R_L + jX_L \begin{cases} R_L = \text{Constant} \\ X_L = \text{Variable} \end{cases}$



Case(5): AC soc. with soc. impedance $Z_s = R_s + jX_s$ connected to load impedance $Z_L = R_L + jX_L$ [R_L = Variable, X_L = Variable]

Proof:-

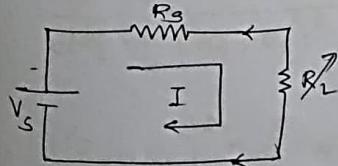Case(1): DC Soc. with soc. resistance ' R_s ' connected to load resistance ' R_L '



$$I = \frac{V_s}{R_s + R_L}$$

$$P = I^2 R_L = \frac{V_s^2 \cdot R_L}{(R_s + R_L)^2}$$

For max. power transfer, $\frac{dP}{dR_L} = 0$.

$$\frac{d}{dR_L} \left[\frac{V_s^2 \cdot R_L}{(R_s + R_L)^2} \right] = 0$$

$$\frac{(R_s + R_L)^2 V_s - 2(R_s + R_L)R_L V_s}{(R_s + R_L)^2} = 0$$

$$(R_s + R_L)^2 - 2R_L(R_s + R_L) = 0$$

$$R_s^2 + R_L^2 + 2R_s R_L - 2R_L R_s - 2R_L^2 = 0$$

$$R_s^2 - R_L^2 = 0$$

$$R_s^2 = R_L^2$$


$\boxed{R_s = R_L}$ This is the condition for max. power transfer.

\therefore Under this condition the max. power transferred to the load is,

$$P_{\max} = \frac{V_s^2 R_s}{(R_s + R_s)^2} = \frac{V_s^2 R_s}{(2R_s)^2} = \frac{V_s^2 R_s}{4R_s^2}$$

$$\therefore \boxed{P_{\max} = \frac{V_s^2}{4R_s}}$$

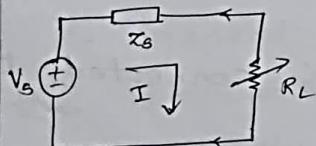Case(2) AC src with $Z_s = R_s + jX_s$ connected to load resistance ' R_L ' [R_L = variable]



$$I = \frac{V_s}{R_s + R_L + jX_s}$$

$$|I| = \frac{V_s}{\sqrt{(R_s + R_L)^2 + X_s^2}}$$

$$P = |I|^2 R_L = \frac{V_s^2 \cdot R_L}{(R_s + R_L)^2 + X_s^2} \rightarrow \textcircled{2}$$

For max. power transfer, $\frac{dP}{dR_L} = 0$;

$$\frac{d}{dR_L} \left[\frac{V_s^2 R_L}{(R_s + R_L)^2 + X_s^2} \right] = 0 \quad \frac{[(R_s + R_L)^2 + X_s^2](1) - 2R_L(R_s + R_L)}{[(R_s + R_L)^2 + X_s^2]^2} = 0$$

$$(R_s + R_L)^2 + X_s^2 - R_L [2(R_s + R_L)] = 0$$

$$R_s^2 + R_L^2 + 2R_s R_L + X_s^2 - 2R_L R_s - 2R_L^2 = 0$$

$$R_s^2 + X_s^2 - R_L^2 = 0$$

$$R_L^2 = R_s^2 + X_s^2$$

Replace $R_L \rightarrow |Z_s|$ in ④


$$\therefore P_{\max} = \frac{V_s^2 |Z_s|}{(R_s + |Z_s|)^2 + X_s^2}$$

$$R_L = \sqrt{R_s^2 + X_s^2} = |Z_s|$$

This is the condition for max power transfer.

Case (3) :- AC source with $Z_s = R_s + jX_s$ connected to load

impedance $Z_L = R_L + jX_L$

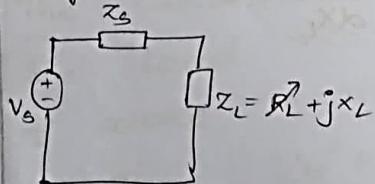

$$I = \frac{V_s}{R_s + jX_s + R_L + jX_L}$$

$$I_s = \frac{V_s}{(R_s + R_L) + j(X_s + X_L)}$$

$$|I| = \frac{V_s}{\sqrt{(R_s + R_L)^2 + (X_s + X_L)^2}}$$

$$\therefore P = |I|^2 R_L = \frac{V_s^2 R_L}{(R_s + R_L)^2 + (X_s + X_L)^2}$$

For max. power transfer, $\frac{dP}{dR_L} = 0$

$$\frac{d}{dR_L} \left[\frac{V_s^2 R_L}{(R_s + R_L)^2 + (X_s + X_L)^2} \right] = 0$$

$$(R_s + R_L)^2 + (X_s + X_L)^2 - 2R_L(R_s + R_L) = 0$$

$$R_s^2 + R_L^2 + 2R_s R_L + X_s^2 + X_L^2 + 2X_s X_L - 2R_s R_L - 2R_L^2 = 0$$


$$R_s^2 - R_L^2 + X_s^2 + X_L^2 + 2X_s X_L = 0$$

$$\therefore R_L = \sqrt{R_s^2 + (X_s + X_L)^2}$$

$$(or) R_L = |Z_s + jX_L|$$

Case(4) :- AC src. with $Z_s = R_s + jx_s$ connected to

$$Z_L = R_L + jx_L$$

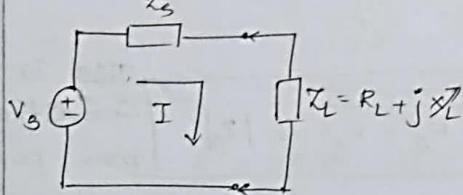

$$I = \frac{V}{Z_s + Z_L} = \frac{V_s}{(R_s + R_L) + j(x_s + x_L)}$$

$$|I| = \frac{V_s}{\sqrt{(R_s + R_L)^2 + (x_s + x_L)^2}}$$

$$\therefore P = |I|^2 R_L = \frac{\frac{V_s^2 R_L}{2}}{\sqrt{(R_s + R_L)^2 + (x_s + x_L)^2}} = \frac{V_s^2 R_L}{(R_s + R_L)^2 + (x_s + x_L)^2}$$

for max. power transfer, $\frac{\partial P}{\partial x_L} = 0$

$$0 - R_L [2(x_s + x_L)] = 0$$

$$x_s + x_L = 0$$


$$x_L = -x_s$$

The condition for max. power transfer is load reactance should be conjugate of source reactance. Under this condition,

$$P_{max} = \frac{V_s^2 R_L}{(R_s + R_L)^2 + (-x_s + x_L)^2}$$

$$P_{max} = \frac{V_s^2 R_L}{(R_s + R_L)^2}$$

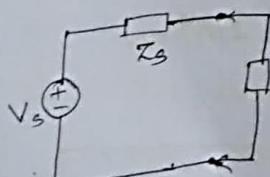~~7.7~~ Case(5) :- AC source with $Z_s = R_s + jx_s$ connected to a $Z_L = R_L + jx_L$



$$I = \frac{V_s}{(R_s + R_L) + j(x_s + x_L)}$$

$$|I| = \frac{V_s}{\sqrt{(R_s + R_L)^2 + (x_s + x_L)^2}}$$

$$P = |I|^2 R_L = \frac{V_s^2 R_L}{(R_s + R_L)^2 + (x_s + x_L)^2}$$

For max. power transfer, $\frac{dP}{dx_L} = 0$

$$\frac{d}{dx_L} \left[\frac{V_s^2 R_L}{(R_s + R_L)^2 + (x_s + x_L)^2} \right] = 0.$$

$$0 - R_L [0 + 2(x_s + x_L)] = 0.$$

$$x_s + x_L = 0$$

$$x_L = -x_s$$

The condition for max. power transfer is the load reactance should be conjugate of source reactance. Under this condition,

$$P_{\max} = \frac{V_s^2 R_L}{(R_s + R_L)^2}$$

$$\therefore \frac{dP}{dR_L} = 0,$$

$$\frac{d}{dR_L} \left[\frac{V_s^2 R_L}{(R_s + R_L)^2} \right] = 0$$

$$(R_s + R_L)^2 (1) - R_L [2(R_s + R_L)] = 0.$$

$$R_s^2 + R_L^2 + 2R_s R_L - 2R_s R_L - 2R_L^2 = 0$$

$$R_s^2 - R_L^2 = 0$$

$$R_s^2 = R_L^2$$

WKT,

$$Z_L = R_L + jx_L$$

$$\text{put, } R_L = R_s \quad \& \quad x_L = -x_s$$

$\therefore Z_L = R_s - jx_s$ \therefore The condition for max. power transfer is the load impedance should be complex conjugate of source impedance.

* Summary :-

i) $R_L = R_S = R_{Th}$




ii) $R_L = |Z_S|$

iii) $R_L = |Z_S + jX_L|$


iv) $X_L = -X_S$

v) $Z_L = Z_S^* = Z_{Th}^*$

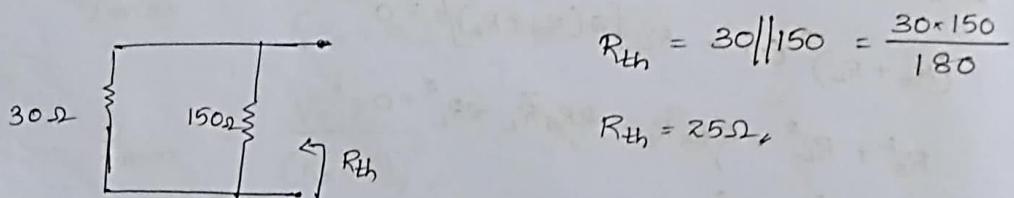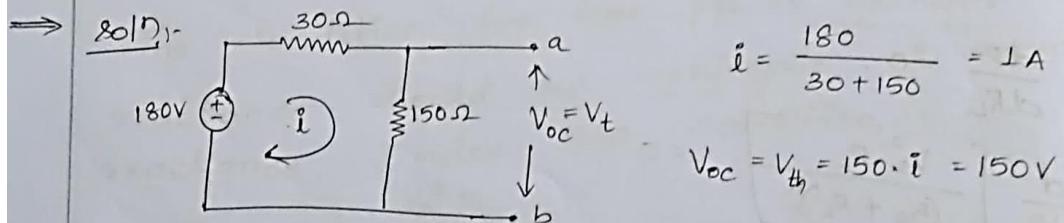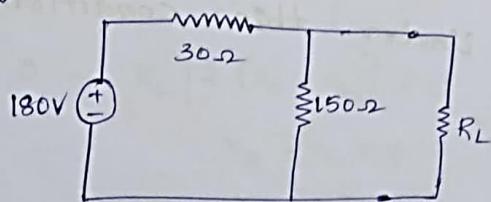1. Find the load ' R_L ' that will result in maximum power delivered to the load for the ckt. of fig. Also determine the max. power P_{max} .



Thévenin's ckt,

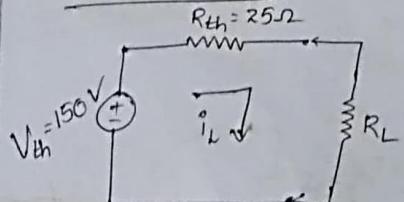

i. For max. power transfer,

$$R_L = R_{Th} = 25 \Omega$$

$$\therefore P_{max} = \frac{V_{Th}^2}{4R_L} = \frac{150^2}{4 \cdot 25}$$


$$P_{max} = 225 W$$

\therefore Total power, $P_t = 150 \cdot i_L$


$$P_t = 150 \cdot \left[\frac{150}{25+25} \right]$$

$$\boxed{P_t = 450 \text{ Watts}}$$

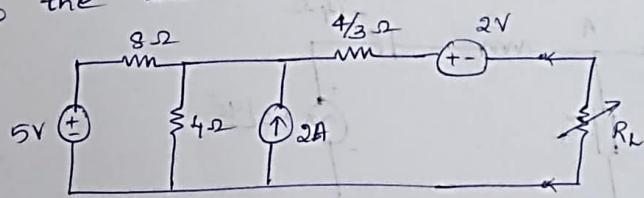2. Find the value of R_L for max. power to be transferred to the load. Also find max. power transferred.



\rightarrow Soln:- i) V_{th} :

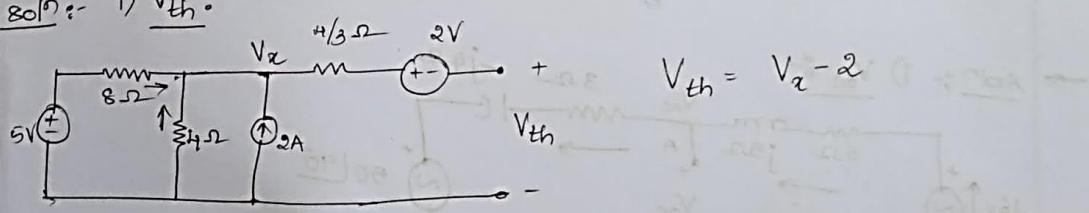

$$2 + \frac{0 - V_x}{4} + \frac{5 - V_x}{8} = 0$$


$$16 - 2V_x + 5 - V_x = 0$$

$$-3V_x = -21$$

$$V_x = 7 \text{ V}$$


$$\therefore V_{th} = 7 - 2 = 5 \text{ V}$$

ii) R_{th} :

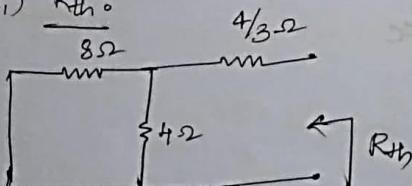

$$\begin{aligned} R_{th} &= \frac{4}{3} + [8 \parallel 4] \\ &= \frac{4}{3} + \frac{4 \times 8}{12} \\ &\Rightarrow R_{th} = 4\Omega \end{aligned}$$

Thévenin's ckt,

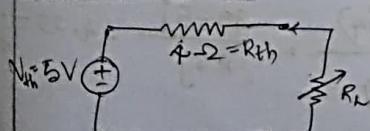

\therefore For max. power transfer, $R_L = R_{th}$


$$R_L = 4\Omega$$

\therefore Total power, $P_t = 150 \cdot i_L$


$$P_t = 150 \cdot \left[\frac{150}{25+25} \right]$$

$$\boxed{P_t = 450 \text{ Watts}}$$

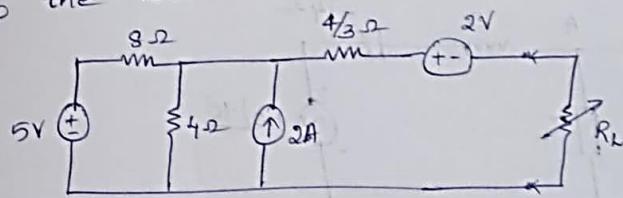2. Find the value of R_L for max. power to be transferred to the load. Also find max. power transferred.



→ Soln:- i) V_{th} :

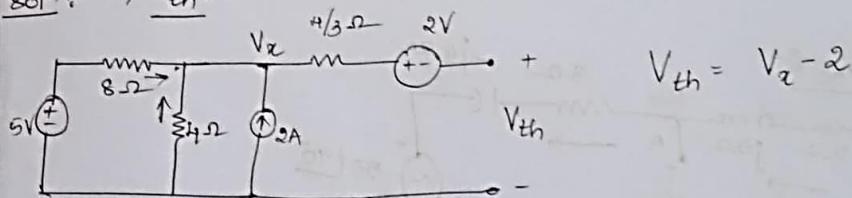

$$2 + \frac{0 - V_x}{4} + \frac{5 - V_x}{8} = 0$$


$$16 - 2V_x + 5 - V_x = 0$$

$$13V_x = 21$$

$$V_x = 7 \text{ V}$$


$$\therefore V_{th} = 7 - 2 = 5 \text{ V}$$

ii) R_{th} :

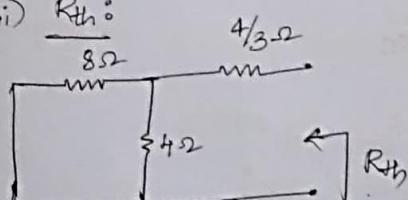

$$\begin{aligned} R_{th} &= \frac{4}{3} + [8 \parallel 4] \\ &= \frac{4}{3} + \frac{4 \times 8}{12} \\ &\Rightarrow R_{th} = 4\Omega \end{aligned}$$

Thevenin's ckt,

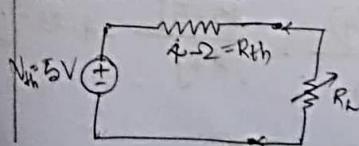

\therefore For max. power transfer, $R_L = R_{th}$

$$R_L = 4\Omega$$


Maximum power transfer, $P_{max} = I^2 R_L$

$$= 4 \times \left[\frac{5}{4+4} \right]$$


$$= \frac{20}{8}$$

$$\boxed{P_{max} = 1.5625 \text{ Watts}}$$

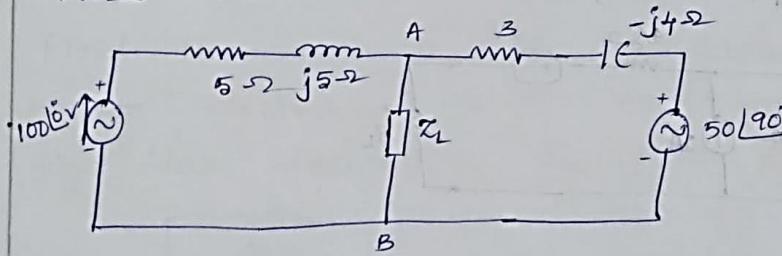May June 10
3. Find the max. P.T. to load Z_L of the n/w.



→ Sol :- i) V_{oc}

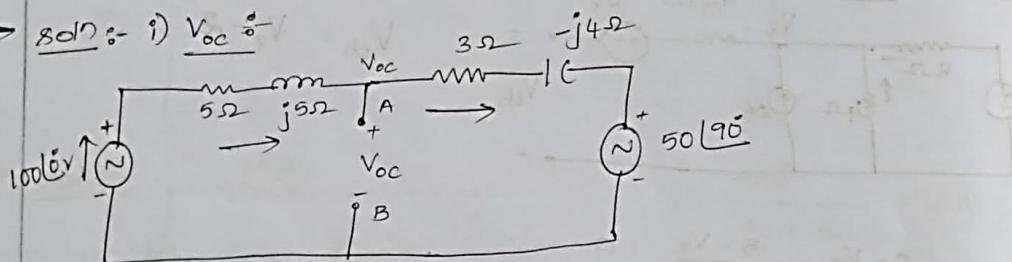

$$\frac{100\angle 0^\circ - V_{oc}}{5+j5} = \frac{V_{oc} - 50\angle 90^\circ}{3-j4}$$

$$(3-j4)(100) - (3-j4)V_{oc} = (5+j5)V_{oc} - 50j(5+j5)$$

$$(300 - j400) - (3-j4)V_{oc} - (5+j5)V_{oc} + 250j - 250 = 0$$


$$(50 - j150) = [3+5-j4+j5]V_{oc}$$

$$V_{oc} = \frac{50 - j150}{8 + j}$$

$$V_{oc} = (3.84 - 19.2j) V.$$

$$ii) Z_{th}: (5+j5) \parallel (3-j4) = \frac{(5+j5)(3-j4)}{5+j5+3-j4} = \frac{35-5j}{8+j} = 4.23 - 1.15j$$

Thevenin's ckt,

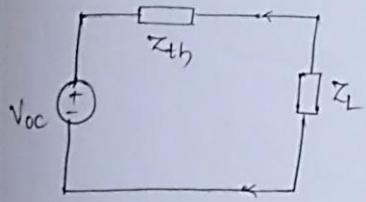

From fig., it belongs to case(s),

$$Z_L = Z_{th}^* = 4.23 + 1.15j$$

$$\therefore P_{max} = R_L \cdot I^2$$

$$I = \frac{3.84 - 19.2j}{4.23 - 1.15j + 4.23 + 1.15j} = 0.45 - 2.26j$$

∴