

## MODULE 4

## LAPLACE TRANSFORMATION AND APPLICATIONS

A transform is a change in the mathematical description of a physical variable to facilitate computation.

$$\mathcal{L}\{f(t)\} = F(s) = \int_0^{\infty} f(t) e^{-st} dt \rightarrow (1)$$


Time domain  
to freq.  
domain

\* Important functions:-

- i) Unit step function,  $u(t)$
- ii) Delta function,  $\delta(t)$
- iii) Ramp function,  $\sigma(t)$ .

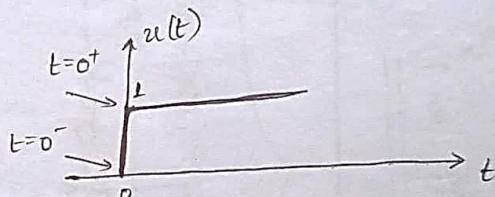
i) Unit step function,  $u(t)$ :

$$u(t) = \begin{cases} 0, & t \leq 0 \\ 1, & t \geq 0 \end{cases}$$




$$u(t) = \begin{cases} 0, & t \leq 0^+ \\ 1, & t \geq 0^- \end{cases}$$

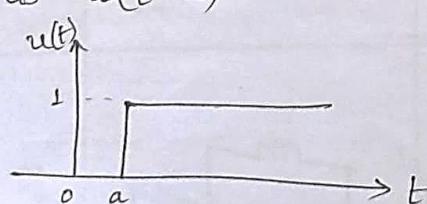Unit step function that occurs at  $t=a$  is expressed as  $u(t-a)$


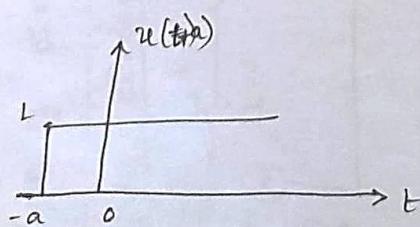
$$u(t-a) = \begin{cases} 0, & t-a < 0 \text{ or } t < a \\ 1, & t-a > 0 \text{ or } t > a \end{cases}$$



$$u(t+a) = \begin{cases} 0, & t+a < 0 \text{ or } t < -a \\ 1, & t+a > 0 \text{ or } t > -a \end{cases}$$



(ii) The derivative of the unit step function is the unit impulse function ' $\delta(t)$ '.

$$\delta(t) = \frac{d u(t)}{dt} = \begin{cases} 0 & t < 0 \\ \text{undefined} & t=0 \\ 0 & t > 0 \end{cases}$$

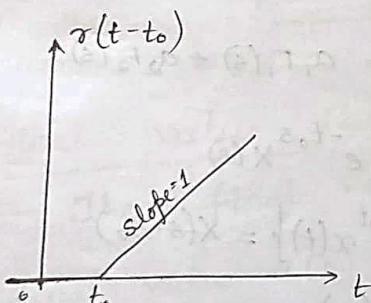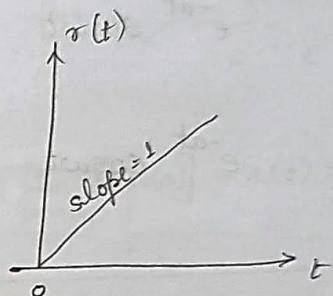
(iii) Integrating of unit step function is unit ramp function ' $r(t)$ '.

$$r(t) = \int_{-\infty}^t u(c) dc = t u(t)$$

$$r(t) = \begin{cases} 0 & t \leq 0 \\ t & t \geq 0 \end{cases}$$


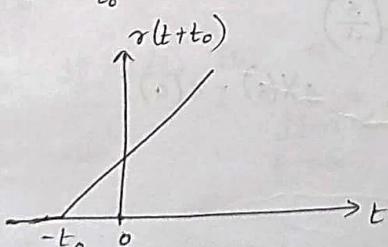
$$r(t-t_0) = \begin{cases} 0 & t \leq t_0 \\ t-t_0 & t \geq t_0 \end{cases}$$



$$r(t+t_0) = \begin{cases} 0 & t \leq -t_0 \\ t+t_0 & t \geq -t_0 \end{cases}$$

\* Laplace formulae

$f(t) \quad (t \geq 0)$	$F(s)$
$\delta(t)$	$1$
$u(t)$	$1/s$
$t$	$1/s^2$
$e^{-at}$	$1/s+a$

$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
$t^n$	$\frac{n!}{s^{n+1}}$
$t e^{-at}$	$\frac{1}{(s+a)^2}$
$e^{-at} \sin \omega t$	$\frac{\omega}{(s+a)^2 + \omega^2}$
$e^{-at} \cos \omega t$	$\frac{s+a}{(s+a)^2 + \omega^2}$

\* Properties of Laplace transform:-

1. Linearity :  $L\{a_1 f_1(t) + a_2 f_2(t)\} = a_1 F_1(s) + a_2 F_2(s)$ .
2. Time shifting :  $L\{x(t-t_0) u(t-t_0)\} = e^{-t_0 s} X(s)$ .
3. Frequency domain shifting :  $L\{e^{s_0 t} x(t)\} = X(s-s_0)$
4. Time scaling :  $L\{x(at)\} = \frac{1}{a} \times \left(\frac{s}{a}\right)$
5. Time differentiation :  $L\{\frac{dx(t)}{dt}\} = sX(s) - x(0)$ .
6. Integration in time-domain:  
If  $y(t) = \int_0^t x(c) dc$ .  
Then,  $L\{y(t)\} = Y(s) = \frac{X(s)}{s}$
7. Convolution :  $L\{x(t) * h(t)\} = X(s) \cdot H(s)$ .

\* Initial value theorem :-

Initial value theorem allow us to find the initial value  $x(0)$  directly from its L.T.  $X(s)$ .

$$x(0) = \lim_{s \rightarrow \infty} X(s)$$

Proof :-

(W.K.T.)

$$\mathcal{L} \left\{ \frac{dx(t)}{dt} \right\} = sX(s) - x(0) = \int_0^{\infty} \frac{dx}{dt} e^{-st} dt$$

$$= 0 \because e^{-\infty} = 0$$

If  $s \rightarrow \infty$ , then

$$\lim_{s \rightarrow \infty} [sX(s) - x(0)] = 0; \lim_{s \rightarrow \infty} [sX(s)] = x(0) = 0$$

$$\boxed{x(0) = \lim_{s \rightarrow \infty} [sX(s)]}$$

\* Final value theorem :-

The final value theorem allow us to find the final value  $x(\infty)$  directly from its LT  $X(s)$ .

If  $x(t)$  is a causal signal,

$$\lim_{t \rightarrow \infty} x(t) = \lim_{s \rightarrow 0} sX(s)$$

Proof :-

$$\mathcal{L} \left\{ \frac{dx(t)}{dt} \right\} = sX(s) - x(0) = \int_0^{\infty} \frac{dx}{dt} e^{-st} dt$$

$$\begin{aligned} \text{If } s \rightarrow 0 & \lim_{s \rightarrow 0} [sX(s) - x(0)] = \lim_{s \rightarrow 0} \int_0^{\infty} \frac{dx}{dt} e^{-st} dt \\ & = \int_0^{\infty} \frac{dx(t)}{dt} \left[ \lim_{s \rightarrow 0} e^{-st} \right] dt \end{aligned}$$

$$= \int_0^\infty \frac{dx(t)}{dt} dt$$

$$= x(t) \Big|_0^\infty$$

$$\Rightarrow x(\infty) - x(0)$$

$$\lim_{s \rightarrow 0} [sx(s) - x(0)] = \lim_{s \rightarrow 0} sx(s) - x(0)$$

$$x(\infty) - x(0) = \lim_{s \rightarrow 0} sx(s) - x(0)$$

$$\boxed{x(\infty) = \lim_{s \rightarrow 0} sx(s)}$$

\* Circuit element models & initial conditions:-


1. Resistor :-

$$v(t) = i(t) R$$

Take LT.

$$V(s) = I(s) R$$

$$(or) Z(s) = \frac{V(s)}{I(s)}$$

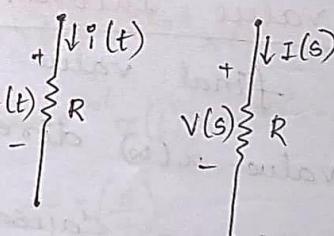

Z  $\xrightarrow{\text{only}}$  freq. domain


2. Capacitor :-

$$v(t) = \frac{1}{C} \int_0^t i(c) dc + v(0)$$

L.T.

$$V(s) = \frac{1}{Cs} I(s) + \frac{v(0)}{s}$$

To find impedance of 'C' set  $v(0) = 0$ ,  $\therefore Z(s) = \frac{V(s)}{I(s)} = \frac{1}{Cs}$

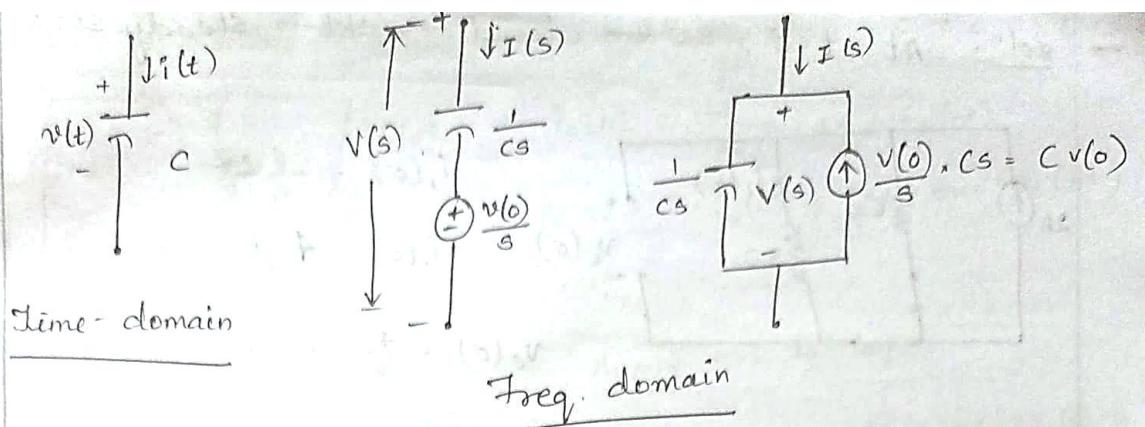3. Inductors


$$v(t) = L \frac{di(t)}{dt}$$

Take L.T


$$V(s) = Ls I(s) - Li(0)$$

To find impedance of an inductor, set  $i(0) = 0$ ,

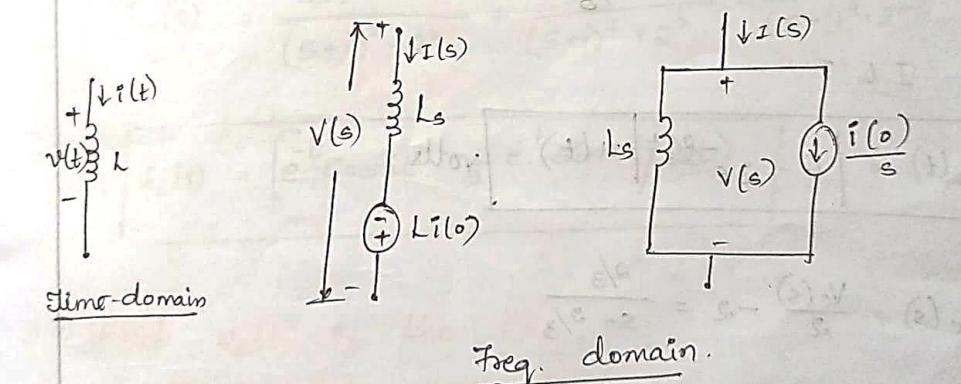
$$\therefore Z(s) = \frac{V(s)}{I(s)} = Ls.$$




1. Determine the voltage  $v_c(t)$  & the current  $i_c(t)$  for

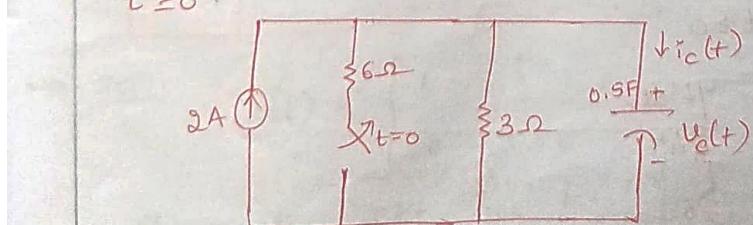 $t \geq 0$ .

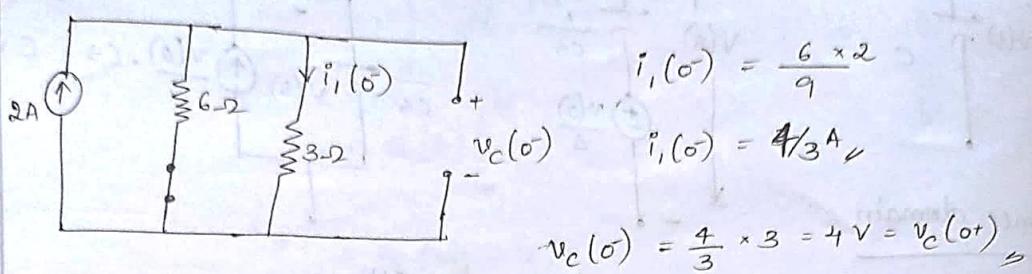solt: At  $t=0^-$ ; SW  $\rightarrow$  closed  $\rightarrow$  ckt  $\rightarrow$  steady state



Frequency domain representation is,

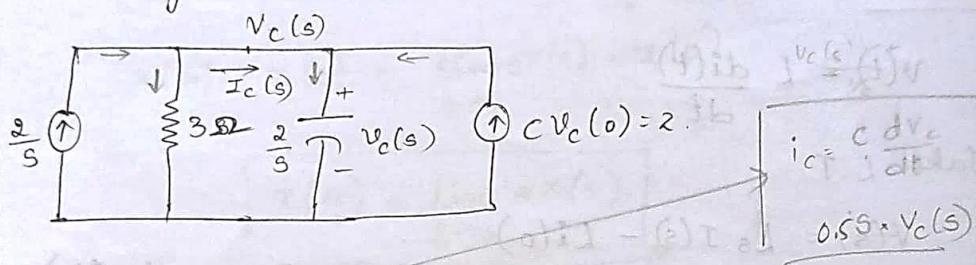

$$\frac{V_c(s)}{3} + \left[ \frac{s}{2} V_c(s) \right] = 2 + \frac{2}{s}$$

$$V_c(s) = \frac{6}{s} - \frac{2}{s+2/3}$$


I.C.T

$$v_c(t) = [6 - 2e^{-2/3 t}] u(t) \text{ volts}$$


$$\text{Also, } I_c(s) = \frac{V_c(s)}{2} - 2 = \frac{2/3}{s+2/3}$$

$$i_c(t) = \frac{2}{3} e^{-2/3 t} u(t) A$$

2. Determine  $i_L(t)$  for  $t \geq 0$

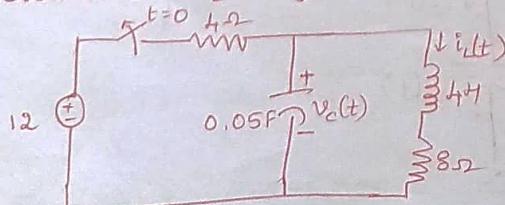

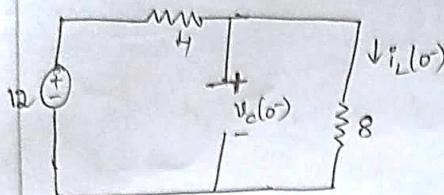$\Rightarrow$  At  $t=0^-$ :  $s \rightarrow \infty \rightarrow$  closed  $\rightarrow$  steady state,  $C \rightarrow 0, C; L \rightarrow \infty$




$$i_L(0) = \frac{12}{12} = 1A = i_L(0^+)$$

$$v_c(0^-) = 8 \times i_L(0^-) = 8 \times 1 = 8V = v_c(0^+).$$

At  $t=0^+$ :

Apply KVL to loop 2.

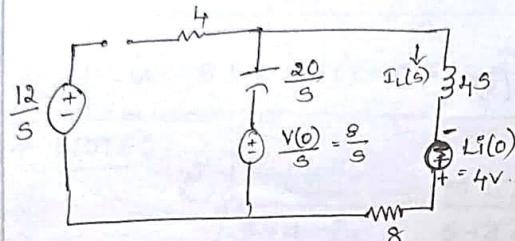

$$\frac{8}{s} - \frac{20}{s} I_L(s) - 4sI_L(s) + 4 - 8I_L(s) = 0$$

$$\frac{8}{s} + 4 = \left[ \frac{20}{s} + 4s + 8 \right] I_L(s)$$


$$I_L(s) = \frac{(8+4s)/s}{20+4s^2+8s}$$

$$I_L(s) = \frac{(s+2)A}{A(s^2+2s+5)} = \frac{s+2}{s^2+2s+5} = \frac{(s+1)+1}{(s+1)^2+2^2}$$

$$I_L(s) = \frac{s+1}{(s+1)^2+2^2} + \frac{1}{(s+1)^2+2^2} = \frac{s+1}{(s+1)^2+2^2} + \frac{1}{2} \times \frac{2}{(s+1)^2+2^2}$$

$$\therefore i_L(t) = \left[ e^{-t} \cos 2t + \frac{1}{2} e^{-t} \sin 2t \right] u(t)$$

3. Find  $v_o(t)$  of the ckt.

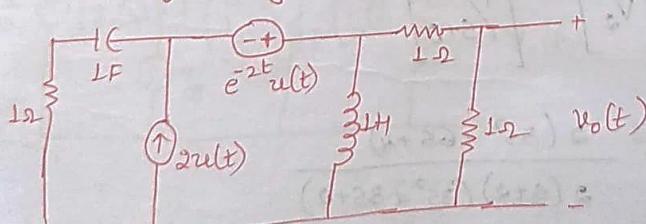

$$\Rightarrow \text{So if } u(t) = \begin{cases} 1, & t \geq 0^+ \\ 0, & t \leq 0^- \end{cases}$$


Since the ckt has two independent sources energized by 'u(t)', the ckt is inactive for  $t \leq 0^-$ .  $\therefore$  initial

conditions are zero

$$\therefore i_L(0^-) = i_L(0^+) = 0$$

$$v_c(0^-) = v_c(0^+) = 0$$

At  $t = 0^+$ :

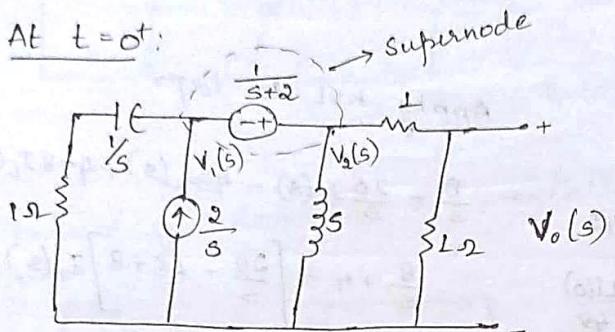

KCL at supernode:

$$\frac{V_1(s)}{1 + \frac{1}{s}} + \frac{V_2(s)}{s} + \frac{V_2(s)}{2} = \frac{2}{s}$$

$$V_1(s) \left\{ \frac{s}{s+1} \right\} + V_2(s) \left\{ \frac{2+s}{2s} \right\} = \frac{2}{s} \rightarrow (1)$$

$\therefore$  The constraint eqn. is,  $V_2 - V_1 = \frac{1}{s+2} \rightarrow (2)$

Solve (1) & (2)

$$\begin{bmatrix} \frac{s}{s+1} & \frac{2+s}{2s} \\ -1 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \frac{2}{s} \\ \frac{1}{s+2} \end{bmatrix}$$

$$\therefore V_o(s) = \frac{1}{2} V_2(s) = \frac{2(3s^2 + 6s + 4)}{2(s+2)(3s^2 + 3s + 2)}$$

$$V_o(s) = \frac{\left[ s^2 + 2s + \frac{4}{3} \right]}{(s+2)[s+0.5-j0.646][s+0.5+j0.646]}$$

$$V_o(s) = \frac{k_1}{s+2} + \frac{k_2}{s+0.5-j0.646} + \frac{k_2^*}{s+0.5+j0.646}$$

$$\therefore k_1 = 0.5 \text{ & } k_2 = 0.316 \underline{[-37.76]}$$


$$\therefore V_o(s) = \frac{0.5}{s+2} + \frac{0.316 \underline{[-37.76]}}{s+0.5-j0.646} + \frac{0.316 \underline{[37.76]}}{s+0.5+j0.646}$$

$$\therefore \boxed{V_o(t) = 0.5 e^{-2t} u(t) + 0.632 e^{-0.5t} \cos [0.646t - 37.76] u(t)}$$


\* NOTE:

$$\mathcal{L}^{-1} \left\{ \frac{m \angle 0}{s+a-j\omega} + \frac{m \angle -0}{s+a+j\omega} \right\} = 2me^{-at} \cos(\omega t + \theta) u(t)$$

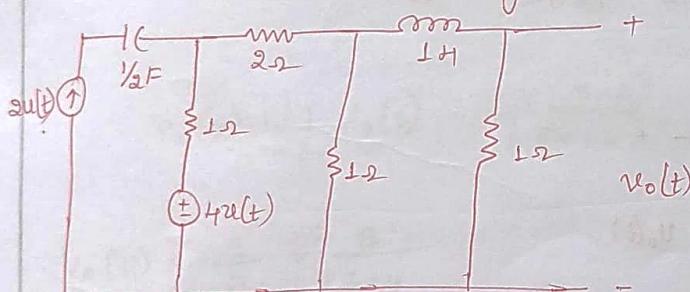4. Find  $v_o(t)$ ,  $t > 0$  using mesh eqns.


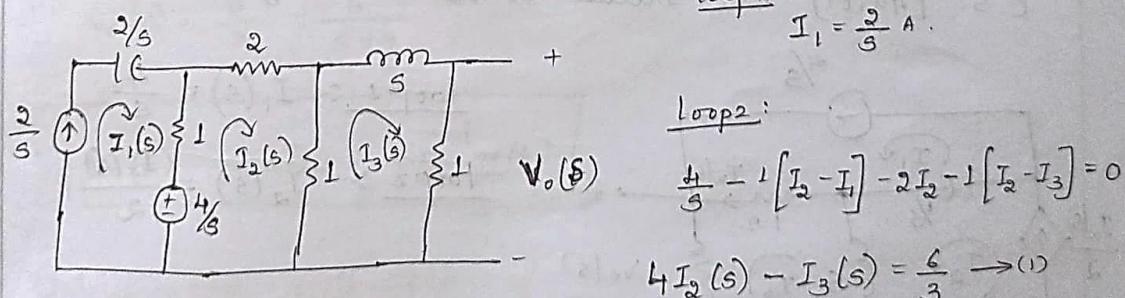
$$\Rightarrow \text{Soln: } u(t) = \begin{cases} 1 & t \geq 0^+ \\ 0 & t \leq 0^- \end{cases}$$



$$\text{Loop 3: } -1[I_3 - I_2] - sI_3 - 1 \cdot I_3 = 0$$

$$+ I_2 - [s+2]I_3 = 0 \rightarrow (2)$$

$$\text{Solve (1) \& (2), } I_3 = \frac{1.5}{s[s + \sqrt{\frac{5}{4}}]}$$

$$\therefore V_o(s) = 1 \cdot I_3(s) + 1 \cdot \frac{1.5}{s + \frac{7}{4}}$$


$$V_o(s) = \frac{k_1}{s} + \frac{k_2}{s + \frac{7}{4}}$$

$$\therefore k_1 = 6/7 \quad \& \quad k_2 = -6/7$$


$$\therefore V_o(s) = \frac{6/7}{s} - \frac{6/7}{s + \frac{7}{4}}$$

$$\boxed{V_o(t) = \frac{6}{7} \left[ 1 - e^{-\frac{7}{4}t} \right] u(t)}$$

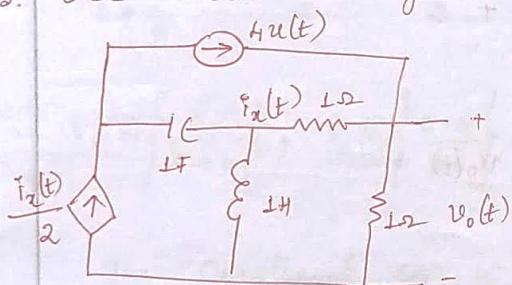5. Use mesh analysis & find  $v_o(t)$ ,  $t > 0$



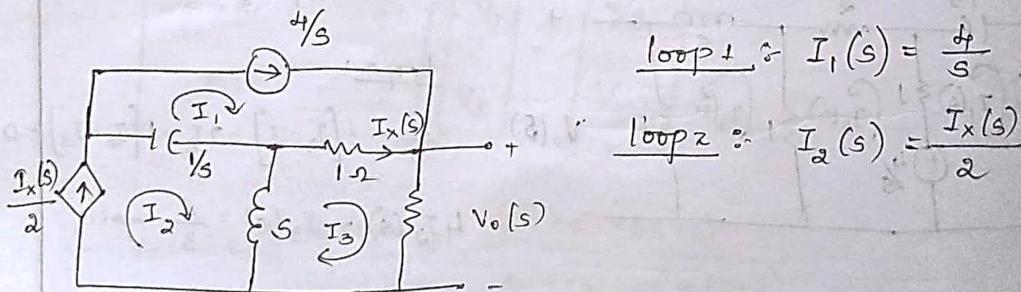→ soln. At  $t \leq 0^-$ : ckt is not energized  $\therefore$  of independent C.S.  $[4u(t)]$   $\therefore$  Initial conditions are zero.



$$\text{But } I_x(s) = I_3 - I_1 = I_3 - \frac{4}{s}$$

$$\therefore I_2(s) = \frac{1}{2} \left[ I_3 - \frac{4}{s} \right]$$

Loop 3 :-

$$-s [I_3 - I_2] - 1 [I_3 - I_1] - I_3 = 0$$

$$s[I_3 - I_2] + 1 [I_3 - I_1] + I_3 = 0$$

$$-I_1 - sI_2 + [s+2]I_3 = 0$$

$$-\frac{4}{s} - s \left[ \frac{1}{2} \left\{ I_3 - \frac{4}{s} \right\} \right] + [s+2]I_3 = 0$$

$$-\frac{4}{s} - \frac{s}{2}I_3 + 2 + (s+2)I_3 = 0$$

$$\left[ -\frac{4}{s} + 2 \right] + \left[ s+2 - \frac{s}{2} \right] I_3 = 0$$

$$I_3 = \frac{-\left[ \frac{2s-4}{s} \right]}{\frac{2s+4-s}{2}} = \frac{-4[s-2]}{[4+s]s}$$

$$\therefore V_o(s) = 1 \cdot I_3(s) = \frac{-4(s-2)}{s(s+4)}$$


$$V_o(s) = \frac{A}{s} + \frac{B}{s+4}$$

$$\therefore A = 2, B = -6$$


$$\therefore V_o(s) = \frac{2}{s} - \frac{6}{s+4}$$

$$\therefore \boxed{V_o(t) = 2u(t) - 6e^{-4t}u(t)}$$

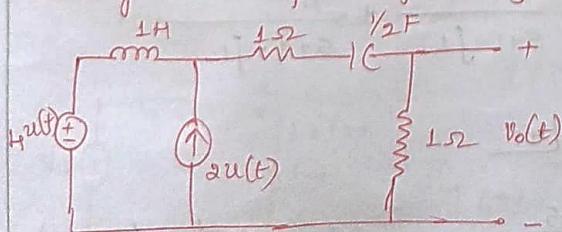6. Using the principle of superposition, find  $v_o(t)$  for  $t > 0$



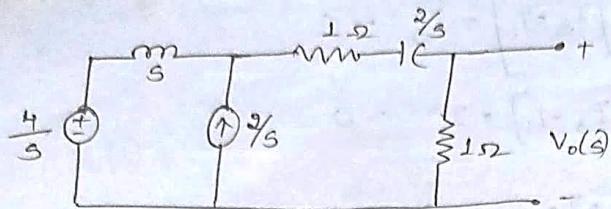Soln: At  $t \leq 0^-$ ; no initial condition.



Case(1): Let  $\frac{4}{s}$  be present

$$\text{Circuit diagram for Case(1) with } \frac{4}{s} \text{ present:}$$

$$\therefore I(s) = \frac{\frac{4}{s}}{s+1+\frac{2}{s}+1} = \frac{\frac{4}{s}}{s^2+2s+2}$$

$$\therefore V_{o1}(s) = I(s) = \frac{4}{s^2+2s+2}$$

$$I(s) = \frac{4}{s^2+2s+2}$$

Case(2): Let  $\frac{2}{s}$  be present

$$\text{Circuit diagram for Case(2) with } \frac{2}{s} \text{ present:}$$

$$I_1(s) = \frac{s \times \frac{2}{s}}{s+1+\frac{2}{s}+1} = \frac{2s}{s^2+2s+2}$$

$$\therefore V_{o2}(s) = I_1(s) = \frac{2s}{s^2+2s+2}$$

$$\therefore V_o(s) = V_{o1}(s) + V_{o2}(s)$$


$$= \frac{4}{s^2+2s+2} + \frac{2s}{s^2+2s+2}$$

$$\therefore = \frac{4+2s}{s^2+2s+2} = \frac{A}{s+1-j\omega} + \frac{A^*}{s+1+j\omega}$$

$$\therefore A = \sqrt{2} \angle -45^\circ; A^* = \sqrt{2} \angle 45^\circ$$

$$V_o(s) = \frac{\sqrt{2} \angle -45^\circ}{s+1-j\omega} + \frac{\sqrt{2} \angle 45^\circ}{s+1+j\omega}; V_o(t) = 2\sqrt{2} e^{-t} \cos(t+45^\circ) u(t)$$

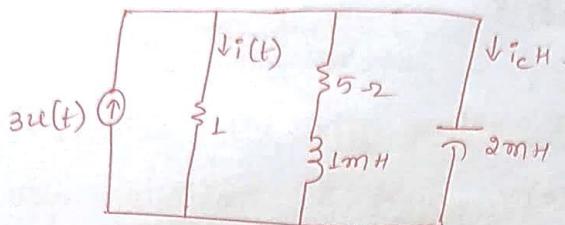
7. a) Convert the ckt. to an appropriate 's' domain representation.  
 b) Find thevenin equivalent seen by  $L_2$  resistor  
 c) Analyze the simplified ckt. to find an expression for  $i(t)$




$\Rightarrow$  soln:-

- a) At  $t \leq 0$ ; ckt. is not active.  $\therefore$  the initial conditions are zero.

At  $t \geq 0^+$ :

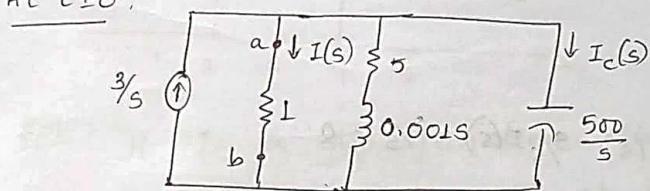

- b) Thevenin's equivalent:-

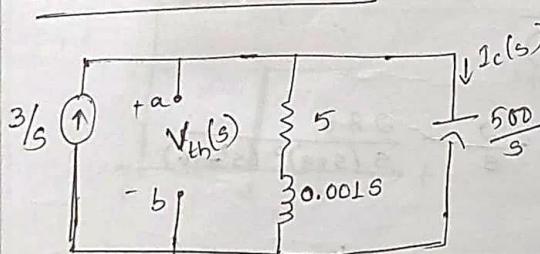


$$\therefore Z_{th}(s) = (5 + 0.001s) \parallel \frac{500}{s}$$

$$L = \frac{2500 + 0.5s}{0.001s^2 + 5s + 500} \Omega$$

$$V_{th}(s) = Z_{th}(s) \cdot \frac{3}{s}$$

$$I(s) = \frac{7.5 \times 10^6 + 1500s}{s(s^2 + 5000s + 5 \times 10^5)}$$

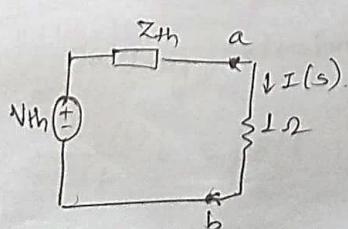$\therefore$  Thevenin's equivalent ckt. is,




$$I(s) = \frac{V_{th}}{Z_{th} + L} = \frac{7.5 \times 10^6 + 1500s}{s(s+4886)(s+614)}$$

$$\therefore I(s) = \frac{2.5}{s} + \frac{0.008}{s+4886} + \frac{2.508}{s+614}$$


$$\therefore i(t) = [2.5 + 0.008e^{-4886t} - 2.508e^{-614t}] u(t)$$

8. Find the complete response for

Take  $v(0) = 2V$

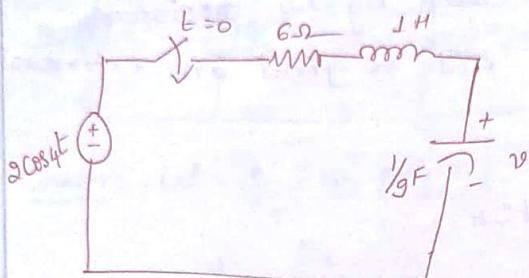

→ Soln:

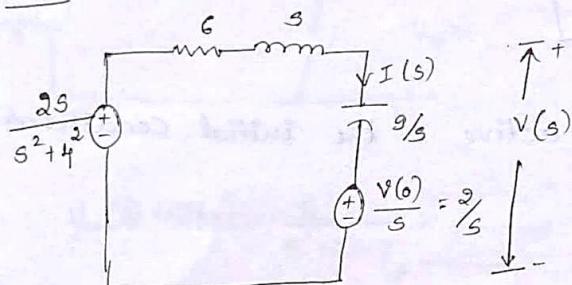

Apply KVL,

$$\frac{2s}{s^2+4^2} - 6I(s) - sI(s) - \frac{9}{s}I(s) - \frac{2}{s} = 0$$

$$\therefore I(s) = \frac{-32}{(s^2+6s+9)(s^2+16)}$$

$$\text{Hence, } V(s) = \frac{2}{s} + \frac{9}{s} I(s) = \frac{2}{s} - \frac{288}{s(s+3)^2(s^2+16)}$$

$$\therefore V(s) = \frac{2}{s} + \frac{k_1}{s} + \frac{k_2}{s+3} + \frac{k_3}{(s+3)^2} + \frac{k_4}{s-j4} + \frac{k_4'}{s+j4}$$

$$\therefore k_1 = \left. \frac{-288}{(s+3)^2(s^2+16)} \right|_{s=0} = -2$$

$$k_2 = -2.2$$

$$k_3 = 3.84$$

$$k_4 = 0.36 \quad \underline{-106.2}$$


$$k_5 = 0.36 \quad \underline{106.2}$$

$$V(s) = \frac{2}{s} - \frac{2}{s} + \frac{2.2}{s+3} + \frac{3.84}{(s+3)^2} + \frac{0.36(-106.2)}{s-j4} + \frac{0.36(106.2)}{s+j4}$$


$$\therefore v(t) = [2.2e^{-3t} + 3.84te^{-3t} + 0.72 \cos(4t - 106.2^\circ)] u(t)$$

\* Waveform Synthesis :-

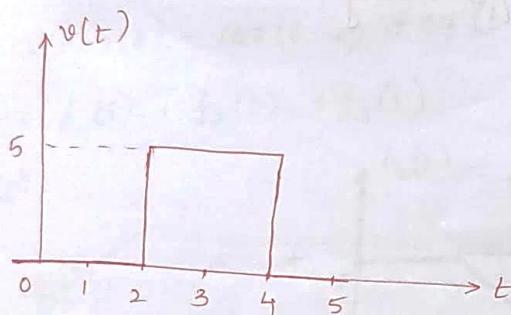1. Express the v(tg. pulse in fig. in terms of unit step function & find  $V(s)$ . Also find  $\mathcal{L}\left\{\frac{dv(t)}{dt}\right\}$ .



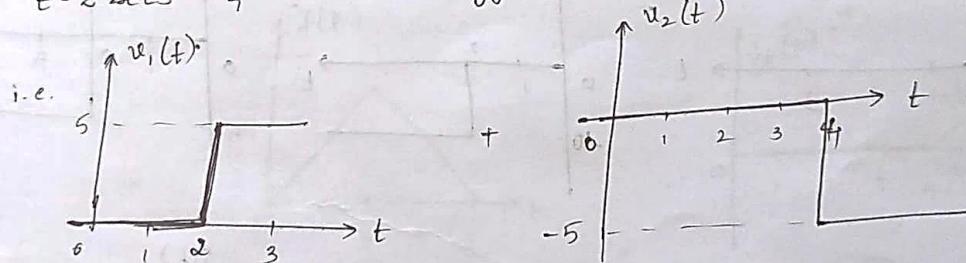→ Soln: It is a step function, that switches on at  $t=2$  secs & switches off at  $t=4$  secs.




$$\therefore v(t) = v_1(t) + v_2(t)$$

$$\mathcal{L} = 5u(t-2) - 5u(t-4).$$

$$V(s) = \frac{5}{s} e^{-2s} - \frac{5}{s} e^{-4s} = \frac{5}{s} \left[ e^{-2s} - e^{-4s} \right].$$

Taking derivative of  $v(t)$ , yields.

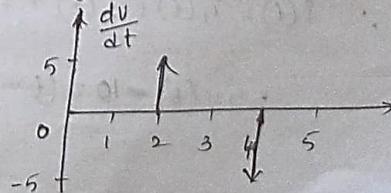
$$\frac{dv(t)}{dt} = 5 [\delta(t-2) - \delta(t-4)]$$









$$\mathcal{L}\{\delta(t-a)\} = e^{-as} \quad \mathcal{L}\{\delta(t)\} = e^{0s}$$

$$\begin{aligned} \mathcal{L}\left\{\frac{du(t)}{dt}\right\} &= \mathcal{L}\left\{5[\delta(t-2) - \delta(t-4)]\right\} \\ &= 5[e^{-2s} - e^{-4s}] \end{aligned}$$

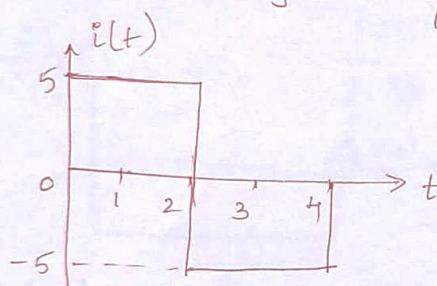2. Express the current pulse in terms of unit step functions  
 Find (i)  $\mathcal{L}\{i(t)\}$  (ii)  $\mathcal{L}\{\int i(t)dt\}$ .



$\Rightarrow$  Soln:-

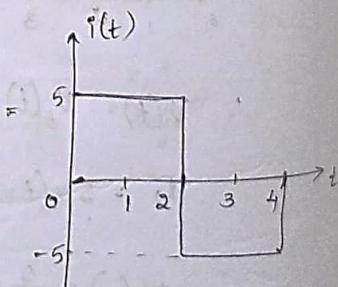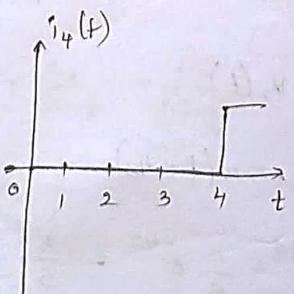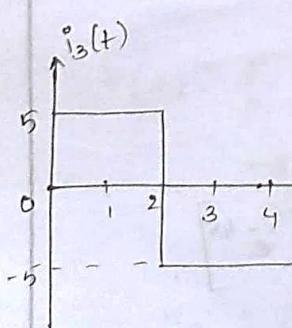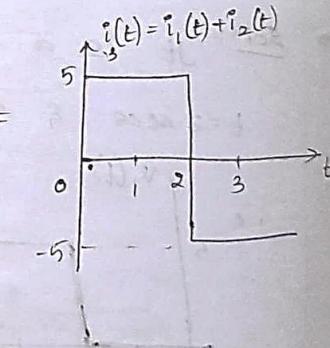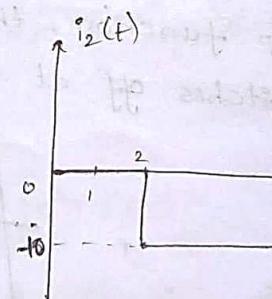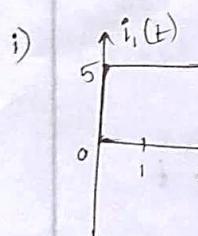

$$\therefore i(t) = i_1(t) + i_2(t) + i_3(t)$$

$$= 5u(t) - 10u(t-2) + 5u(t-4)$$

$$\therefore I(s) = \frac{5}{s} - \frac{10}{s} e^{-2s} + \frac{5}{s} e^{-4s}$$

$$= \frac{5}{s} [1 - 2e^{-2s} + e^{-4s}]$$






$$\Leftrightarrow = \frac{5}{s} [1 - e^{-2s}]^2$$

ii)  $f(t) = \int i(t) dt$

$$= \int [5u(t) - 10e^{-(t-2)} + 5u(t-4)] dt$$

$$= 5\tau(t) - 10\tau(t-2) + 5\tau(t-4)$$
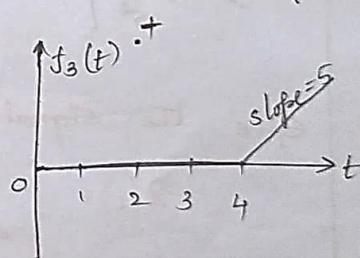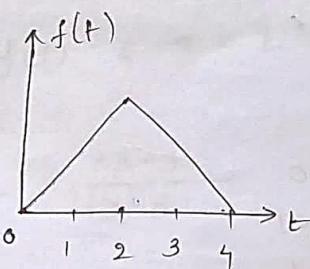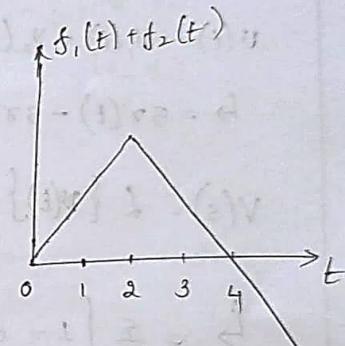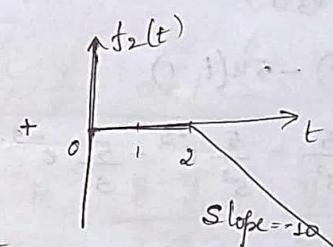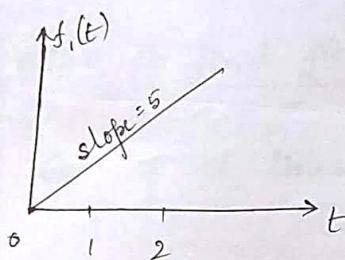
$$\Leftrightarrow = f_1(t) + f_2(t) + f_3(t)$$





$$\therefore L[f(t)] = L[5\tau(t) - 10\tau(t-2) + 5\tau(t-4)]$$

$$= \frac{5}{s^2} - \frac{10}{s^2} e^{-2s} + \frac{5}{s^2} e^{-4s}$$

$$\Leftrightarrow = \frac{5}{s^2} [1 - 2e^{-2s} + e^{-4s}]$$

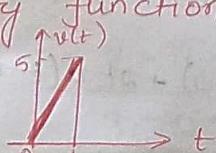3. Express the sawtooth function in terms of singularity function. Then find  $L\{v(t)\}$ .



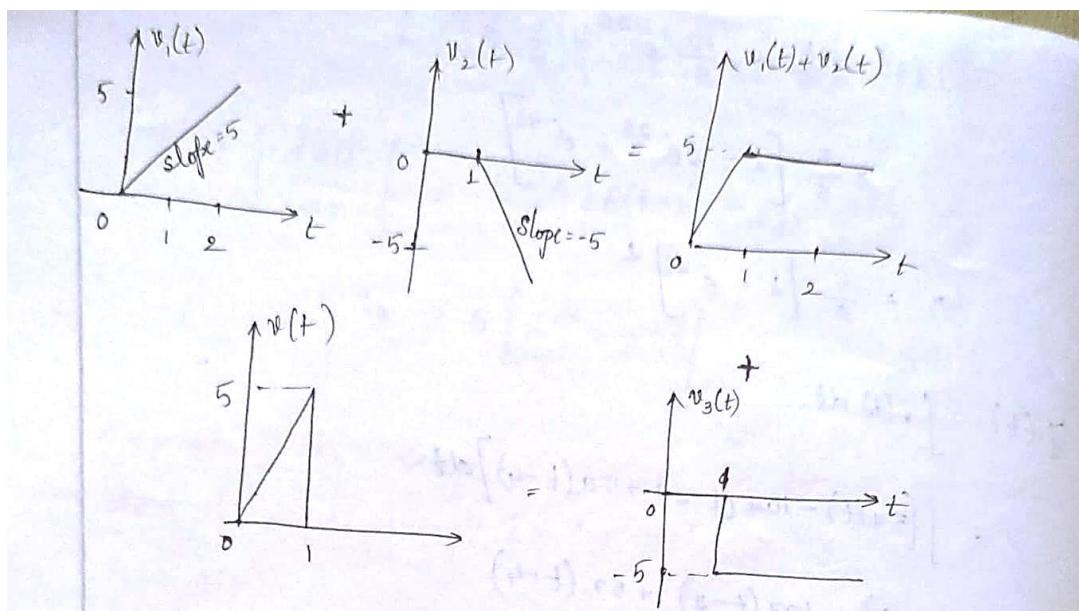

$$v(t) = v_1(t) + v_2(t) + v_3(t)$$

$$\Rightarrow 5\delta(t) - 5\delta(t-1) - 5u(t-1)$$

$$V(s) = \mathcal{L}\{v(t)\} = \frac{5}{s^2} - \frac{5}{s} e^{-s} - \frac{5}{s} e^{-s}$$

$$\therefore = \frac{5}{s^2} \left[ 1 - e^{-s} - s e^{-s} \right]$$

4. Give the signal,

$$x(t) = \begin{cases} 3 & t < 0 \\ -2 & 0 < t < 1 \\ 2t-4 & t > 1 \end{cases}$$

Express  $x(t)$  in terms of singularity functions. Also find  $\mathcal{L}\{x(t)\}$ .

$\Rightarrow$  soln: i) At  $t < 0$ ,  $x(t) = 3u(-t)$

$$\text{ii)} \quad 0 < t < 1, \quad x(t) = -2 [u(t) - u(t-1)]$$



$$\text{iii)} \quad t > 0, \quad x(t) = (2t-4)u(t-1)$$

$$\therefore x(t) = 3u(-t) - 2[u(t) - u(t-1)] + (2t-4)u(t-1)$$

$$= 3[1 - u(t)] - 2u(t) + 2u(t-1) + 2t u(t-1) - 4u(t-1)$$

$$\begin{aligned}x(t) &= 3 - 5u(t) - 2u(t-1) + 2(t-1+1)u(t-1) \\&= 3 - 5u(t) - 2u(t-1) + 2(t-1)u(t-1) + 2u(t-1) \\&\hookrightarrow 3 - 5u(t) + 2\delta(t-1)\end{aligned}$$

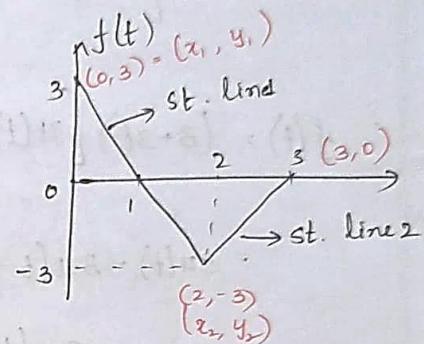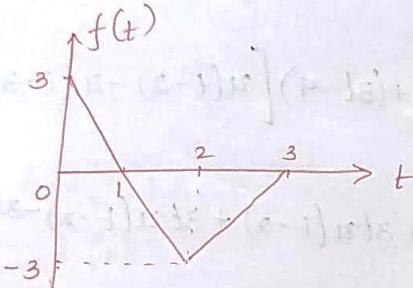5. Express 'f(t)' in terms of singularity functions & then find F(s).



$\Rightarrow$  soln:- To find  $f(t)$  for  $0 < t < 2$ :

$$\text{Eqn. of st. line 1 is, } \frac{y-y_1}{x-x_1} = \frac{y_2-y_1}{x_2-x_1}$$

Here,  $y(t) = f(t)$  &  $x = t$

$$\frac{f(t)-3}{t-0} = \frac{-3-3}{2-0}$$

$$\frac{f(t)-3}{t} = \frac{-6}{2}$$

$$2[f(t)-3] = -6t$$

$$f(t)-3 = -3t$$

$$(00) \quad f(t) = -3t + 3$$

For  $2 < t < 3$ :

$$\text{St. line 2, } \frac{y_1-y_2}{x_1-x_2} = \frac{y_3-y_2}{x_3-x_2}, \frac{f(t)+3}{t-2} = \frac{0+3}{3-2}$$

$$f(t) + 3 = 3t - 6$$

$$f(t) = 3t - 9$$

$$f(t) = \begin{cases} 3-3t & 0 < t < 2 \\ 3t-9 & 2 < t < 3 \\ 0 & \text{otherwise} \end{cases}$$

$$f(t) = (3-3t)[u(t) - u(t-2)] + (3t-9)[u(t-2) - u(t-3)]$$

$$= 3u(t) - 3u(t-2) - 3tu(t) + 3tu(t-2) + 3tu(t-2) - 3tu(t-3) \\ - 9u(t-2) + 9u(t-3)$$

$$= 3u(t) - 3tu(t) - 12u(t-2) + 6tu(t-2) - 3tu(t-3) + 9u(t-3)$$

$$= 3u(t) - 3tu(t) - 12u(t-2) + 9u(t-3) + 6(t-2)u(t-2) \\ - 3(t+3-3)u(t-3)$$

$$= 3u(t) - 3tu(t) - 12u(t-2) + 9u(t-3) + 6(t-2)u(t-2) \\ - 3(t-3)u(t-3) + 9u(t-3)$$

$$\therefore f(t) = 3u(t) - 3tu(t) + 6(t-2)u(t-2) - 3(t-3)u(t-3)$$

$$\therefore F(s) = \frac{3}{s} - \frac{3}{s^2} + \frac{6}{s^2} e^{-2s} - \frac{3}{s^2} e^{-3s}$$

6. Express the function  $f(t)$  using singularity functions & find  $F(s)$



→ Soln:


$$\frac{f_1(t) + 1}{t - 1} = \frac{-2 + 1}{2 - 1}$$

$$\frac{f_1(t) + 1}{t - 1} = \frac{-1}{1}$$

$$f_1(t) + 1 = 1 - t$$

$$f_1(t) = -t \quad [t \text{ lying b/w '1' & '2'}]$$

$$\therefore f(t) = f_1(t) g(t)$$

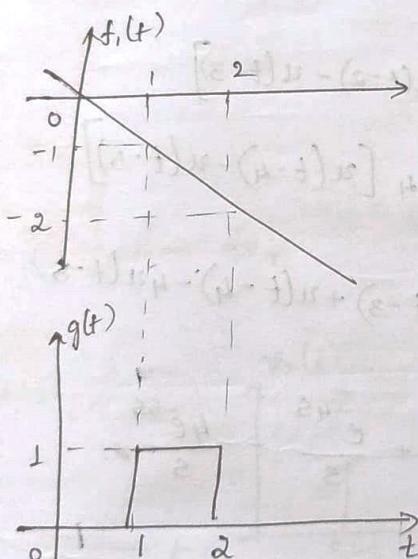

$$f(t) = -t [u(t-1) - u(t-2)]$$

$$f(t) = -tu(t-1) + tu(t-2)$$


$$f(t) = -(t-1+1)u(t-1) + (t-2+2)u(t-2)$$

$$= -(t-1)u(t-1) - u(t-1) + (t-2)u(t-2) + 2u(t-2)$$

$$\therefore f(t) = -\sigma(t-1) - u(t-1) + \sigma(t-2) + 2u(t-2)$$

$$\therefore F(s) = \frac{-1}{s^2} e^{-s} - \frac{1}{s} e^{-s} + \frac{1}{s^2} e^{-2s} + \frac{2e^{-2s}}{s}$$

- Q. a) Find the L.T. of the staircase w/f. [fig. a]  
 b) If this vfg. were applied to an RL series ckt.

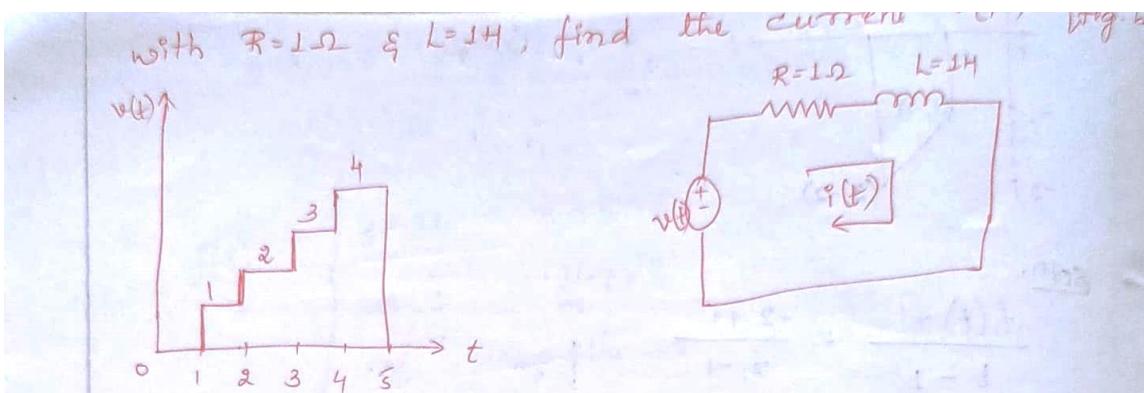
Fig(a) $\rightarrow$  soln:-

$$(a) \quad v(t) = \begin{cases} 1 & 1 < t < 2 \\ 2 & 2 < t < 3 \\ 3 & 3 < t < 4 \\ 4 & 4 < t < 5 \\ 0 & \text{elsewhere} \end{cases}$$

$$v(t) = [u(t-1) - u(t-2)] + 2[u(t-2) - u(t-3)] \\ + 3[u(t-3) - u(t-4)] + 4[u(t-4) - u(t-5)]$$

$$\therefore v(t) = u(t-1) + u(t-2) + u(t-3) + u(t-4) - 4u(t-5)$$
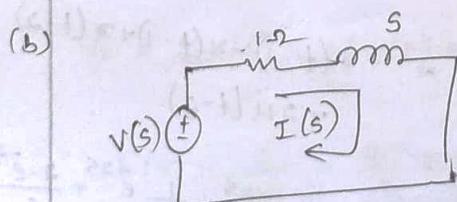
$$\therefore V(s) = \frac{1}{s}e^{-s} + \frac{e^{-2s}}{s} + \frac{e^{-3s}}{s} + \frac{e^{-4s}}{s} - \frac{4e^{-5s}}{s}$$



$$\therefore I(s) = \frac{V(s)}{s+1}$$


$$\therefore I(s) = \frac{e^{-s}}{s(s+1)} + \frac{e^{-2s}}{s(s+1)} + \frac{e^{-3s}}{s(s+1)} + \frac{e^{-4s}}{s(s+1)} - \frac{4e^{-5s}}{s(s+1)}$$

$$= \left[ \frac{1}{s} - \frac{1}{s+1} \right] e^{-s} + \left[ \frac{1}{s} - \frac{1}{s+1} \right] e^{-2s} + \left[ \frac{1}{s} - \frac{1}{s+1} \right] e^{-3s} + \left[ \frac{1}{s} - \frac{1}{s+1} \right] e^{-4s} + 4 \left[ \frac{1}{s} - \frac{1}{s+1} \right] e^{-5s}$$

$$\begin{aligned}
 i(t) &= [u(t) - e^{-t} u(t)]_{t \rightarrow t-1} + [u(t) - e^{-t} u(t)]_{t \rightarrow t-2}^+ \xrightarrow{\text{doubt}} \\
 &\quad [u(t) - e^{-t} u(t)]_{t \rightarrow t-3} + [u(t) - e^{-t} u(t)]_{t \rightarrow t-4} \\
 &\quad - 4[u(t) - e^{-t} u(t)]_{t \rightarrow t-5} \\
 &= [1 - e^{-(t-1)}] u(t-1) + [1 - e^{-(t-2)}] u(t-2) + [1 - e^{-(t-3)}] u(t-3) \\
 &\quad + [1 - e^{-(t-4)}] u(t-4) + 4[1 - e^{-(t-5)}] u(t-5).
 \end{aligned}$$

8. A vtg. pulse of 10V magnitude & 5msc duration is applied to RC n/w. Find  $i(t)$  if  $R = 10\Omega$  &

$$C = 0.05 \mu F$$

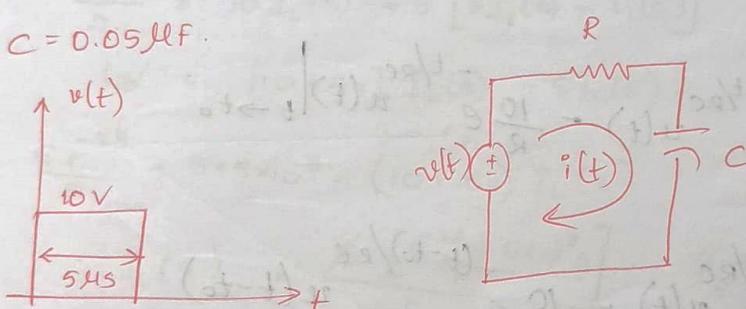

$\Rightarrow$

$$\frac{80t}{10} \text{ V}$$

$$v_1(t)$$

$$10$$

$$10$$

$$10$$

$$10$$

$$I(s) = \frac{10 [1 - e^{-t_0 s}]}{s [R + \frac{1}{C s}]}$$

$$\begin{aligned} I(s) &= \frac{10 C s}{s(RCs + 1)} \cdot (1 - e^{-t_0 s}) \\ &= \frac{10}{R} \left[ \frac{1}{s + \frac{1}{RC}} \right] (1 - e^{-t_0 s}) \end{aligned}$$

$$\hookrightarrow = \frac{10}{R} \left[ \frac{1}{s + \frac{1}{RC}} - \frac{e^{-t_0 s}}{s + \frac{1}{RC}} \right]$$

ILT

$$i(t) = \frac{10}{R} e^{-\frac{t}{RC}} u(t) - \frac{10}{R} e^{-\frac{t-t_0}{RC}} u(t) \Big|_{t \rightarrow t_0}$$

$$\hookrightarrow = \frac{10}{R} e^{-\frac{t}{RC}} u(t) - \frac{10}{R} e^{-\frac{(t-t_0)}{RC}} u(t-t_0)$$

$$\therefore i(t) = e^{-\frac{t}{0.5 \times 10^6}} u(t) - e^{-\frac{[t-5 \times 10^6]}{0.5 \times 10^6}} u(t-5 \times 10^6)$$